

Homework 5

1. Purpose: Understanding the common-emitter amplifier.

In the circuit below, assume the *npn* BJT is operating in forward-active mode. Let $\beta = 130$, $V_A = 60$ V, and $V_{BE} = 0.7$ V. Assume the capacitors have negligible impedance at the frequency of the ac signal.

Given, $V_{CC}=12$ V, $R_{sig}=1$ k Ω , $R_1=240$ k Ω , $R_2=160$ k Ω , $R_C=15$ k Ω and $R_L=100$ k Ω

(a) What are the purposes of capacitors C_1 , C_2 , and C_3 in this circuit?

(b) Determine all DC terminal voltages and currents as well as the small-signal voltage gain $A_v (=v_o/v_{sig})$ of the amplifier circuit if $R_E = 12$ k Ω .

(c) Repeat part (b) with $R_E = 80$ k Ω .

(d) If the goal is to maximize the voltage gain, what general design rule for common-emitter amplifiers can you infer from the results of parts (b) and (c)?

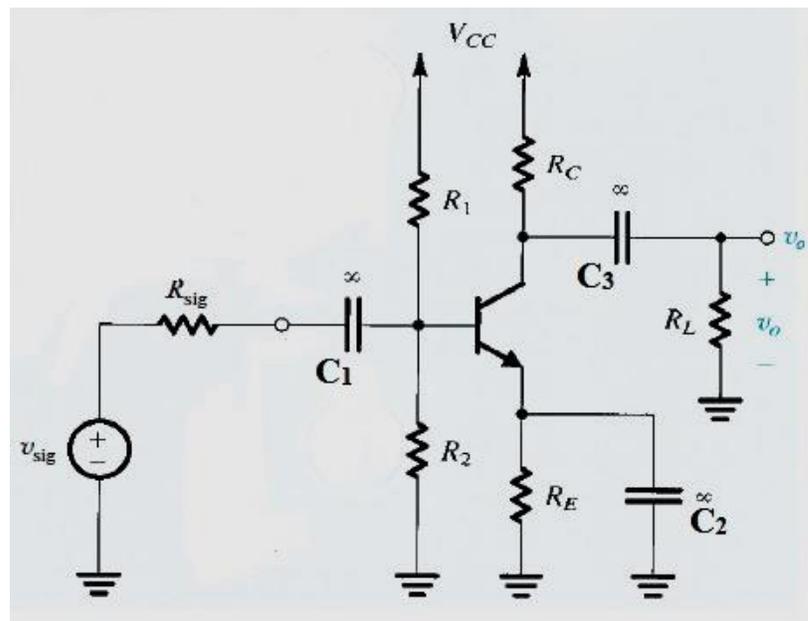


Figure 1. BJT amplifier circuit.

2. Purpose: Coupling diodes and BJTs

In the circuit below, find the Q-point of both the Zener diode and BJT. Assume the BJT is biased in the forward-active regime, that $V_Z = 5V$, $R_Z = 0 \Omega$, $\beta = 100$ and $V_{BE} = 0.7V$.

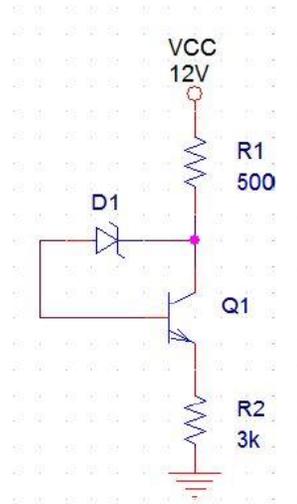


Figure 2. Zener diode with BJT.

3. Purpose: BJT application in circuit designing

Assume forward active mode bias and identical BJTs Q_1 and Q_2 in the following “current mirror” circuit.

Given, $R_2 = 10k\Omega$, $R_3 = 1k\Omega$, $R_7 = 100\Omega$, $R_8 = 100\Omega$, $\beta = 416.4$, and $I_S = 6.73 \text{ fA}$.

(a) Find the current flowing in R_3 and compare it to the current flowing in R_2 .

Note: it may be helpful to use Ebers Moll model only for determining collector currents in the two transistors, but otherwise use Beta/CVD model.

(b) What happens to the currents if R_3 is replaced with a $5k\Omega$ resistor?

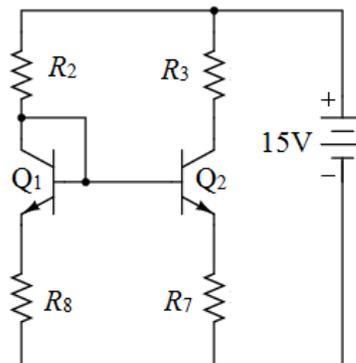


Figure 3. Current mirror circuit.