

Note: The following solutions are given:

- 1) Old Jaeger 14.20 or New Jaeger 14.25
- 2) Old Jaeger 14.21 or New Jaeger 14.27
- 3) Old Jaeger 14.22 or New Jaeger 14.26
- 4) Old Jaeger 14.23 or New Jaeger 14.28



Defining v_1 as the source node:


$$(a) 2k\Omega \parallel 100k\Omega = 1.96k\Omega$$

$$\frac{(v_s - v_1)}{10^6} + 3.54 \times 10^{-3}(v_s - v_1) = \frac{v_1}{1960}$$

$$3.541 \times 10^{-3}v_s = 4.051 \times 10^{-3}v_1$$

$$v_1 = 0.874v_s \quad | \quad A_v = 0.874$$
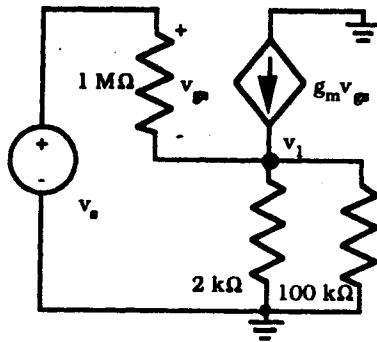
$$R_{IN} = \frac{v_s}{i_s} = \frac{v_s}{10^{-6}(v_s - v_1)} = 7.94 \text{ M}\Omega$$



Driving the output with current source i_x :

$$R_{OUT}: i_x = \frac{v_1}{10^6} + \frac{v_1}{2000} + 3.54 \times 10^{-3}v_1$$

$$R_{OUT} = \frac{v_1}{i_x} = 247 \Omega \quad | \quad (b) R_{IN} = \infty$$

14.21

$$V_{EQ} = 18 \frac{51k\Omega}{51k\Omega + 100k\Omega} = 6.08V \quad | \quad R_{EQ} = 51k\Omega \parallel 100k\Omega = 33.8k\Omega$$

$$I_B = \frac{(6.08 - 0.7 + 18)V}{33.8k\Omega + (126)(4.7k\Omega)} = 37.3\mu A \quad | \quad I_C = 4.67 \text{ mA} \quad | \quad V_{CE} = 36 - 2000I_C - 4700I_E = 4.54 \text{ V}$$

$$\text{Forward-active region is correct.} \quad | \quad r_\pi = \frac{125(0.025V)}{4.67 \text{ mA}} = 669\Omega \quad | \quad r_o = \frac{(50 + 4.54)V}{4.67 \text{ mA}} = 11.7k\Omega$$

$$v_{th} = v_s \frac{33.8\Omega}{500\Omega + 33.8k\Omega} = 0.985v_s \quad | \quad R_{th} = 33.8k\Omega \parallel 500\Omega = 493\Omega$$

$$R_L = 24k\Omega \parallel 4.7k\Omega \parallel 1.7k\Omega = 2.94k\Omega \quad | \quad A_{Vth} = - \frac{126(2.94k\Omega)}{0.493k\Omega + 0.669k\Omega + 126(2.94k\Omega)} = 0.997$$

$$A_v = 0.985A_{Vth} = 0.982 \quad | \quad R_{IN} = 33.8k\Omega \parallel [0.669k\Omega + 126(2.94k\Omega)] = 31.0 \text{ k}\Omega$$

$$A_I = A_v \frac{R_S + R_{IN}}{R_3} = 0.982 \frac{0.5k\Omega + 31.0k\Omega}{24.0k\Omega} = 1.29 \quad | \quad R_{OUT} = \frac{493\Omega + 669\Omega}{126} [2.94k\Omega] = 9.19 \text{ }\Omega$$

$$v_{be} = 0.982v_s \frac{0.669k\Omega}{0.493k\Omega + 0.669k\Omega + 126(2.94k\Omega)} = 0.00177v_s \quad | \quad v_s = \frac{5.00 \text{ mV}}{0.00177} = 2.83 \text{ V}$$

14.22

$$I_B = \frac{(5 - 0.7)V}{1M\Omega + (100 + 1)430k\Omega} = 96.8 \text{ nA} \quad | \quad I_C = 9.68 \mu A \quad | \quad V_{CE} = 10 - 430000I_E = 5.80 \text{ V} \quad | \quad \text{Forward-active region is correct. } r_\pi = \frac{100(0.025V)}{9.68 \mu A} = 258k\Omega \quad | \quad r_o = \frac{(60 + 5.80)V}{9.68 \mu A} = 6.80M\Omega - \text{neglected}$$

In the ac model, R_L appears in parallel with r_π . The circuit appears to have a transistor with $r_\pi = 500k\Omega$, $r_\pi = 170k\Omega$ and $\beta_o = g_m r_\pi = 40(9.68 \mu A)170k\Omega = 65.8$

$$v_{th} = v_s \quad | \quad R_{th} = 500\Omega \quad | \quad R_L = 500k\Omega \parallel 430k\Omega \parallel 500k\Omega = 158k\Omega$$

$$A_v = - \frac{66.8(158k\Omega)}{0.500k\Omega + 170k\Omega + 66.8(158k\Omega)} = 0.984 \quad | \quad R_{IN} = 170k\Omega + 66.8(158k\Omega) = 10.7 \text{ M}\Omega$$

$$A_1 = A_V \frac{R_S + R_{IN}}{R_3} = 0.984 \frac{500\Omega + 10.7M\Omega}{500k\Omega} = 21.1$$

$$R_{OUT} = \frac{500\Omega + 170k\Omega}{66.8} \| 500k\Omega \| 430k\Omega = 2.53 k\Omega$$

$$v_{be} = v_s \frac{170k\Omega}{0.500k\Omega + 170k\Omega + 66.8(158k\Omega)} = 0.0159v_s \quad | \quad v_s \leq \frac{5.00mV}{0.0159} = 0.315 V$$

14.23

$$V_{GS} = 5V \quad | \quad I_{DS} = \frac{4 \times 10^{-4}}{2} (5 - 1)^2 = 3.2mA \quad | \quad V_{DS} = 5 - (-5) = 10V \quad - \text{Saturation region}$$

operation is correct. | $g_m = \sqrt{2(4 \times 10^{-4})(3.2mA)[1 + 0.02(10)]} = 1.75mS$

$$r_o = \frac{\frac{1}{0.02} + 10}{3.2mA} = 18.8k\Omega \quad - \text{Cannot neglect!} \quad | \quad R_L = 18.8k\Omega \| 100k\Omega = 15.8k\Omega$$

$$A_V = \frac{10^6}{10^6 + 10^4} \frac{1.75mS(15.8k\Omega)}{1 + 1.75mS(15.8k\Omega)} = 0.956 \quad | \quad A_I = 10^6 \frac{1.75mS(15.8k\Omega)}{1 + 1.75mS(15.8k\Omega)} \frac{1}{10^5} = 9.56$$

$$R_{IN} = R_G = 1M\Omega \quad | \quad R_{OUT} = \frac{1}{g_m} \| r_o = 555 \Omega$$

$$v_{gs} = v_s \frac{10^6}{10^6 + 10^4} \frac{1}{1 + 1.75mS(15.8k\Omega)} = 0.0346v_s \quad | \quad v_s \leq \frac{0.2(5 - 1)}{0.0346} = 23.2 V \quad \text{But,}$$

v_{DS} must exceed $v_{GS} - V_{TN} \equiv V_{GS} - V_{TN} = 4V$ for saturation.

$V_{DS} = 10 - v_o = 10 - 0.956v_s \geq 4 \rightarrow v_s \leq 6.28 V \quad - \text{Limited by the Q-point voltages}$

14.24

$$\beta_o = g_m r_\pi = 3.54mS(1M\Omega) = 3540 \quad | \quad R_L = 2k\Omega \| 100k\Omega = 1.96k\Omega$$

$$A_V = \frac{(\beta_o + 1)R_L}{r_\pi + (\beta_o + 1)R_L} = \frac{(3540 + 1)(1.96k\Omega)}{1M\Omega + (3540 + 1)(1.96k\Omega)} = 0.874$$

$$R_{IN} = r_\pi + (\beta_o + 1)R_L = 1M\Omega + (3540 + 1)(1.96k\Omega) = 7.94 M\Omega$$

$$R_{OUT} = \frac{r_\pi}{(\beta_o + 1)} \| 2k\Omega = \frac{10^6}{(3541)} \| 2k\Omega = 247 \Omega$$

14.25


$$v_o \leq 0.005(1 + g_m R_L) \quad | \quad R_L = R_4 \| R_7 \equiv R_4$$

$$v_o \leq 0.005(1 + g_m R_L) = 0.005(1 + g_m R_4) = 0.005 \left(1 + \frac{I_C R_4}{V_T} \right)$$

$$v_o \leq 0.005 \left(1 + \alpha_F \frac{I_E R_4}{V_T} \right) \equiv 0.005 \left(1 + \frac{I_E R_4}{V_T} \right)$$

$$v_o \leq 0.005 \left(1 + \frac{V_{R_4}}{V_T} \right) = 0.005 \left(1 + \frac{V_{R_4}}{0.025} \right) = 0.005 + \frac{V_{R_4}}{5}$$

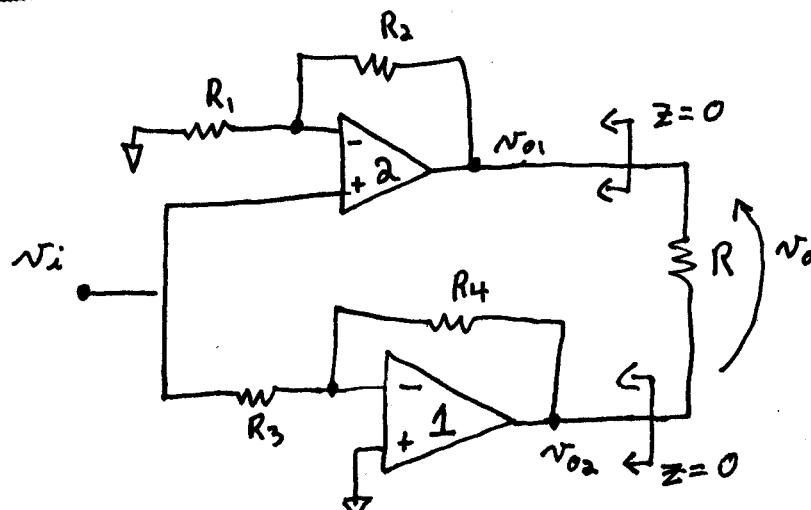Bridge Amplifier: Determine the gain of the following.



Zero output impedance allows us to decouple the stages 1+2


By superposition: $v_{o2} = - \frac{R_4}{R_3} v_i$

$$v_{o1} = \left(1 + \frac{R_2}{R_1}\right) v_i$$

$$v_o = v_{o1} - v_{o2} = v_i \left(1 + \frac{R_2}{R_1} + \frac{R_4}{R_3}\right)$$

$$\frac{v_o}{v_i} = 1 + \frac{R_2}{R_1} + \frac{R_4}{R_3}$$

Mixing signals of different magnitude

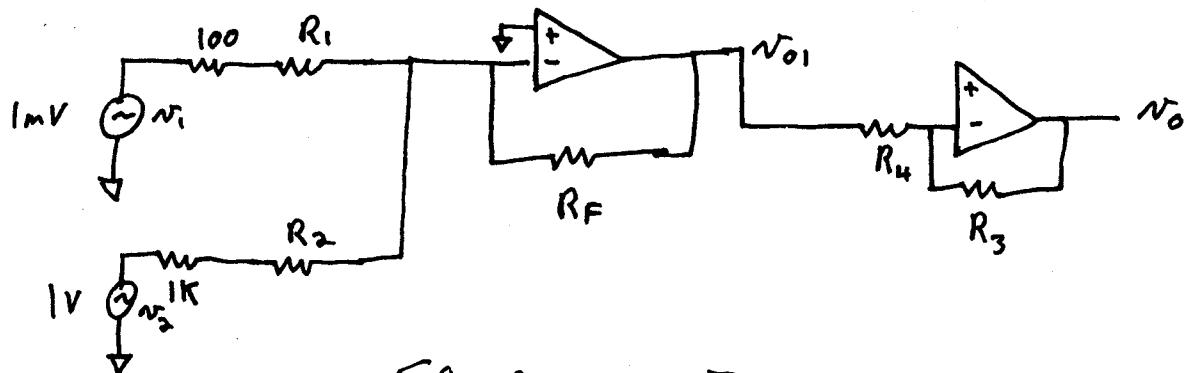

Determine $\begin{bmatrix} R_3, R_4 \\ R_F, R_1 + R_2 \end{bmatrix}$ so that

$$N_0 = 10,000N_1 + 10N_2$$

Let $R_4 = R_3$, then $\frac{N_0}{N_{01}} = -1$ so,

$$N_0 = \frac{R_F}{R_1 + 100} N_1 + \frac{R_F}{1K + R_2} N_2$$

$$\frac{R_F}{R_1 + 100} = 10,000 \quad \frac{R_F}{1K + R_2} = 10$$

$$R_F = 10,000R_1 + 1e6 \iff R_F = 10K + 10R_2$$

$$R_1 = \frac{10K + 10R_2 - 1e6}{10,000}$$

choose $R_2 = 999K \Rightarrow R_F = 10M\Omega \text{ } \Omega$

$$+ R_1 = 900 \Omega$$