

Lecture 15



P-N Junction Diodes: Part 5

**Large signal (complete model) and small signal
(limited use) models of a Diode**



Reading:

Jaeger 3.4-3.14, 13.4, Notes



Diode Applications: 1/2 Wave Rectifier

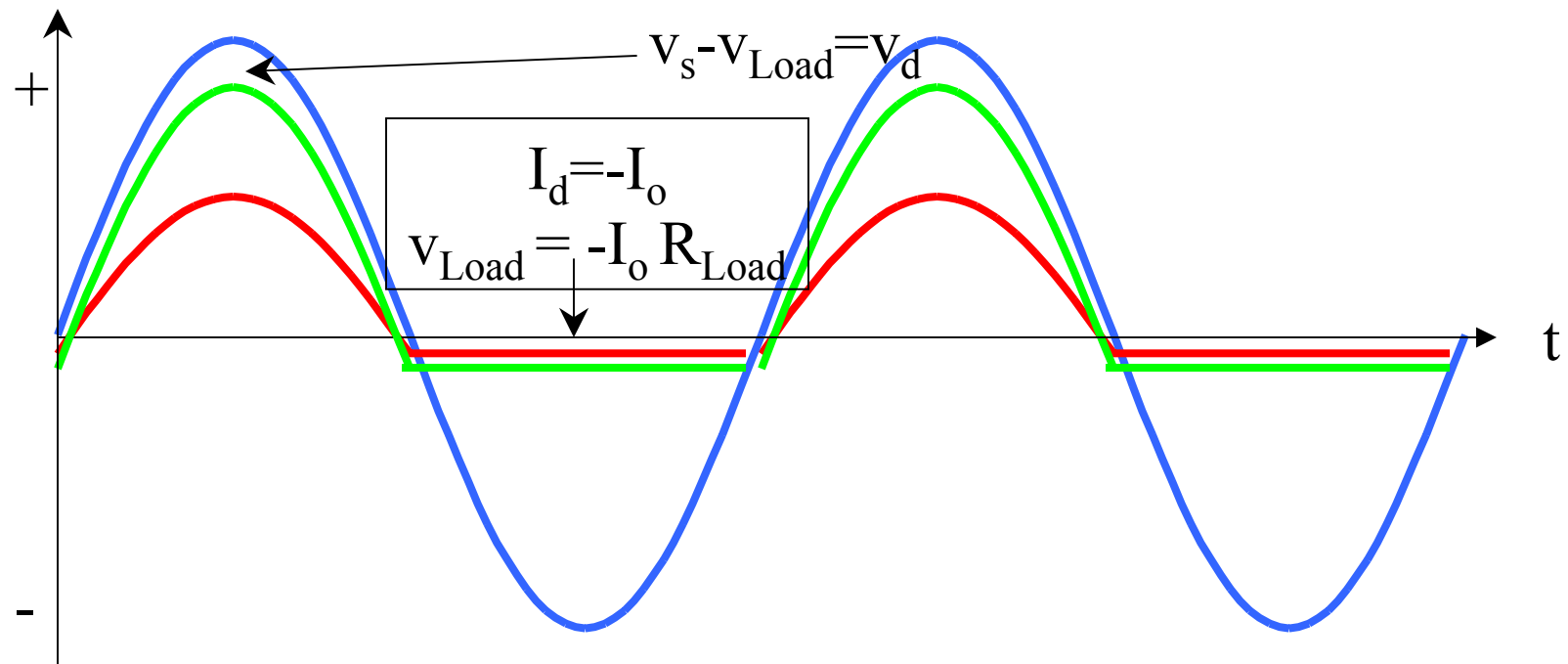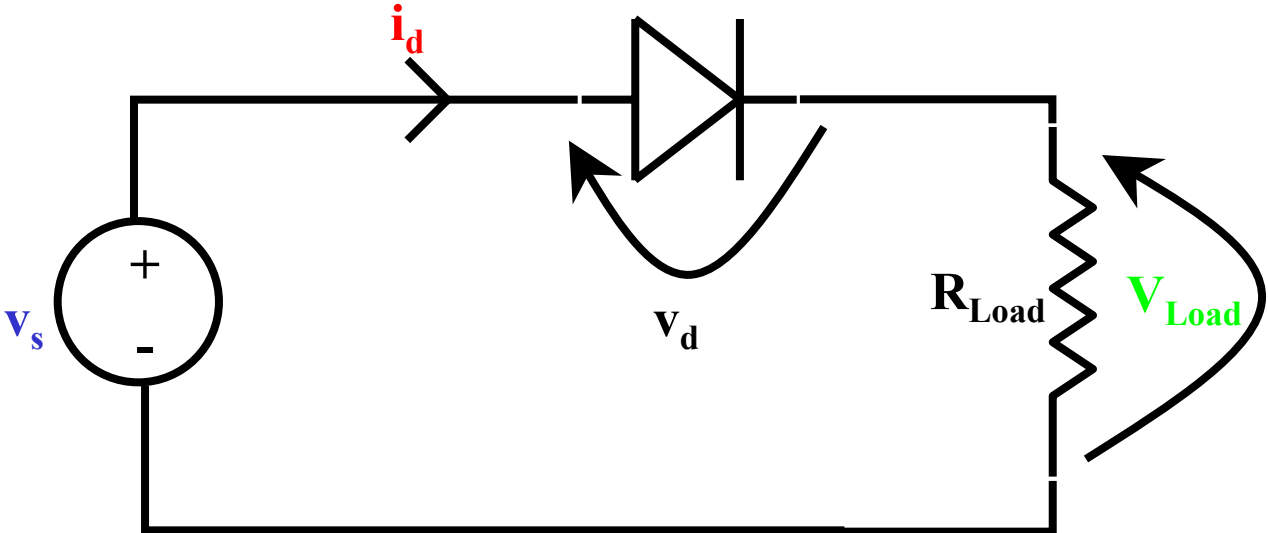


Diode Applications: Peak Detector

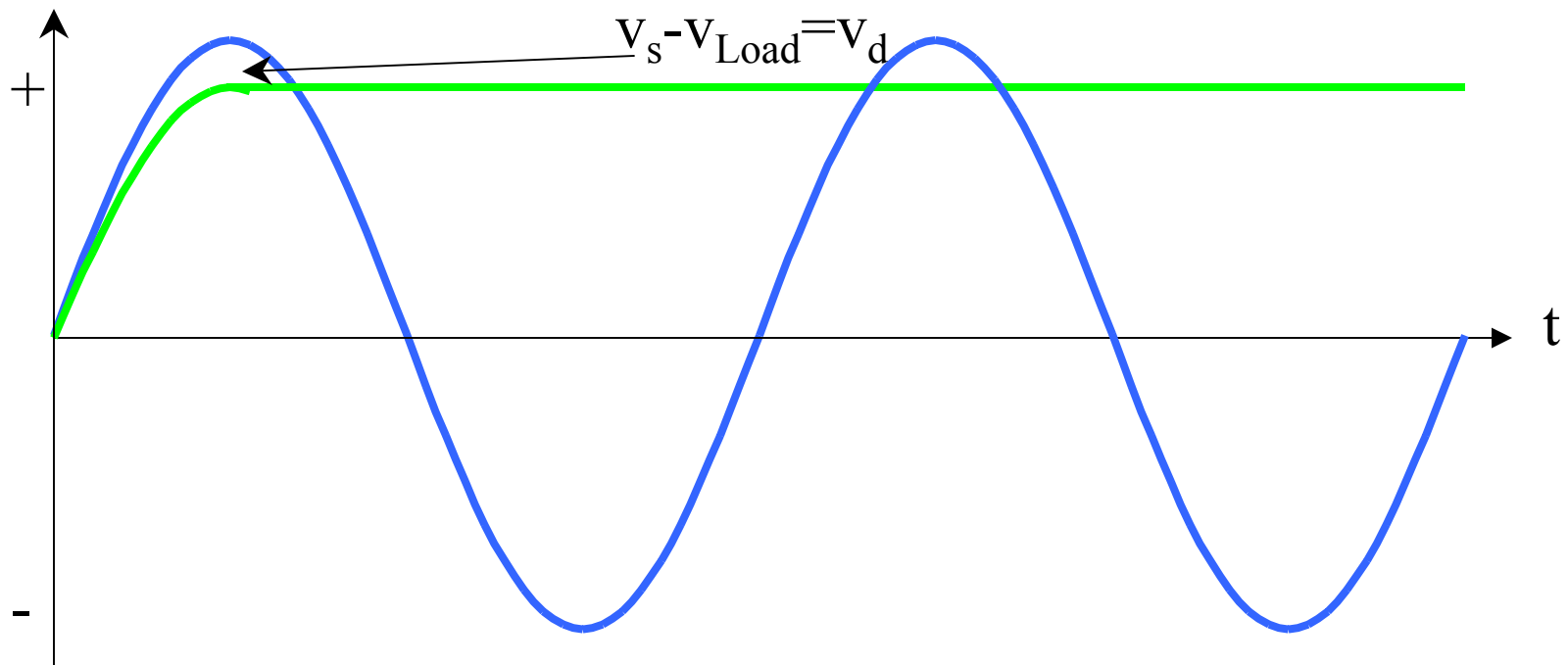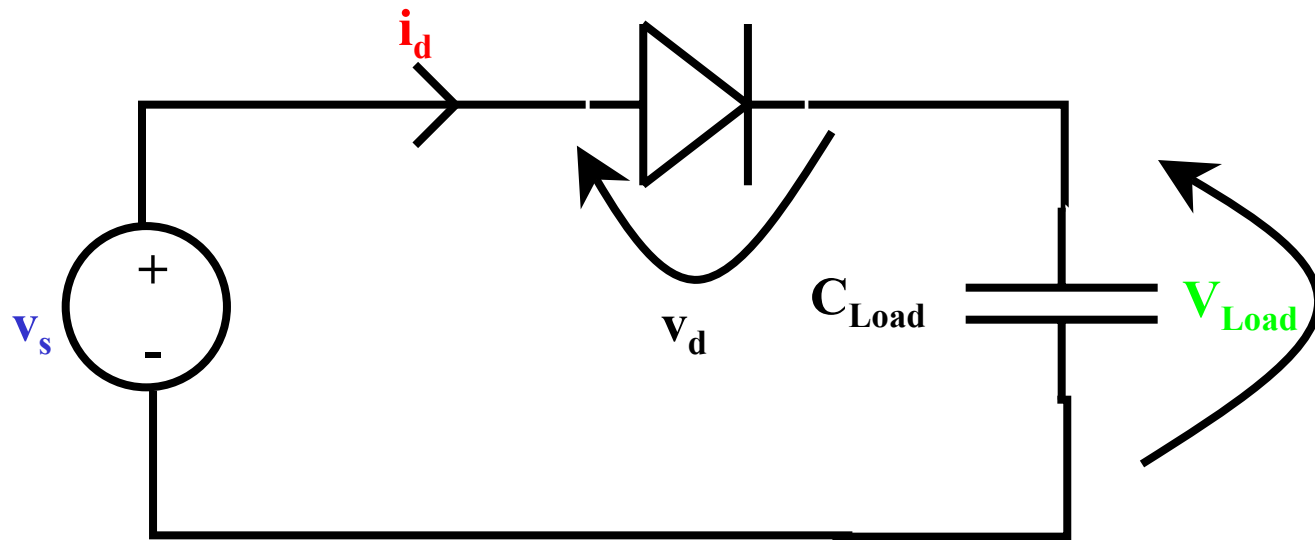

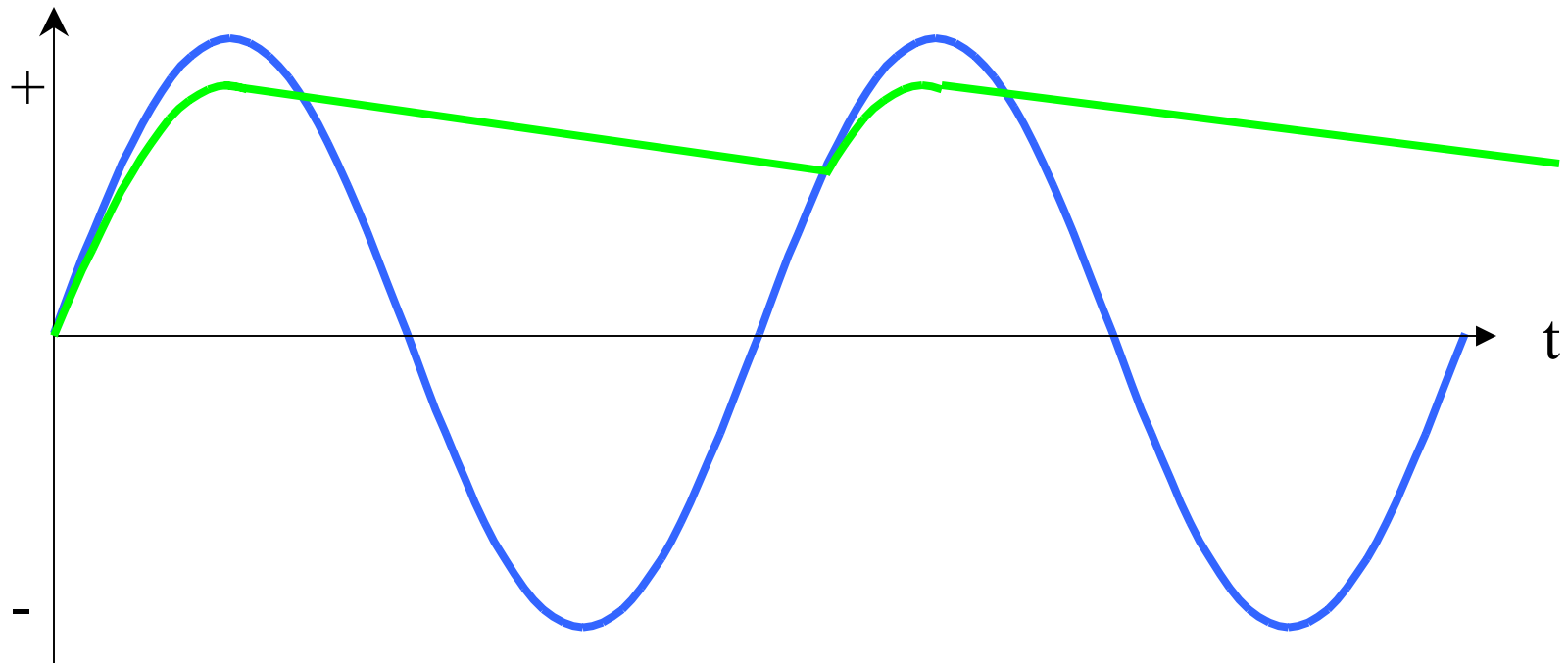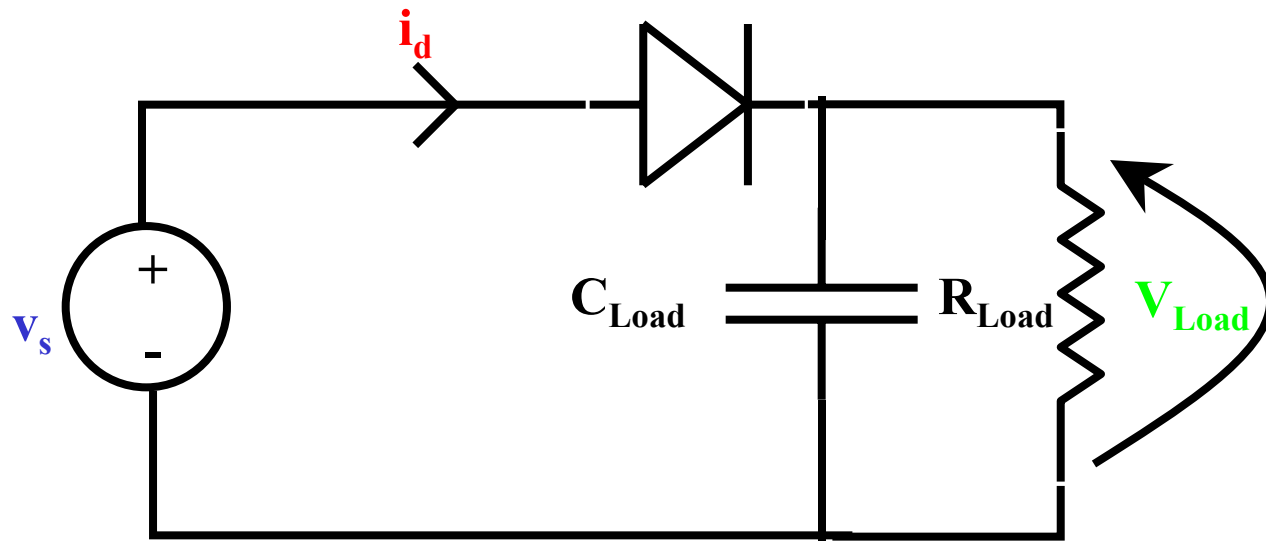Diode Applications: 1/2 Wave Rectifier with an RC Load




Diode Applications: LED or a Laser Diode

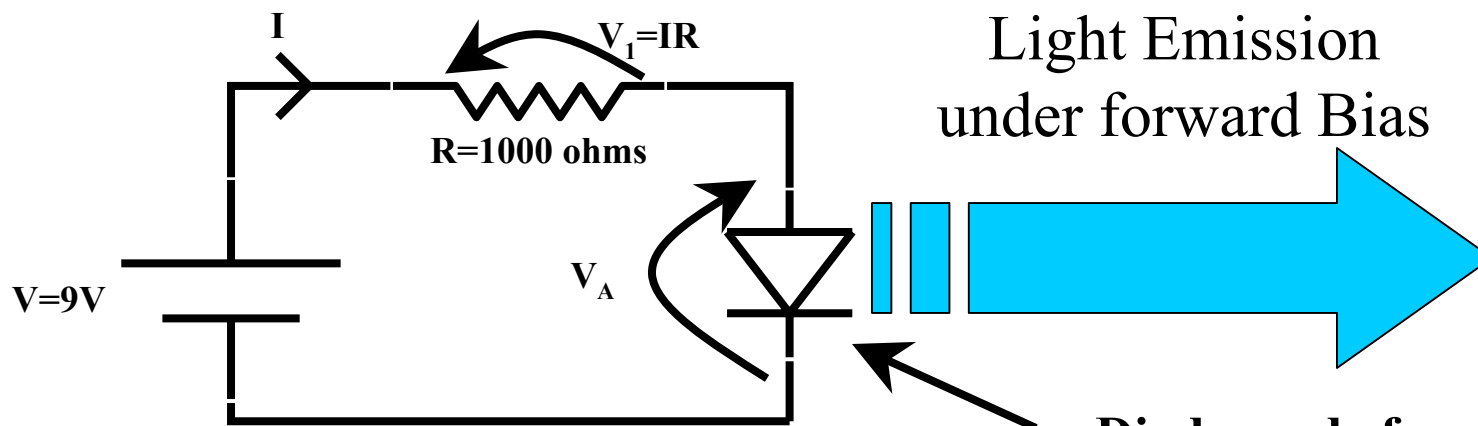

Diode made from a direct bandgap semiconductor.
Note: These devices may not be a simple p-n type diode, but behave electrically identical to a p-n junction diode.

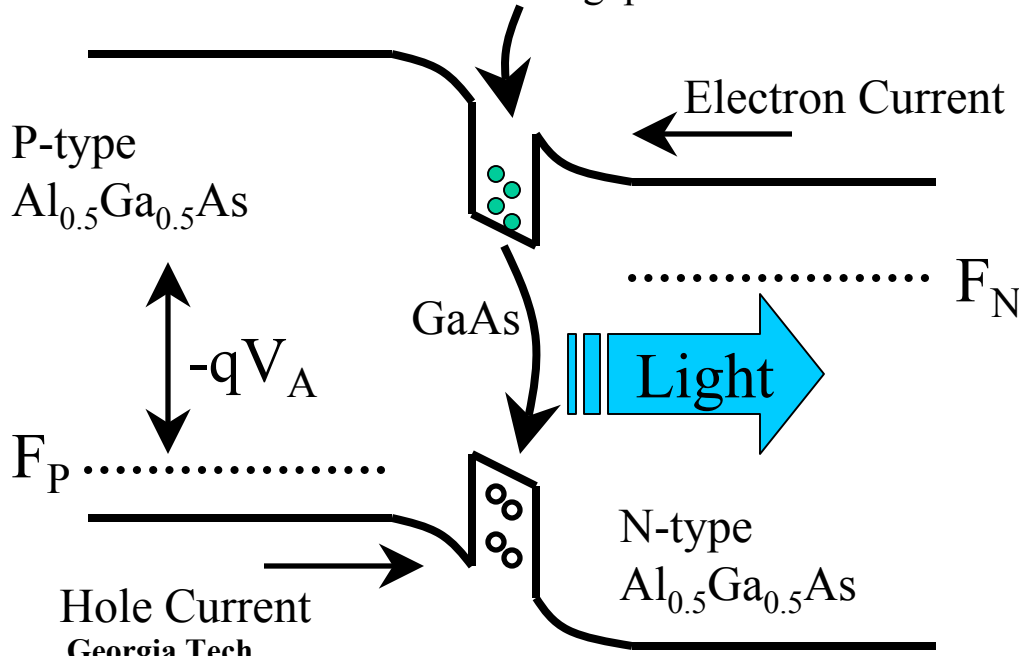Quantum well made from smaller bandgap material



Majority Carriers that are injected to the opposite side of the diode under forward bias become minority carriers and recombine. In a direct bandgap material, this recombination can result in the creation of photons. In a real device, special areas are used to trap electrons and holes to increase the rate at which they recombine. These areas are called quantum wells.

Models used for analysis of Diode Circuits

Mathematical Model (previously developed)

Graphical Analysis

Ideal diode Model

- Treat the diode as an ideal switch

Constant Voltage Drop Model

- Treat as an ideal switch plus a battery


Large signal Model (model used by SPICE transient analysis)

- multi-components
- generally applicable

Small Signal Model (model used by SPICE AC analysis)

- easier math
- valid only for limited conditions-ie small signals

Diode Circuits: Graphical Solution

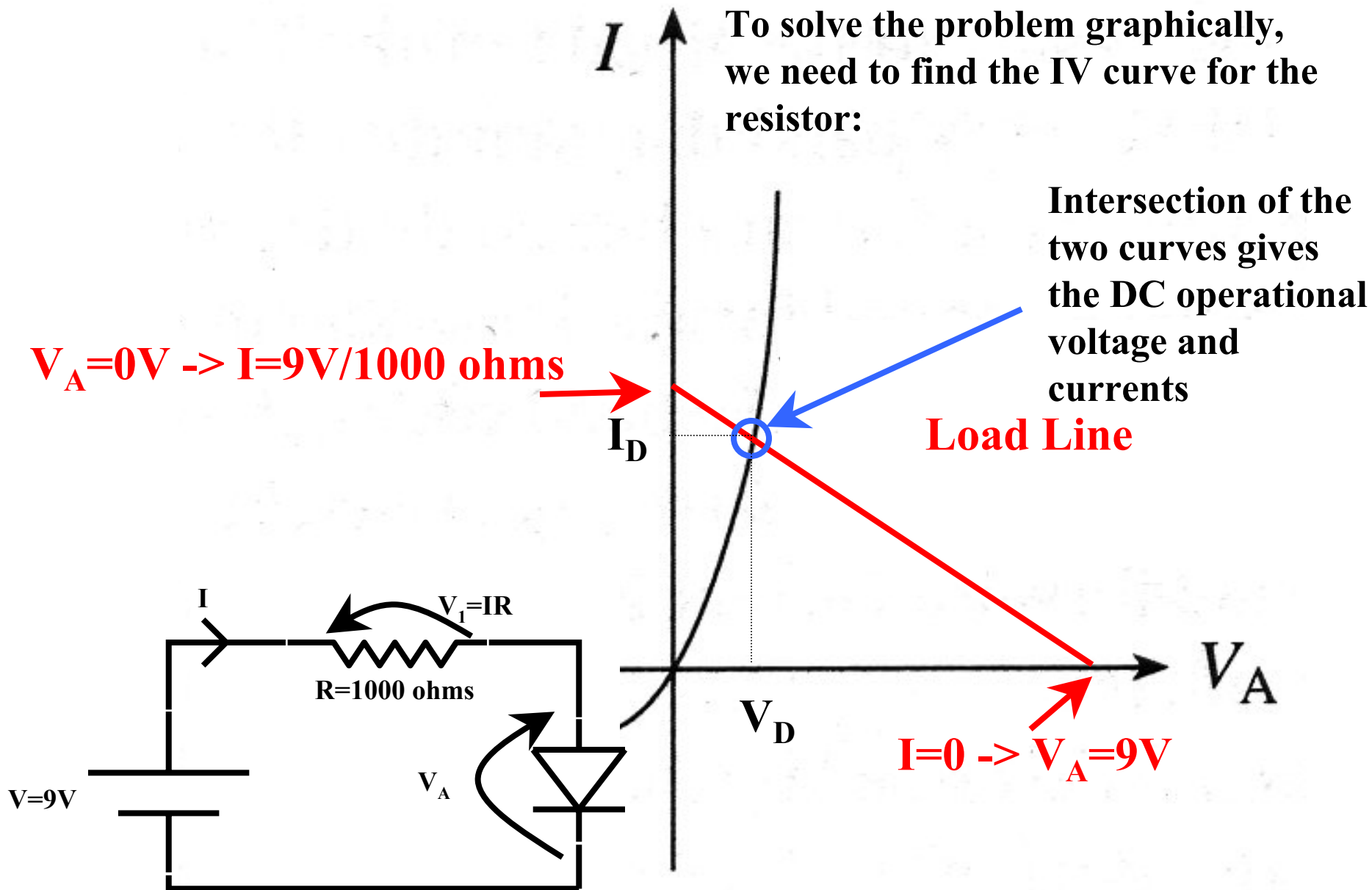


Diode Circuits: Other Models

Besides the direct mathematical solution and the graphical solution, we can use 2 other models to approximate circuit solutions:

1.) Ideal Diode Model:

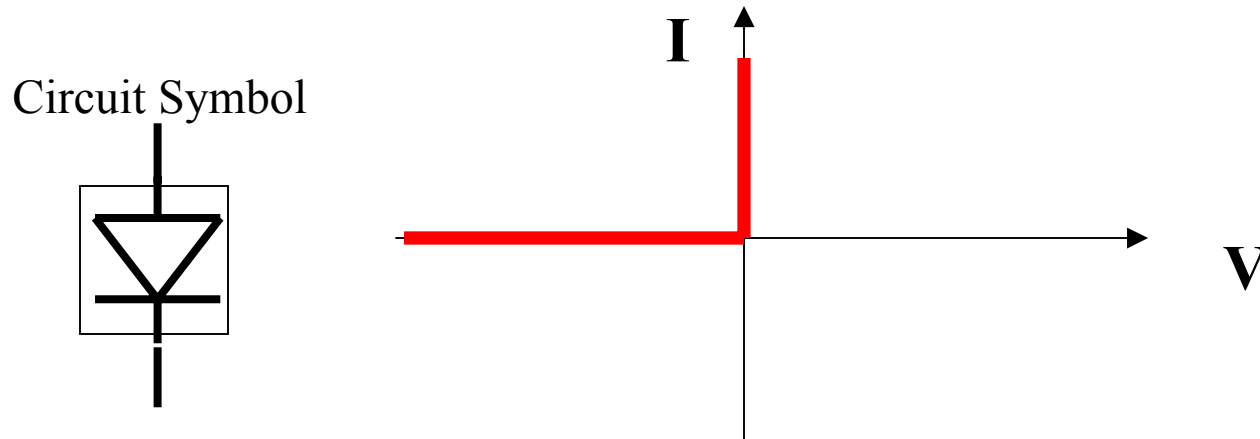
- a) The voltage across the diode is zero for forward bias.
- b) The slope of the current voltage curve is infinite for forward bias.
- c) The current across the diode is zero for reverse bias.



Diode Circuits: Other Models

2.) Constant Voltage Drop (CVD) Model:

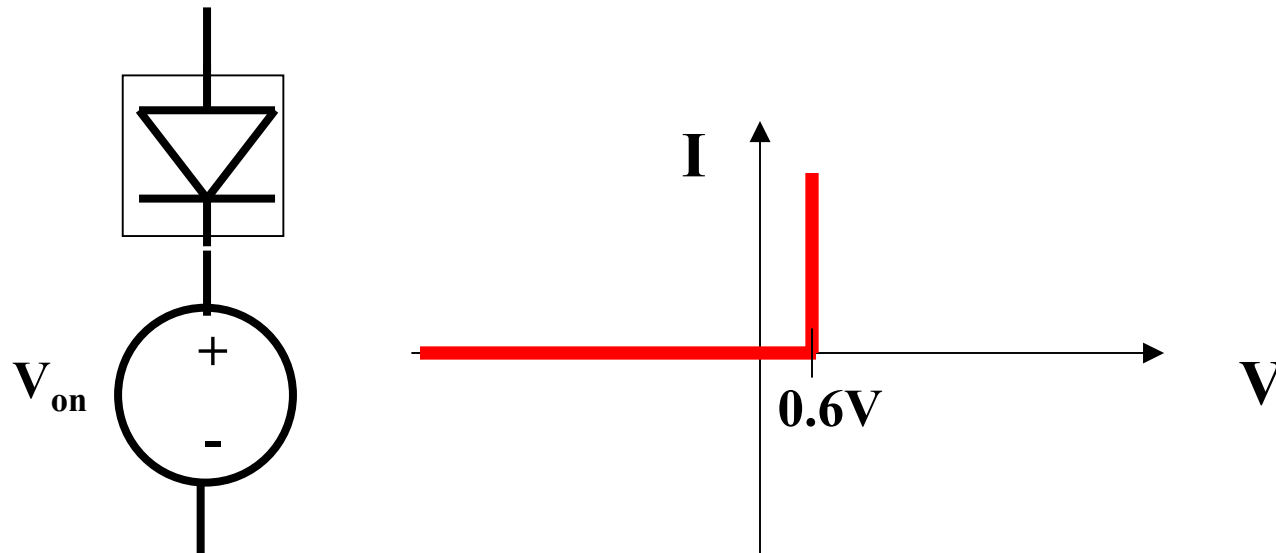- a) The voltage across the diode is a non-zero value for forward bias. Normally this is taken as 0.6 or 0.7 volts.
- b) The slope of the current voltage curve is infinite for forward bias.
- c) The current across the diode is zero for reverse bias.



Concept of the Small- Signal Model

- Superposition principle allows us to separate DC and AC analysis of circuits containing active devices (like diodes, transistors, amplifiers etc...).
- We assume the AC signals are small enough so that the circuit behaves linearly and can be analyzed by replacing “non-linear” components by “Linear Elements” such as resistors etc...
- DC analysis is first performed to determine the bias point which will determine some of the parameters used in the “AC-small signal analysis”.
- Consider a two terminal device (like a pn diode) at a given DC *operating point* (or “Q- point”).

Let: V_D = DC voltage applied to the diode

I_D = DC current produced by the diode


Total current or voltage = DC part + AC part:

$$V_D = V_D + v_d \qquad i_D = I_D + i_d$$

Note: (1) all caps = DC; (2) all lower case = AC; (3) lower case symbol with upper case subscript = total voltage or current

Small Signal Analysis of Diodes

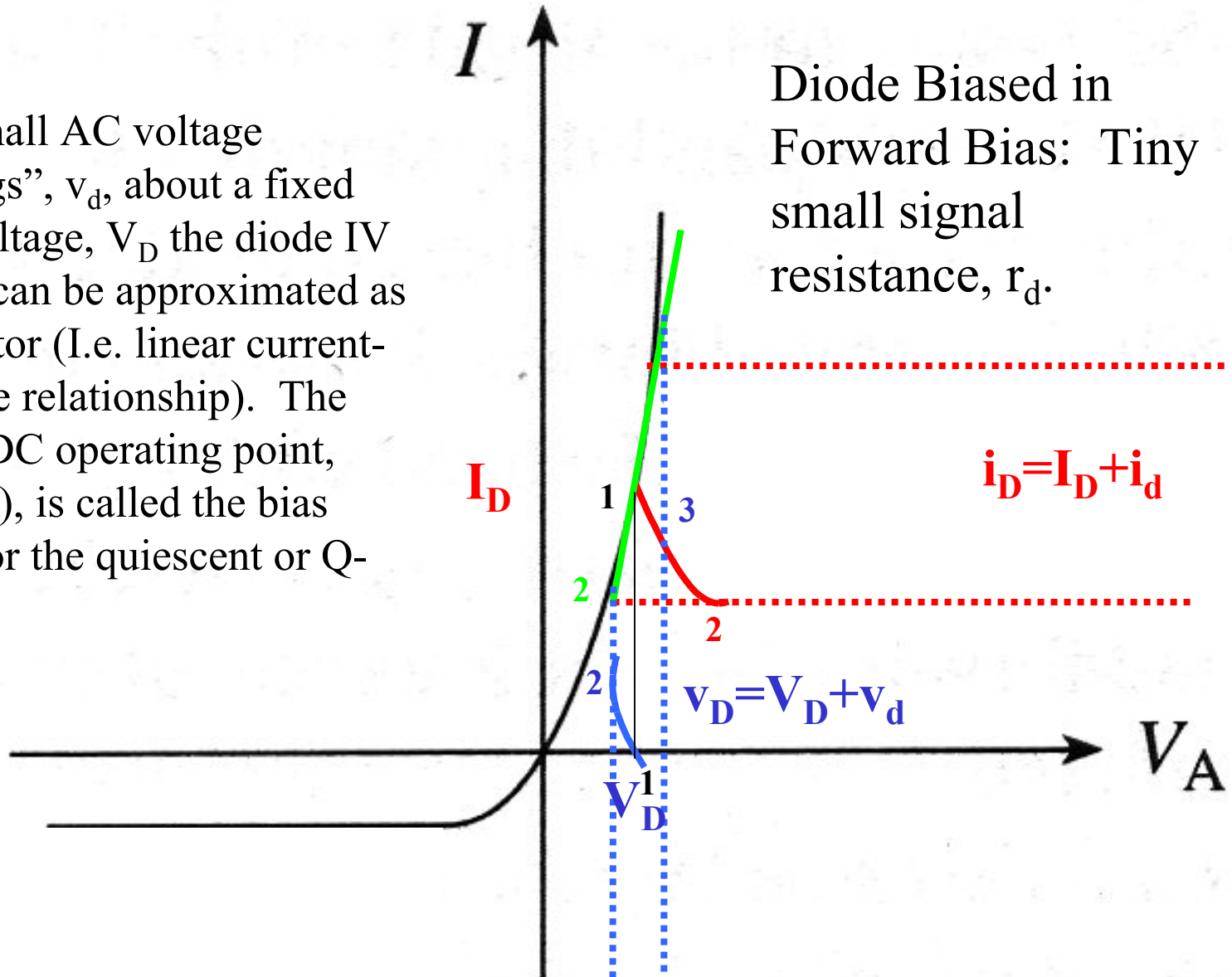
For small AC voltage “swings”, v_d , about a fixed DC voltage, V_D the diode IV curve can be approximated as a resistor (I.e. linear current-voltage relationship). The fixed DC operating point, (V_D, I_D) , is called the bias point or the quiescent or Q-point.



Diode Biased in Forward Bias: Tiny small signal resistance, r_d .


Small Signal Analysis of Diodes

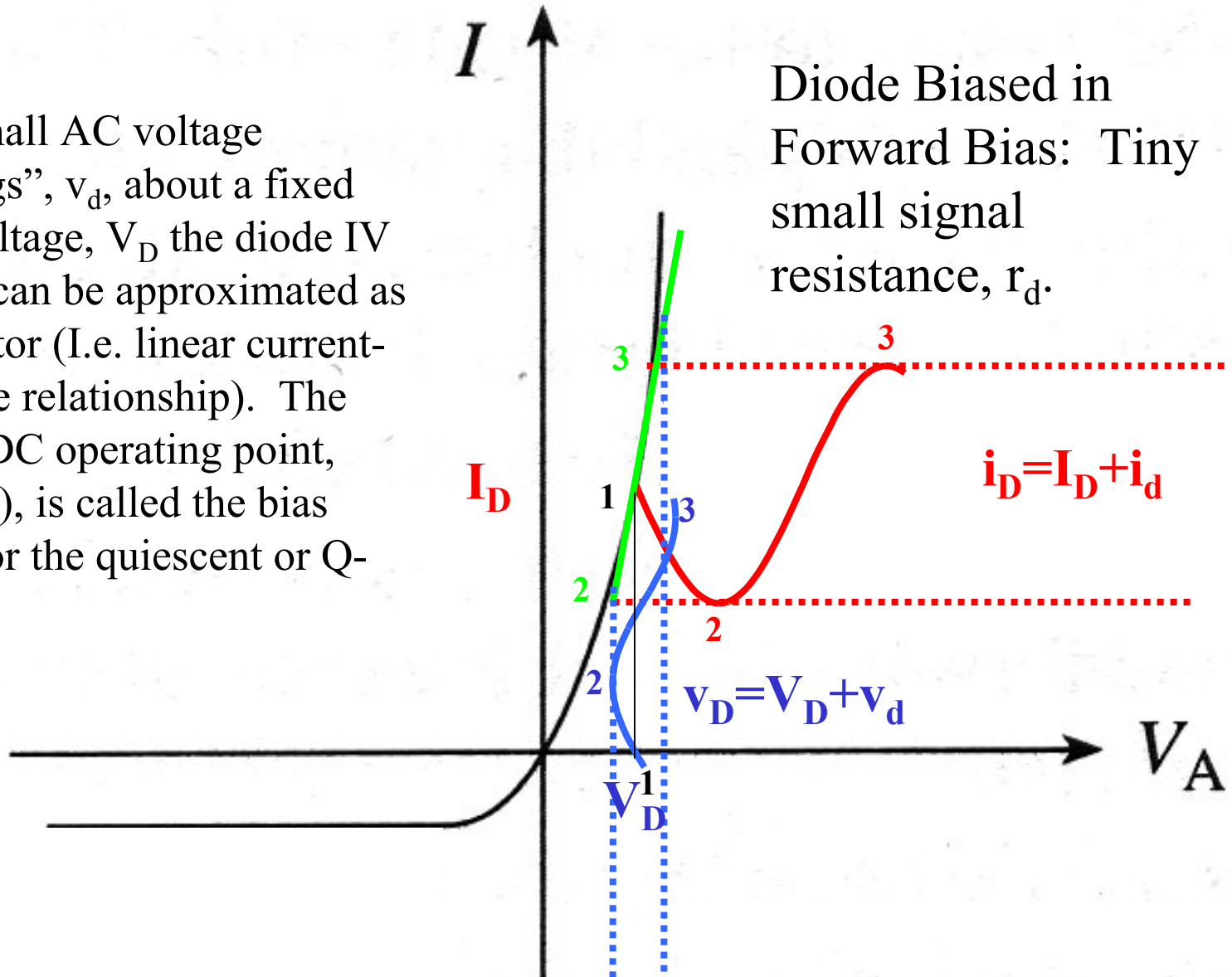For small AC voltage “swings”, v_d , about a fixed DC voltage, V_D the diode IV curve can be approximated as a resistor (I.e. linear current-voltage relationship). The fixed DC operating point, $(V_D - I_D)$, is called the bias point or the quiescent or Q-point.



Small Signal Analysis of Diodes

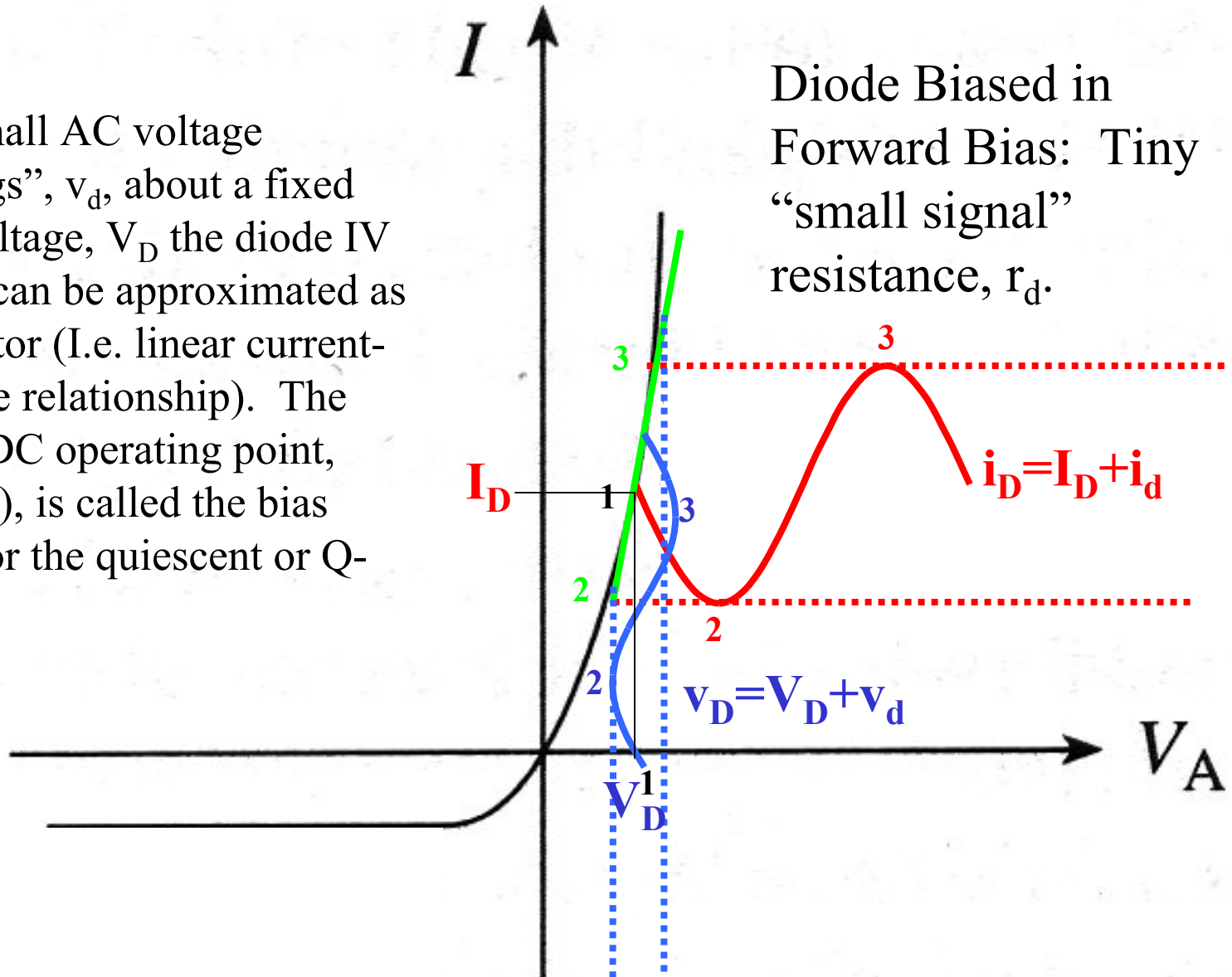For small AC voltage “swings”, v_d , about a fixed DC voltage, V_D the diode IV curve can be approximated as a resistor (I.e. linear current-voltage relationship). The fixed DC operating point, (V_D, I_D) , is called the bias point or the quiescent or Q-point.



Diode Biased in Forward Bias: Tiny “small signal” resistance, r_d .


Small vs Large Signal Concept For Diodes

Consider the small signal case where

$$v_D(t) = 0.6 + 0.025\sin(\omega t) \text{ then,}$$


$$i_D(t) = 1e-12(e^{v_D(t)/0.0259} - 1)$$
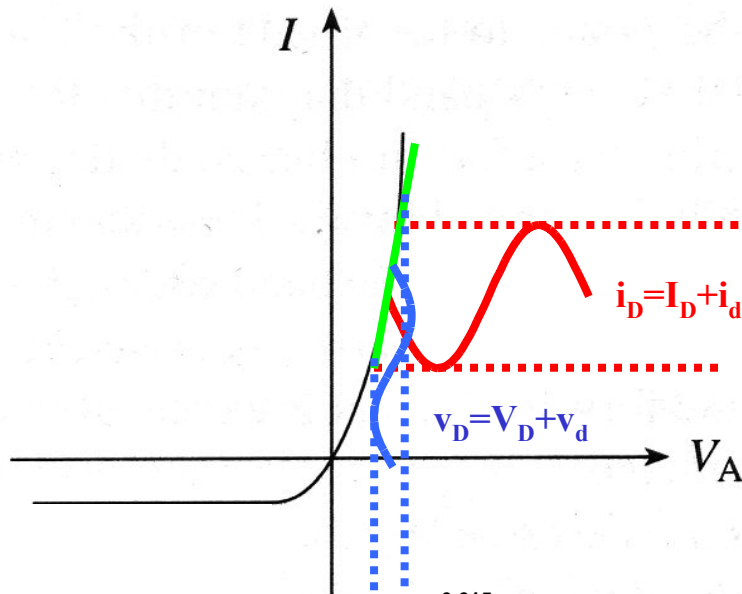
$$\Rightarrow i_d(t) \approx \frac{1}{r_d} v_d(t) \quad \text{but} \quad i_D(t) \neq \frac{1}{r_d} v_D(t)$$




Both Voltage and Current are (approximately) a sine wave.

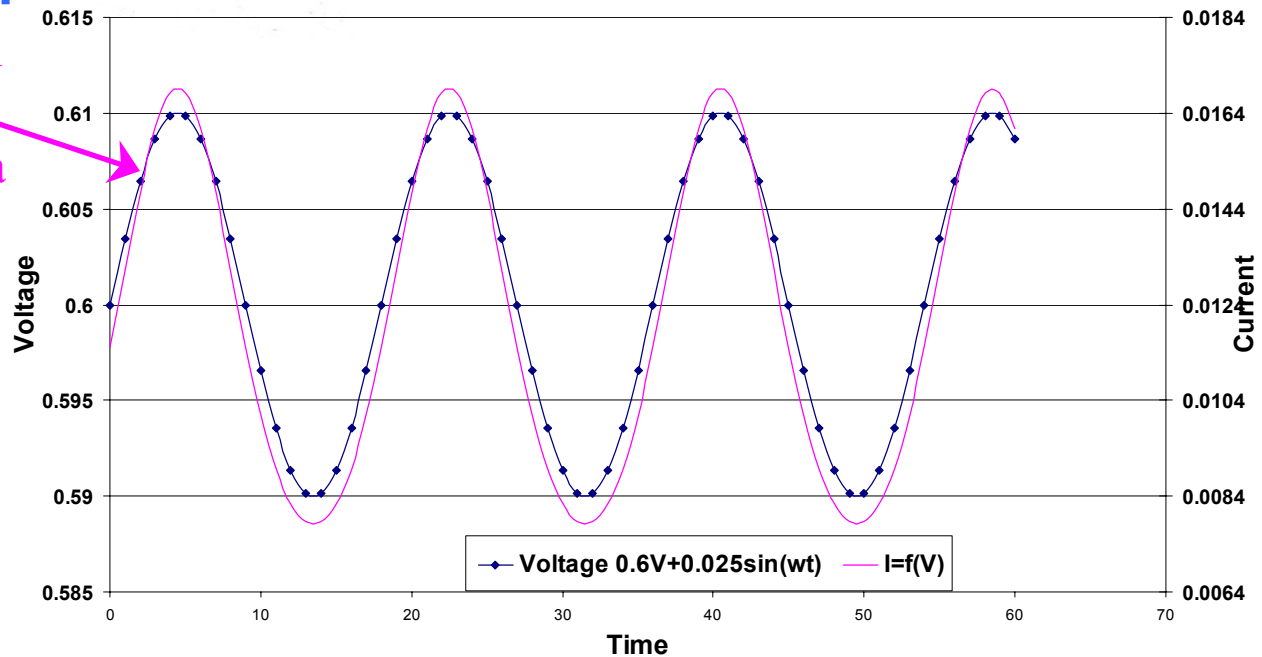Some distortion is observed because in this example we have exceeded the mathematical limits valid for small signal analysis (0.025 is not $\ll kT/q$). In most cases, this is tolerable.



Small vs Large Signal Concept For Diodes

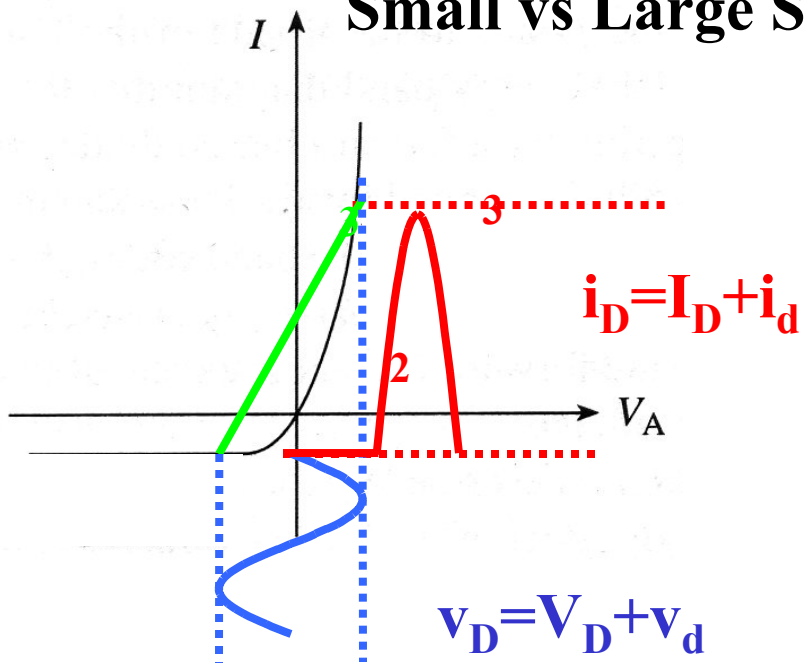


Consider the Large Signal case where

$$v_D(t) = 0.6\sin(\omega t) \text{ then,}$$







$$i_D(t) = 1e-12(e^{v_D(t)/0.0259} - 1)$$

$$\Rightarrow i_D(t) \neq \frac{1}{r_d} v_D(t)$$

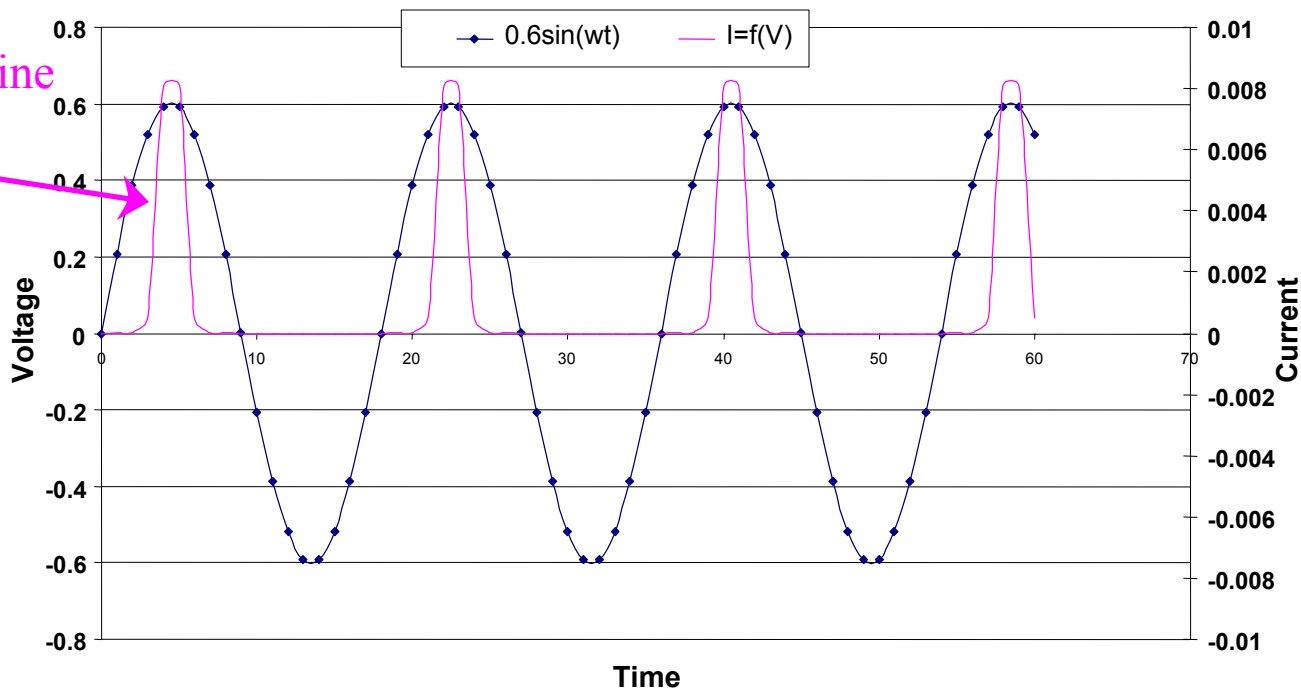Voltage is a sine wave but the current is "distorted"



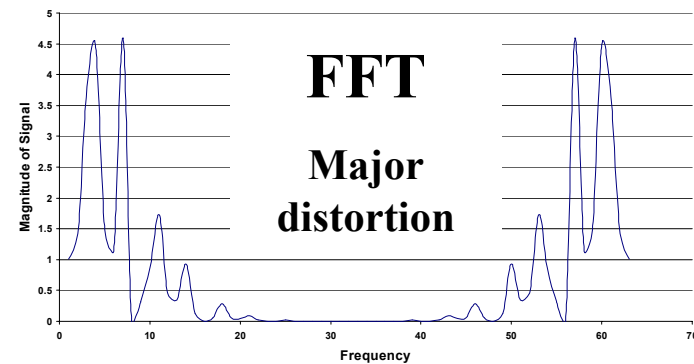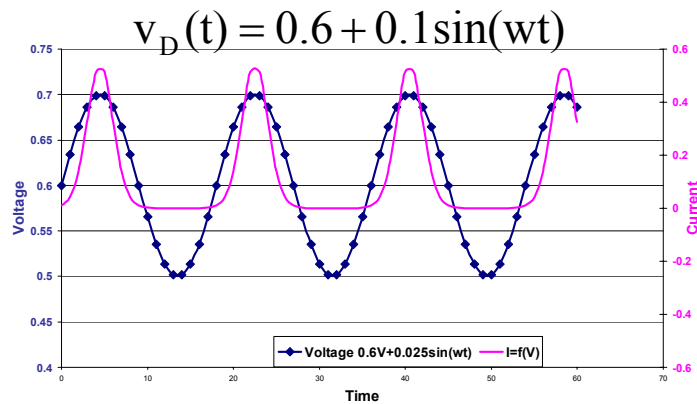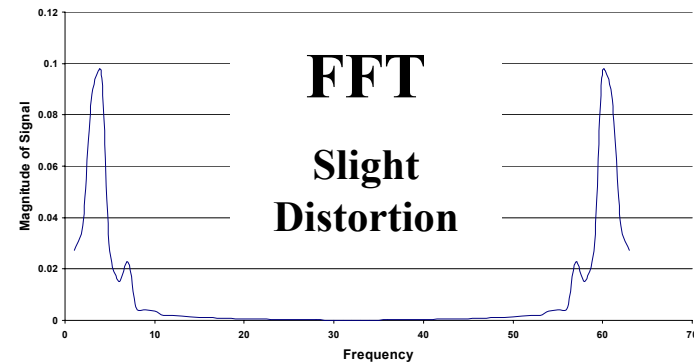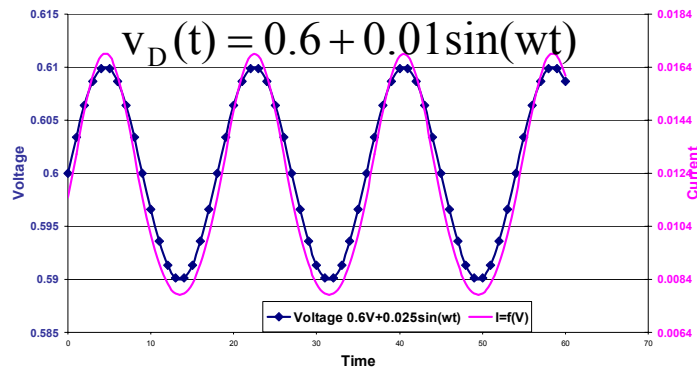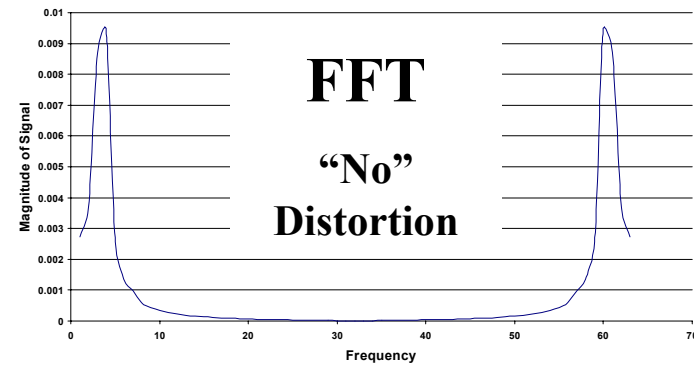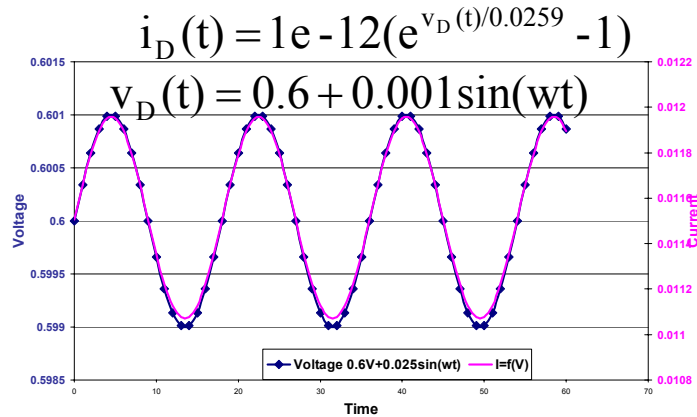The transition from valid small signal limits to Large Signal conditions is a matter of what is acceptable for your requirements



Small Signal Analysis of Diodes

$g_d \equiv$ small signal conductance of the diode

$r_d \equiv$ small signal resistance of the diode, $r_d = \frac{1}{g_d}$

$$\begin{aligned} g_d &= \left. \frac{\partial i_D}{\partial v_D} \right|_{\text{Bias Point or "Quiescent" or "Q-point"}} \\ &= \left. \frac{\partial \left\{ I_S \left(e^{v_D/V_T} - 1 \right) \right\}}{\partial v_D} \right|_{\text{Q-point}} \\ &= \left. \frac{I_S}{V_T} e^{v_D/V_T} \right|_{\text{Q-point}} = \frac{I_S}{V_T} e^{V_D/V_T} e^{v_d/V_T} \end{aligned}$$

Assuming small signals, $v_d \ll V_T$, $e^{v_d/V_T} \rightarrow 1$ and

$$= \frac{I_S e^{V_D/V_T}}{V_T} = \frac{I_S e^{V_D/V_T} - I_S + I_S}{V_T}$$

$$g_d = \frac{I_D + I_S}{V_T}$$

Small Signal Analysis of Diodes

$$i_D = I_D + g_d v_d \quad \longrightarrow \quad I_D = I_o \left(e^{V_A/V_T} - 1 \right) \quad \text{where } V_T = \frac{kT}{q}$$


$$g_d = \frac{I_D + I_S}{V_T} \quad \text{in General}$$

$$g_d \approx \frac{I_D}{V_T} \quad \text{in Forward Bias} \quad \longrightarrow \quad V_A \gg 0 \rightarrow I_D \approx I_o e^{V_A/V_T} \quad \text{where } V_T = \frac{kT}{q}$$

$$g_d \approx \frac{-I_S + I_S}{V_T} \approx 0 \quad \text{in Reverse Bias} \quad \longrightarrow \quad V_A \ll 0 \rightarrow e^{V_A/V_T} \rightarrow 0$$


Small Signal Analysis of Diodes

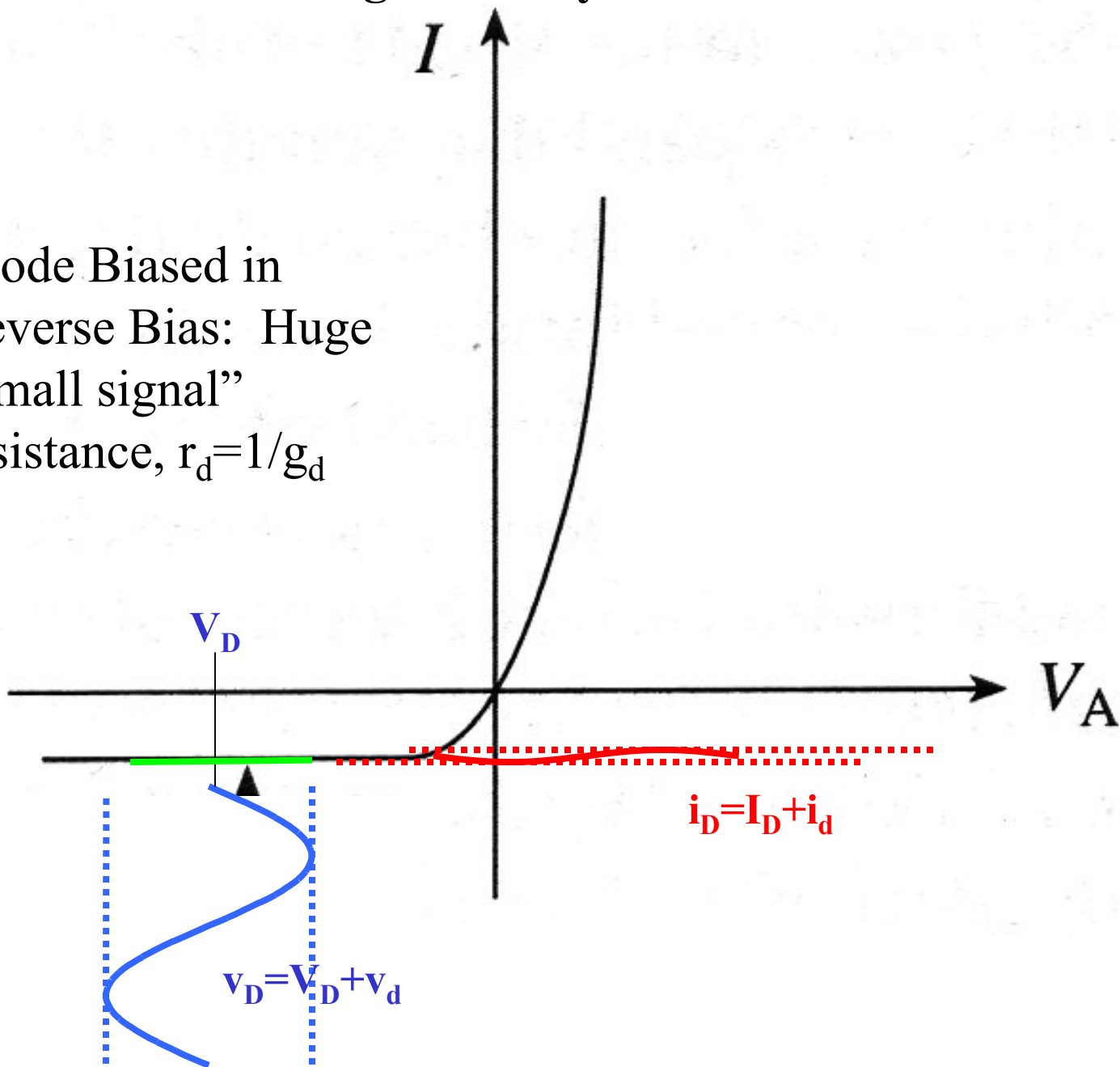Diode Biased in
Reverse Bias: Huge
“small signal”
resistance, $r_d = 1/g_d$




Small Signal Analysis of Diodes:

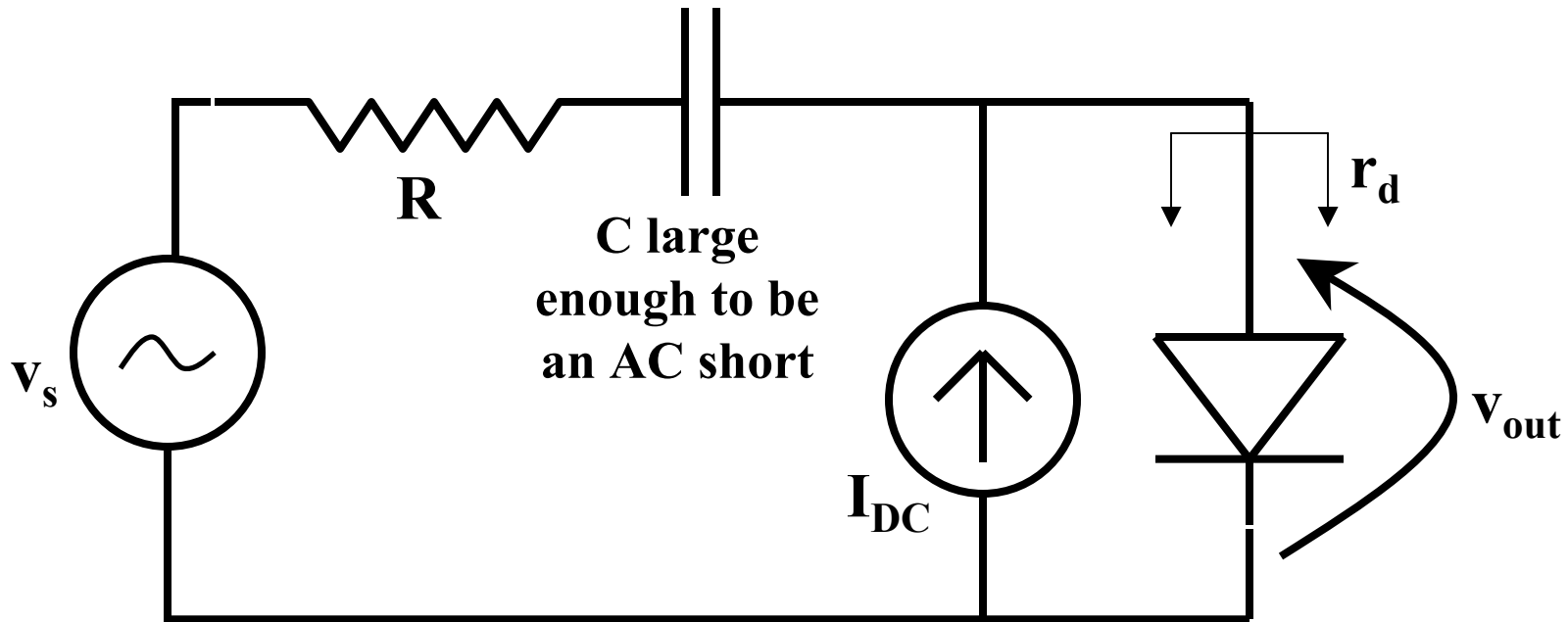Application: Diode as an AC variable attenuator



Small Signal Analysis of Diodes:

Conversion to AC equivalent circuit

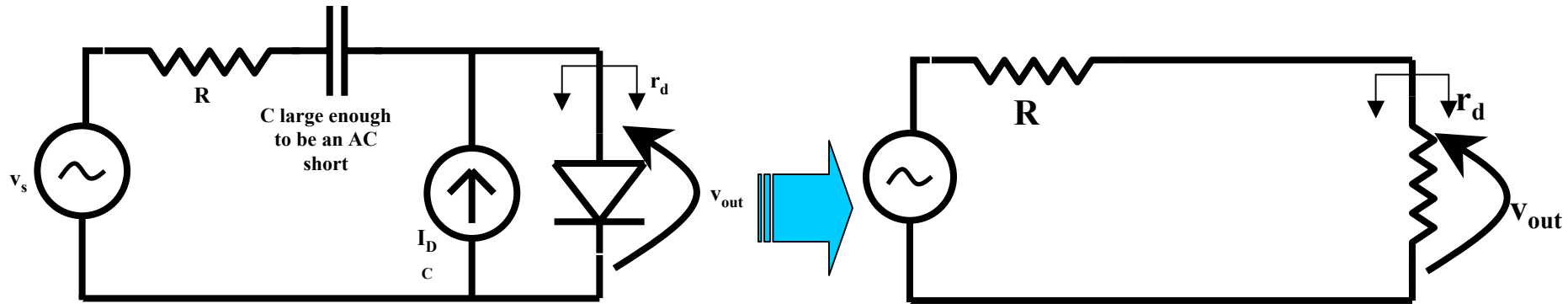


Steps to Analyze a Diode Circuit

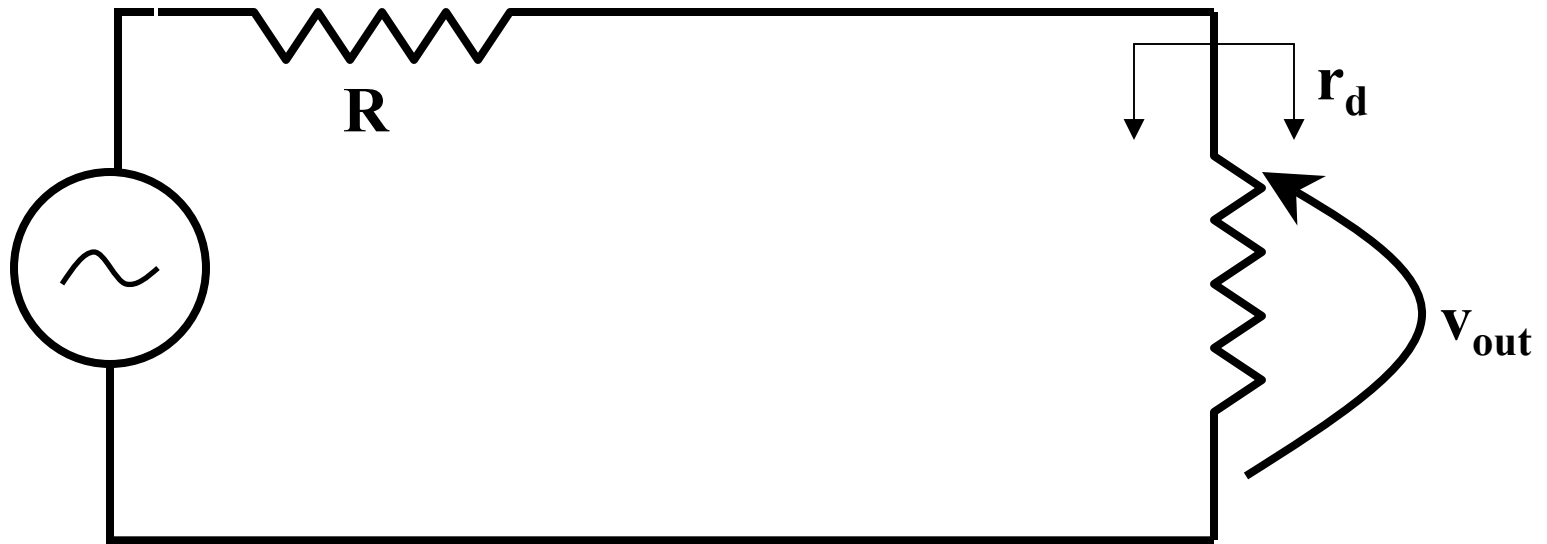- 1.) Determine DC operating point and calculate small signal parameters, r_d and others to come in later lectures)
- 2.) Convert to the AC only model.
 - DC Voltage sources are shorts
 - DC Current sources are open circuits
 - Large capacitors are short circuits
 - Large inductors are open circuits

Small Signal Analysis of Diodes:

Application: Diode as an AC variable attenuator




$$v_{out} = v_{in} \frac{r_d}{r_d + R}$$

$$v_{out} = v_{in} \frac{1}{1 + \frac{R}{r_d}} = v_{in} \frac{1}{1 + \frac{(I_{DC} + I_S)R}{V_T}} \quad \text{or at room temperature}$$

$$v_{out} \approx v_{in} \frac{1}{1 + 40(I_{DC} + I_S)R}$$


Completing the Large signal model of a diode

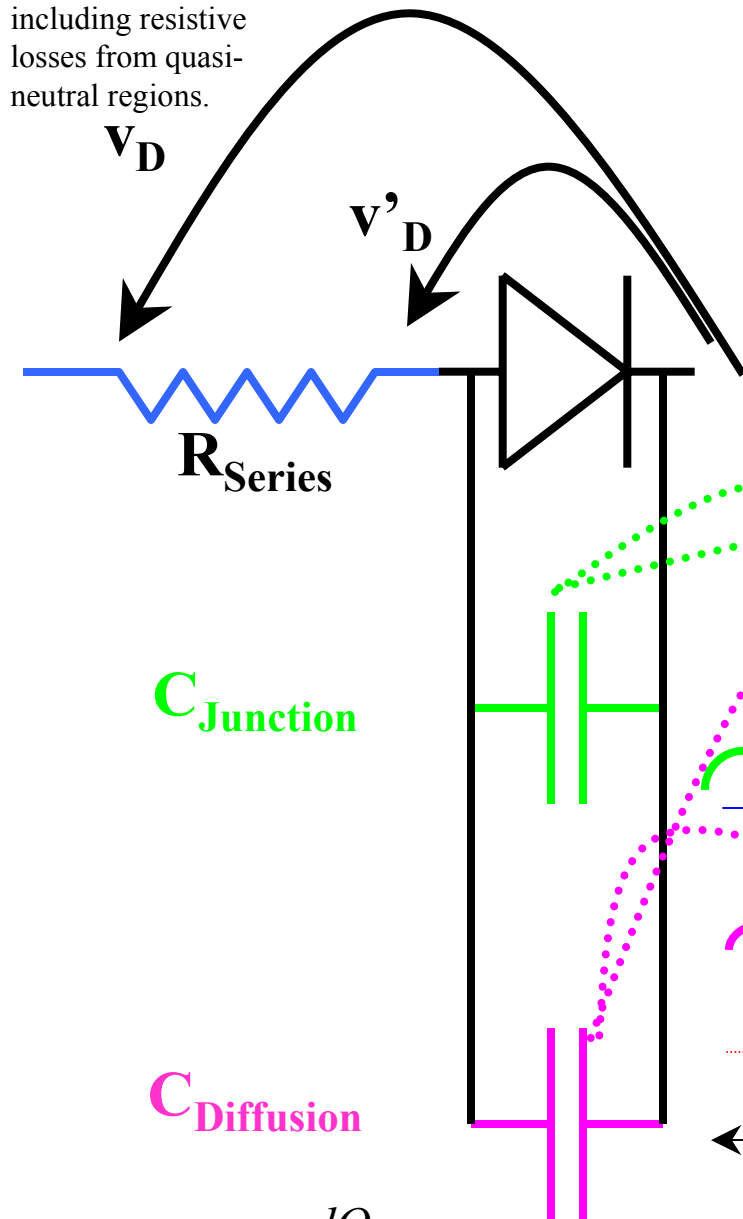Actual voltage drop across the diode including resistive losses from quasi-neutral regions.



$i_D = I_S (\exp(v'_D / (\eta V_T)) - 1)$ where η accounts for previously neglected recombination-generation in the depletion region

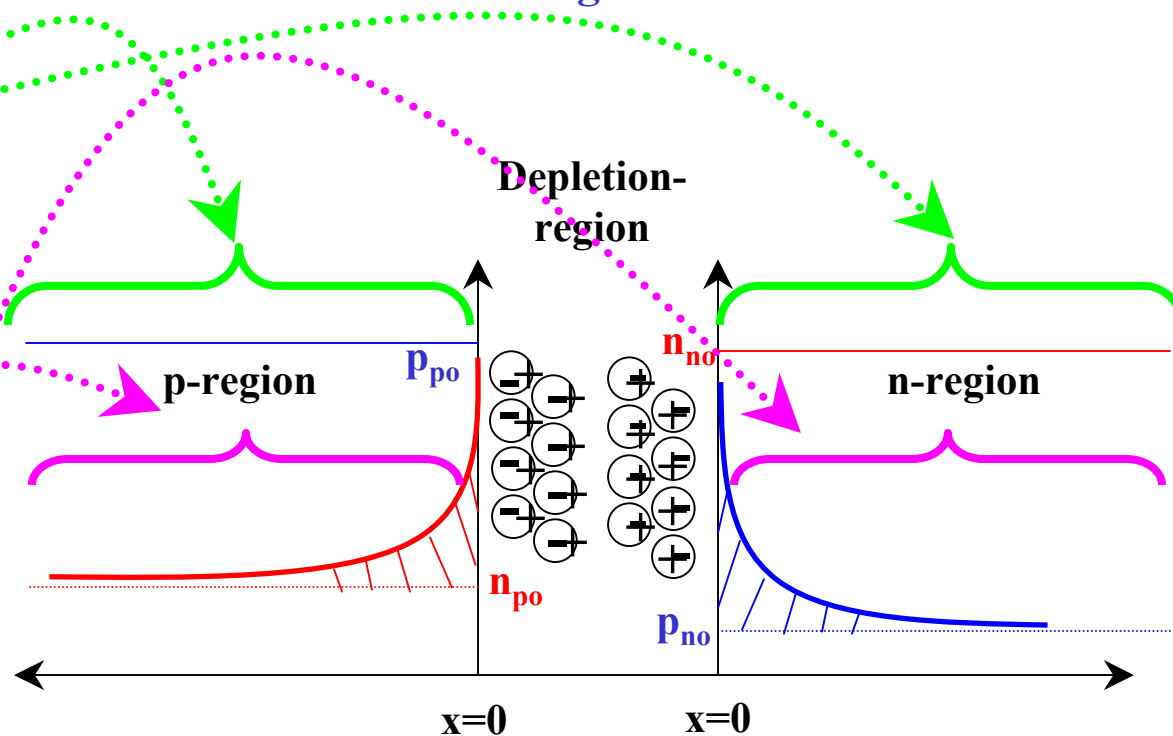$i_D = I_S (\exp[(v_D - i_D R_{Series}) / (\eta V_T)] - 1)$ accounts for the series resistance drop in the quasi-neutral regions.



$C = \frac{dQ}{dv'_D} = \text{Change in charge resulting from a change in voltage}$

Completing the Large signal model of a diode

For an abrupt diode (uniform doping on both sides of the junction):

$$C_{junction} = \frac{K_s \epsilon_o A}{W}$$

but...

$$W = x_p + x_n = \sqrt{\frac{2K_s \epsilon_o (N_A + N_D)}{q N_A N_D} (V_{bi} - V_A)}$$

$$C_{junction} = A \sqrt{\frac{qK_s \epsilon_o N_A N_D}{2 (N_A + N_D) (V_{bi} - V_A)}}$$


Thus,

$$C_{J_0} = C_{junction} \Big|_{V_A=0} = A \sqrt{\frac{qK_s \epsilon_o N_A N_D}{2 (N_A + N_D) (V_{bi})}} \quad \text{and} \quad C_J = \frac{C_{J_0}}{\sqrt{1 - \frac{V_A}{V_{bi}}}}$$

Junction capacitance is due to majority carrier charges displaced by the depletion width (I.e. similar to a parallel plate capacitor).

Completing the Large signal model of a diode

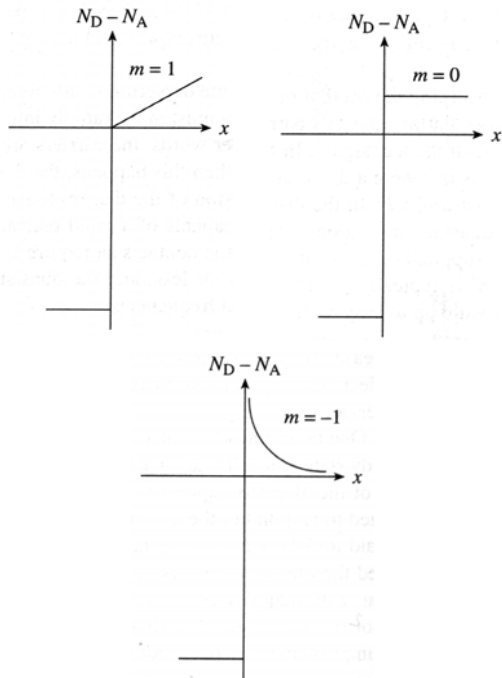More generally for a profile with a constant doping on the heavily doped side of the junction and variable doping profile on the a low doped side that is described by: $N(x)=bx^m$ for all $x>0$



$$C_{junction} = \frac{K_s \epsilon_o A}{W}$$

but...

$$W = x_p + x_n = \left[\frac{(m+2)K_s \epsilon_o}{qb} (V_{bi} - V_A) \right]^{1/(m+2)}$$

$$C_{junction} = \frac{AK_s \epsilon_o}{\left[\frac{(m+2)K_s \epsilon_o}{qb} (V_{bi} - V_A) \right]^{1/(m+2)}}$$

Thus,

$$C_{J0} = C_{junction} \Big|_{V_A=0} = \frac{AK_s \epsilon_o}{\left[\frac{(m+2)K_s \epsilon_o}{qb} (V_{bi}) \right]^{1/(m+2)}} \quad \text{and} \quad C_J = \frac{C_{J0}}{\left(1 - \frac{V_A}{V_{bi}} \right)^{1/(m+2)}}$$

Junction capacitance is due to majority carrier charges displaced by the depletion width (I.e. similar to a parallel plate capacitor).

Completing the Large signal model of a diode

$$C_{Diffusion} = \frac{dQ_D}{dv'_D}$$

$$= \frac{dQ_D}{dt} \frac{dt}{dv'_D}$$

$$Q_D = qA \int_0^\infty p_{no} \left(e^{v'_D/V_T} - 1 \right) e^{-x/L_p} dx + qA \int_0^\infty n_{po} \left(e^{v'_D/V_T} - 1 \right) e^{-x/L_n} dx$$

$$= \left(e^{v'_D/V_T} - 1 \right) [p_{no} L_p + n_{po} L_n] qA$$

$$\frac{dQ_D}{dt} = \frac{1}{V_T} \left(e^{v'_D/V_T} \right) [p_{no} L_p + n_{po} L_n] qA \frac{dv'_D}{dt}$$

$$\frac{dQ_D}{dt} = \frac{1}{V_T} \left[\frac{I_S \left(e^{v'_D/V_T} - 1 + 1 \right)}{I_S} \right] [p_{no} L_p + n_{po} L_n] qA \frac{dv'_D}{dt}$$

Diffusion capacitance due to “excess injected” minority carrier charge at the depletion region edges. Since this charge results from minority carriers, this capacitance is negligible at zero or reverse biases.

Completing the Large signal model of a diode

$$\frac{dQ_D}{dt} = \frac{1}{V_T} \left[\frac{i_D + I_S}{I_S} \right] [p_{no}L_p + n_{po}L_n] qA \frac{dv'_D}{dt}$$

$$\frac{dQ_D}{dt} = \left[\frac{i_D + I_S}{V_T} \right] \frac{[p_{no}L_p + n_{po}L_n] qA}{I_S} \frac{dv'_D}{dt}$$

$i_D = I_D + i_d$
 $i_D \sim I_D$

$$\frac{dQ_D}{dt} = g_d \frac{[p_{no}L_p + n_{po}L_n] qA}{I_S} \frac{dv'_D}{dt}$$

$$C_{Diffusion} = \frac{dQ_D}{dt} \frac{dt}{dv'_D} = g_d \frac{[p_{no}L_p + n_{po}L_n] qA}{I_S} \left(\frac{dv'_D}{dt} \frac{dt}{dv'_D} \right)$$

$$C_{Diffusion} = g_d \frac{[p_{no}L_p + n_{po}L_n] qA}{I_S} = g_d \left[\frac{cm^{-3} cm q cm^2}{\frac{q}{sec}} \right] = g_d [sec]$$

Unit analysis


$C_{Diffusion} = g_d \tau_t$ where $\tau_t = \frac{[p_{no}L_p + n_{po}L_n] qA}{I_S}$ is the transit time or how quickly a carrier can respond to a change in voltage (physically the carriers have to move across the junction, requiring a finite time to do so)

or in SPICE, $C_{Diffusion} = \frac{\partial i_D}{\partial v_D} \tau_t$

Diffusion capacitance due to “excess injected” minority carrier charge at the depletion region edges.

Summary of the Large signal model of a diode (SPICE Model)
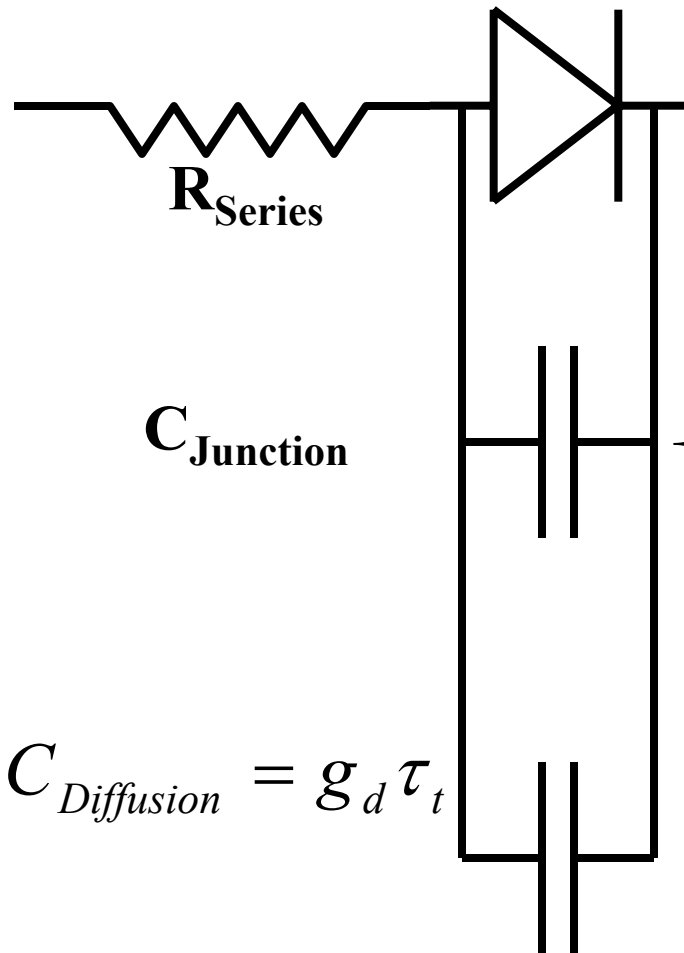
$$i_D = I_S \left(e^{\frac{(v_D - i_D R_{Series})}{\eta V_T}} - 1 \right)$$




$$C_{Jo} = C_{junction} \Big|_{V_A=0} = \frac{AK_S \epsilon_o}{\left[\frac{(m+2)K_S \epsilon_o}{qb} (V_{bi}) \right]^{1/(m+2)}}$$

and $C_J = \frac{C_{Jo}}{\left(1 - \frac{V_A}{V_{bi}} \right)^{1/(m+2)}} \Rightarrow f(V_A)$

- 1.) Mathematical model
- 2.) SPICE Model (this page)
- 3.) Ideal Diode Model
- 4.) Constant Voltage Drop (CVD) Model
- 5.) Graphical circuit model


Addition of Capacitance Components

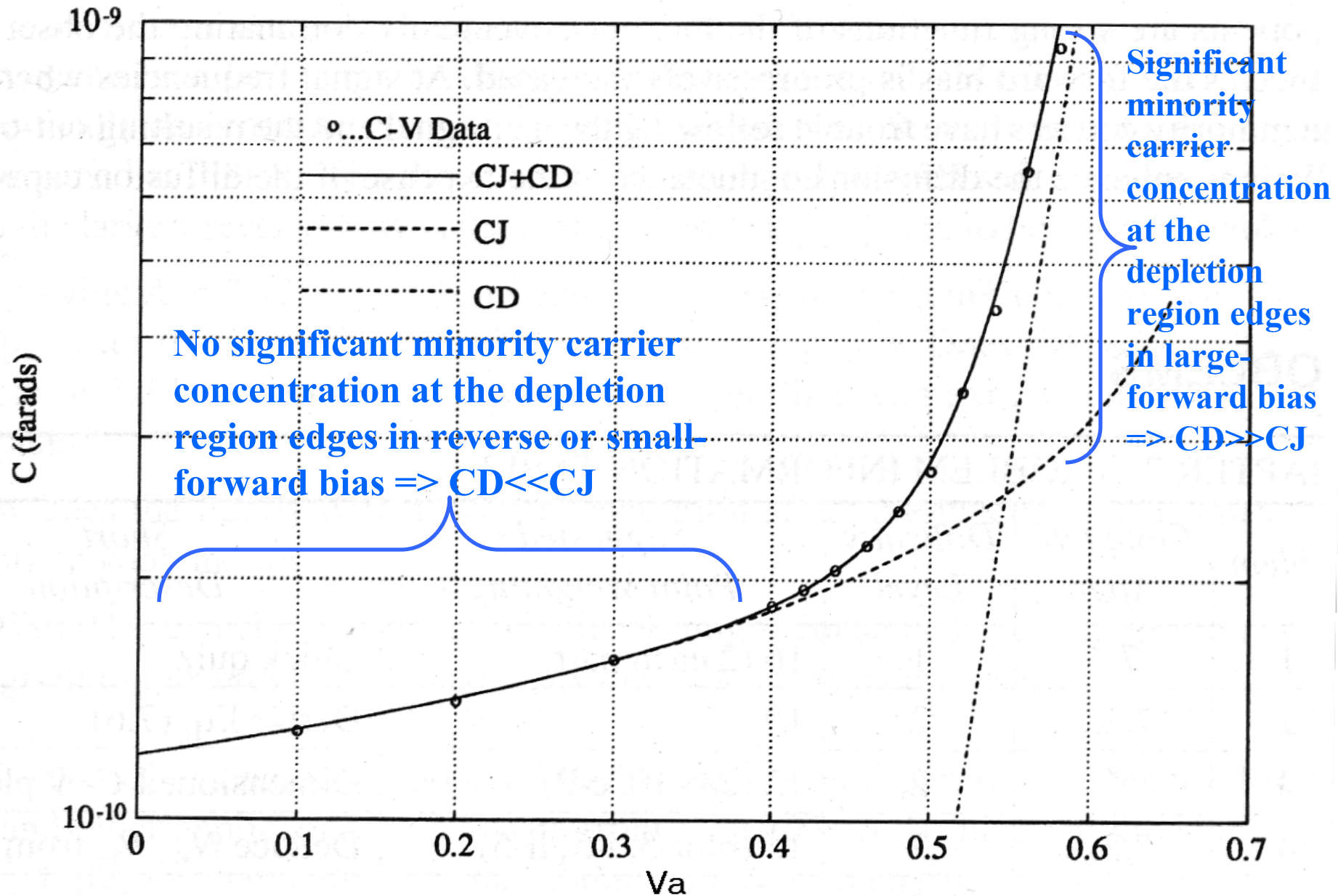

Summary of the Small signal model of a diode

$$i_D = I_D + g_d v_d \quad \text{where} \quad g_d = \frac{I_D + I_S}{V_T}$$

$$r_d = 1/g_d \Rightarrow f(I_D)$$

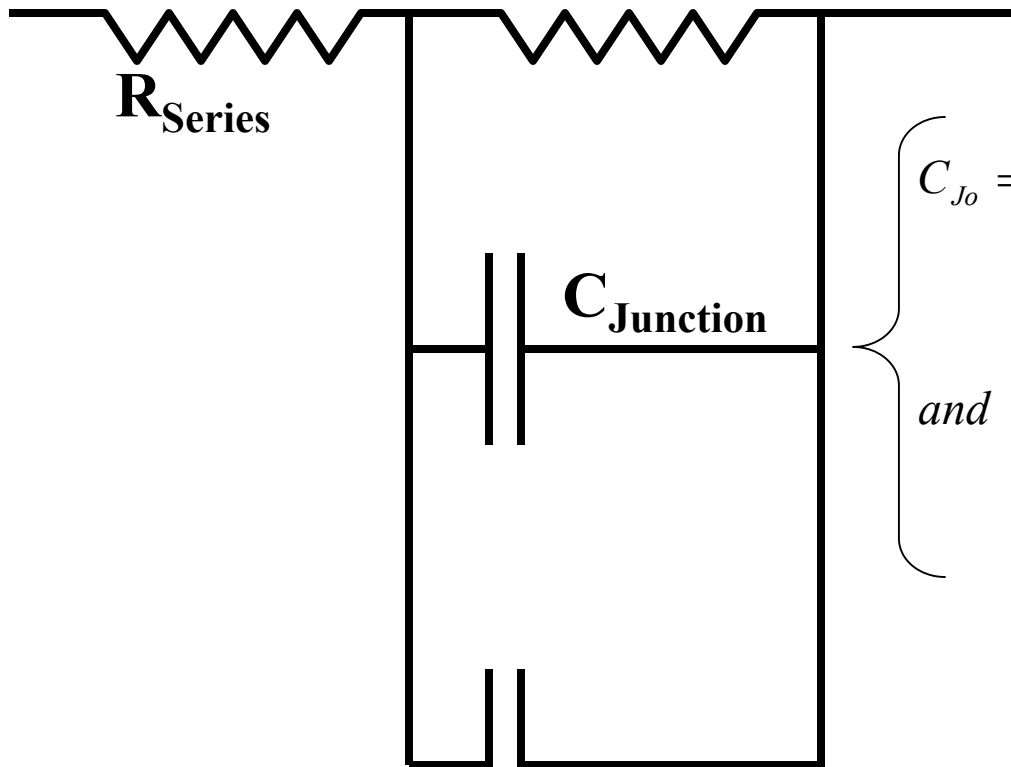

$$C_{J_0} = C_{junction} \Big|_{V_A=0} = \frac{AK_S \epsilon_o}{\left[\frac{(m+2)K_S \epsilon_o}{qb} (V_{bi}) \right]^{1/(m+2)}}$$

and $C_J = \frac{C_{J_0}}{\left(1 - \frac{V_A}{V_{bi}} \right)^{1/(m+2)}} \Rightarrow f(V_A)$

$$C_{Diffusion} = g_d \tau_t \Rightarrow f(I_D)$$

Things we have added to account for “Non-ideal” behavior

- Series resistance to account for finite resistance of the quasi-neutral regions and metal contact resistance's.
- Diode “ideality factor”, η , to account for thermal recombination-generation in the depletion region.
- Junction capacitance due to majority carrier charges displaced by the depletion width (I.e. similar to a parallel plate capacitor).
- Diffusion capacitance due to “excess injected” minority carrier charge at the depletion region edges. Since this charge results from minority carriers, this capacitance is negligible at zero or reverse biases.



Things we still need to add to account for “Non-ideal” behavior

- Reverse “Breakdown” characteristics
 - “Breakdown” is a deceptive term because no damage typically occurs to the device. Often diodes are designed to operate in the breakdown mode.

Breakdown Mechanisms

Avalanche Breakdown:

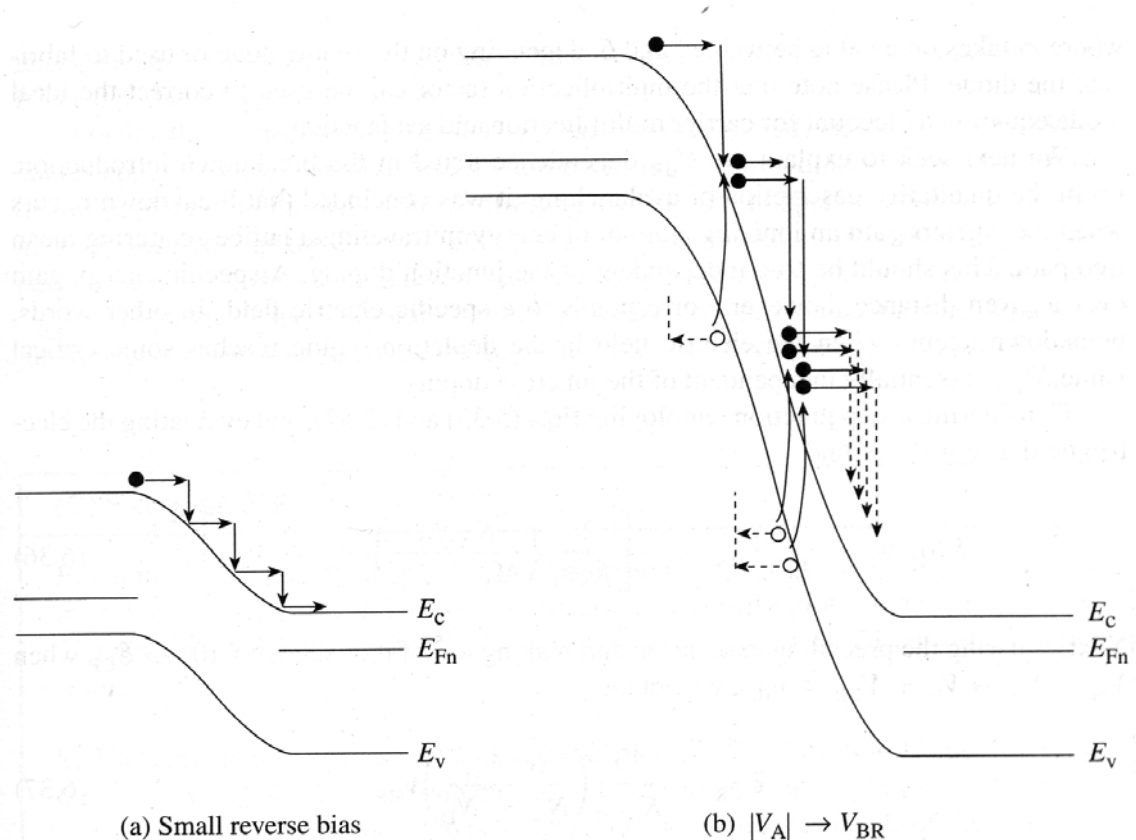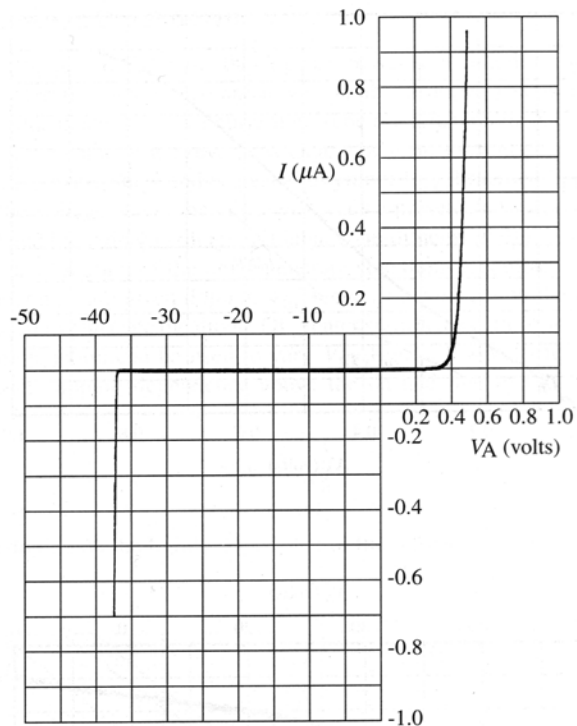Excess current flows due to electron-hole pair multiplication due to impact ionization. This current rapidly increases with increasing reverse bias.



Breakdown Mechanisms

Zener Breakdown:

Excess current flows due to bonding electrons “tunneling” into empty conduction band states. The “tunneling barrier” must be sufficiently thin. This current rapidly increases with increasing reverse bias.


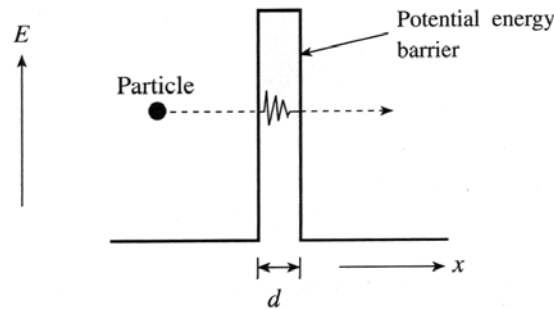


Figure 6.13 General visualization of tunneling.

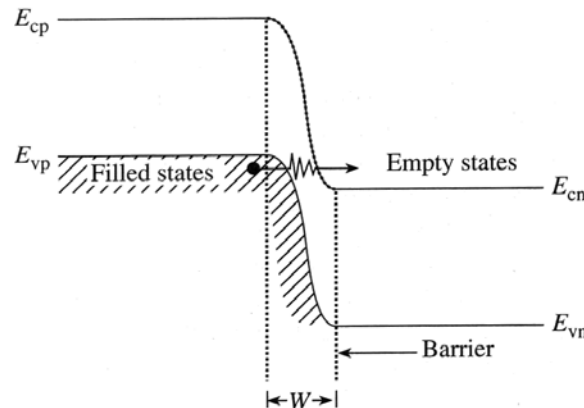

“Zener” Diodes

Zener diodes may actually operate based on either avalanche or zener breakdown mechanisms.

Rule of thumb: $|V_{BR}| > 6E_G/q$ is typically Avalanche Breakdown

Slightly different symbol

