

Lecture 19

Bipolar Junction Transistors (BJT): Part 3



**Ebers Moll Large Signal BJT Model, Using CVD
model to solve for DC bias point**

Reading:

Pierret 11.1



Development of the Large Signal Model of a BJT (Ebers-Moll Model)

PNP in Active Mode

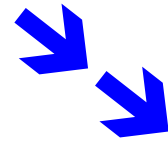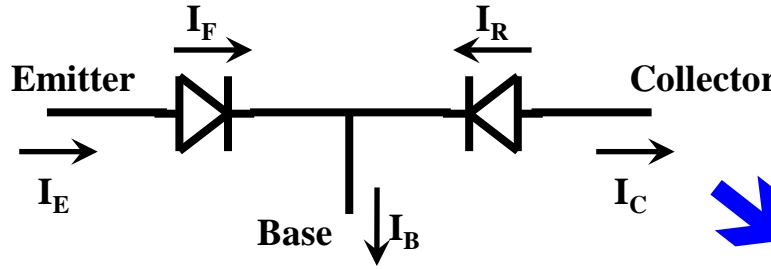


Ideal Diodes
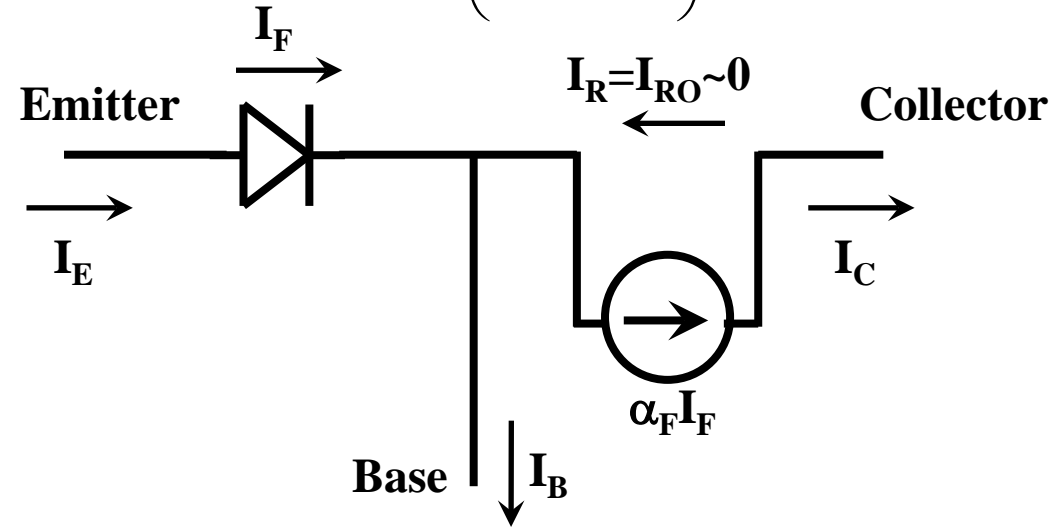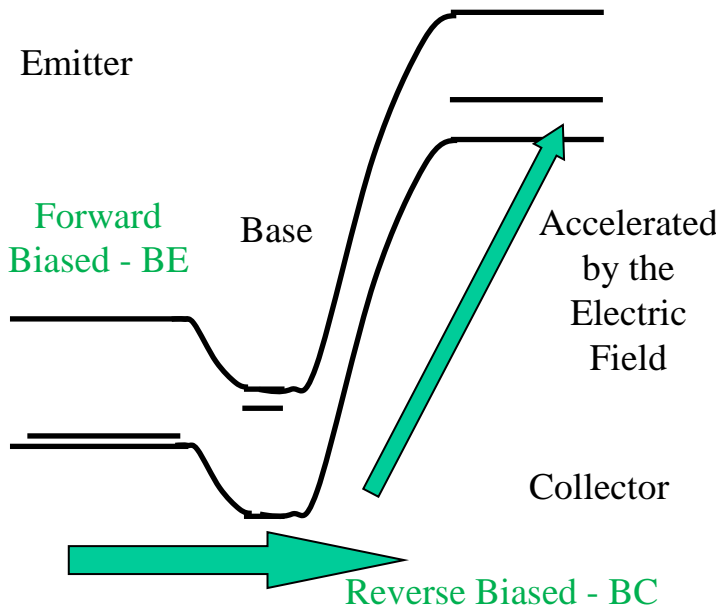
$$I_F = I_{F0} \left(e^{V_{EB}/V_T} - 1 \right)$$






Development of the Large Signal Model of a BJT (Ebers-Moll Model)

PNP in Inverse Active Mode

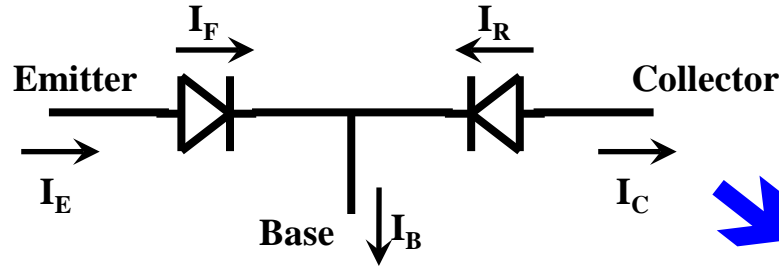

Ideal Diodes
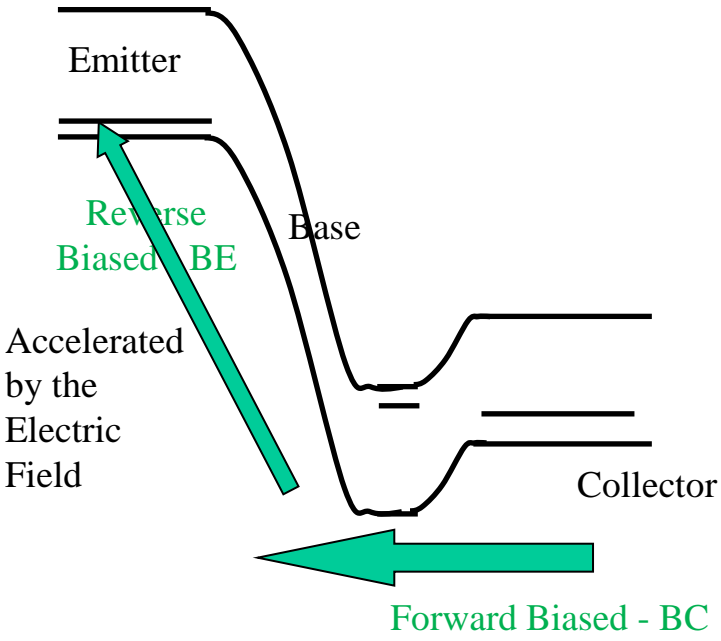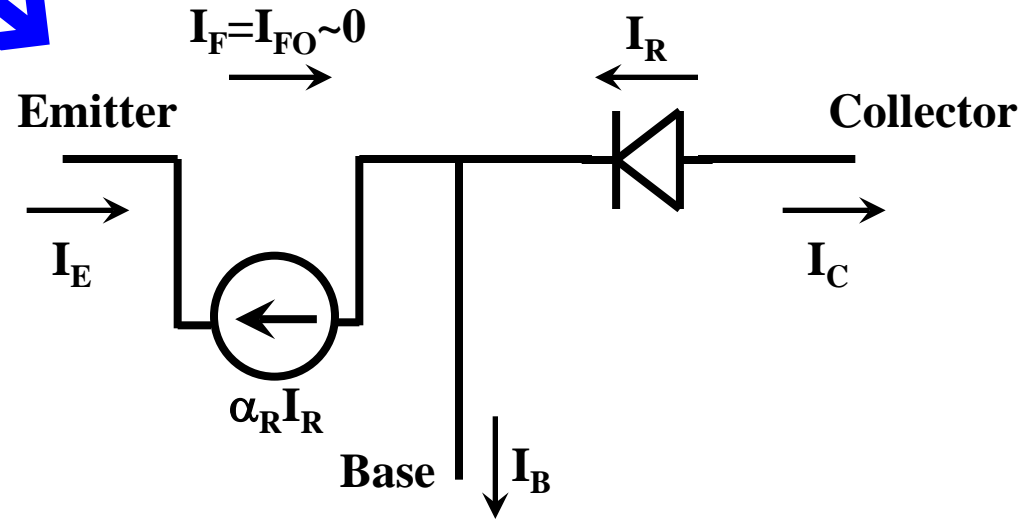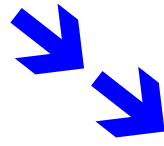
$$I_R = I_{R0} \left(e^{V_{CB}/V_T} - 1 \right)$$



In Inverse Active bias mode, the transistor still “sort of” works (may attenuate instead of amplify) but works poorly because the doping order of emitter, base and collector are reversed.


Development of the Large Signal Model of a BJT (Ebers-Moll Model)

Full Ebers Moll Model of a PNP

Ideal Diodes

Note: $A = \alpha_R I_{R0} = \alpha_F I_{F0}$
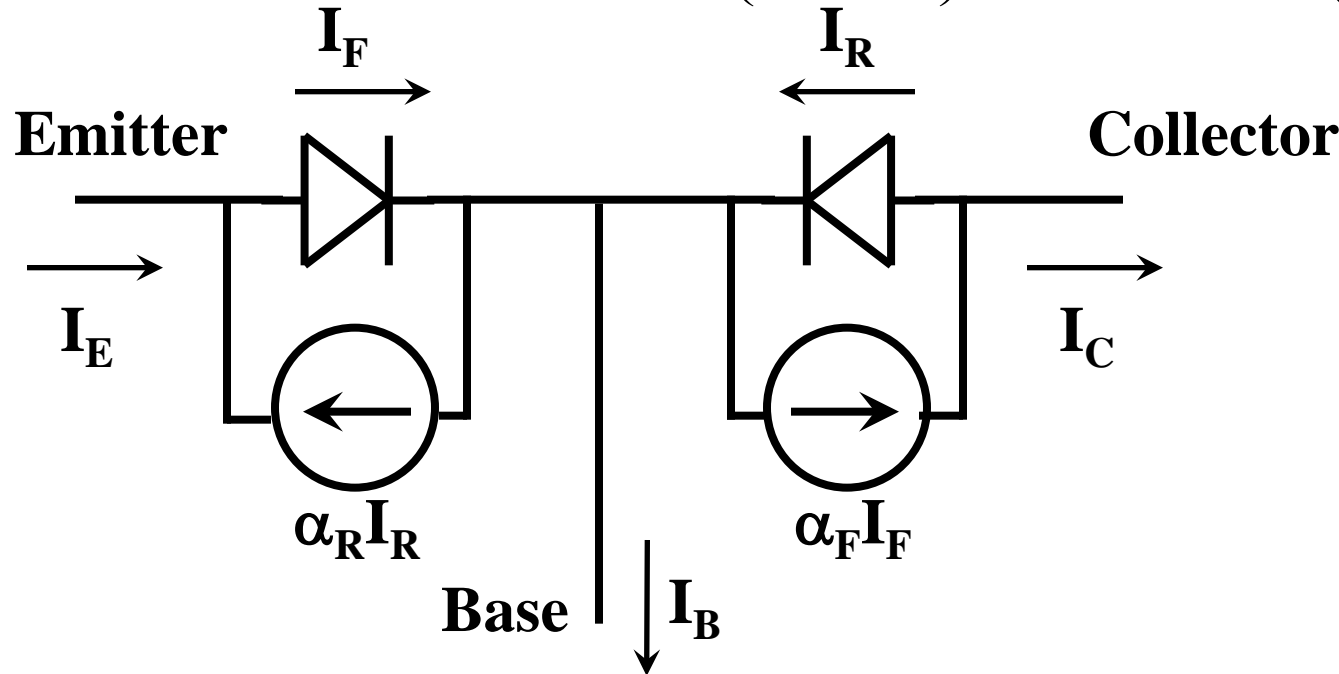
$$I_F = I_{F0} \left(e^{V_{EB}/V_T} - 1 \right) \quad \text{and} \quad I_R = I_{R0} \left(e^{V_{CB}/V_T} - 1 \right)$$



$$I_E = I_{F0} \left(e^{V_{EB}/V_T} - 1 \right) - \alpha_R I_{R0} \left(e^{V_{CB}/V_T} - 1 \right)$$


$$I_C = \alpha_F I_{F0} \left(e^{V_{EB}/V_T} - 1 \right) - I_{R0} \left(e^{V_{CB}/V_T} - 1 \right)$$

Development of the Large Signal Model of a BJT (Ebers-Moll Model)

Full Ebers Moll Model of a NPN

Ideal Diodes
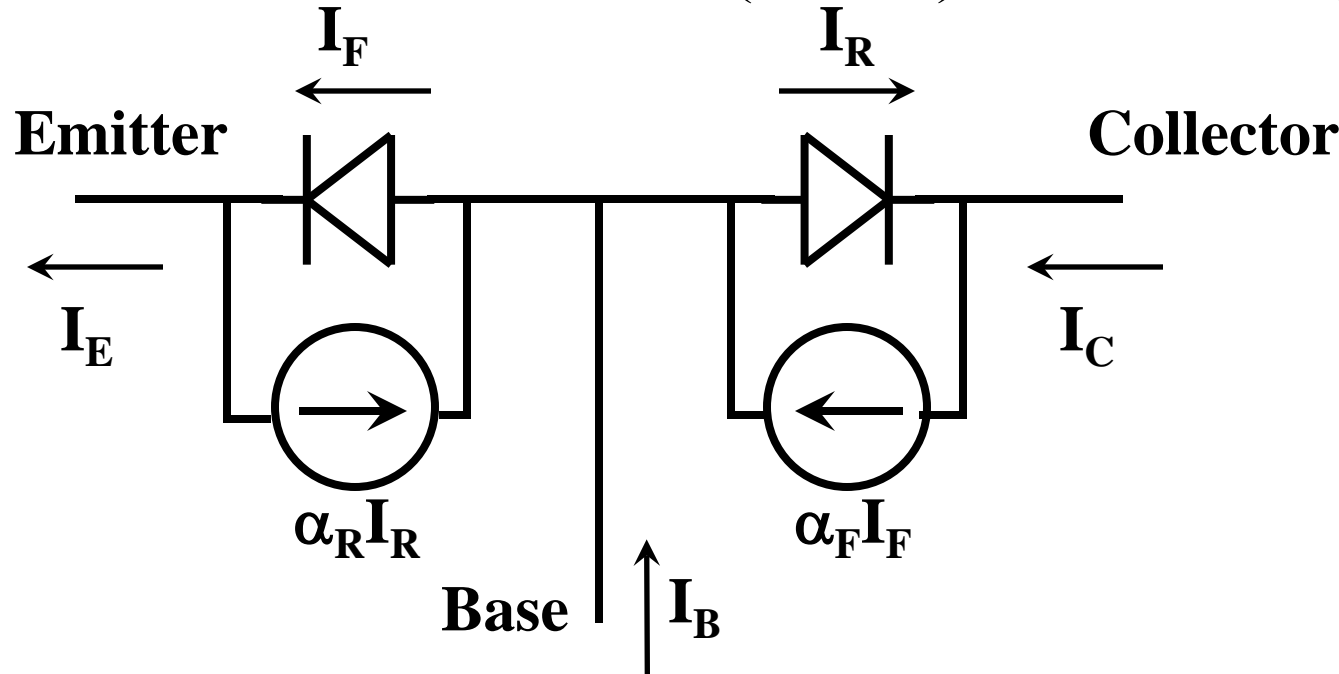
$$I_F = I_{F0} \left(e^{V_{BE}/V_T} - 1 \right) \quad \text{and} \quad I_R = I_{R0} \left(e^{V_{BC}/V_T} - 1 \right)$$



$$I_E = I_{F0} \left(e^{V_{BE}/V_T} - 1 \right) - \alpha_R I_{R0} \left(e^{V_{BC}/V_T} - 1 \right)$$

$$I_C = \alpha_F I_{F0} \left(e^{V_{BE}/V_T} - 1 \right) - I_{R0} \left(e^{V_{BC}/V_T} - 1 \right)$$

Using the Ebers-Moll model requires mathematical complexity (and much pain). Thus, we have an approximate solution method* that allows a quick solution.

*I refer to as the “CVD/Beta Analysis”. This is just my term, not a universal name.

Quick Solution using a CVD/Beta Approach


Consider the following pnp BJT circuit with a common emitter current gain, $\beta_{DC}=180.7$. Find I_B , I_C , and I_E assuming a turn on voltage of 0.7V.

Neglect Leakage currents

$$I_C = \alpha_{dc} I_E + I_{CBo}$$

$$I_C = \beta_{dc} I_B + I_{CEo}$$

$$I_E = I_B + I_C$$

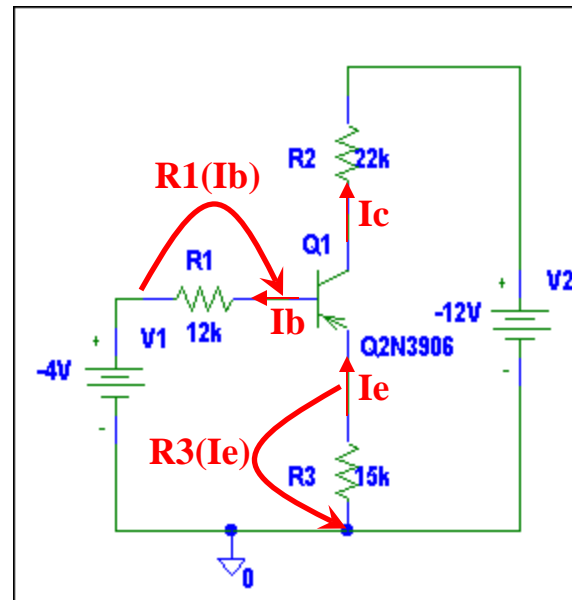

$$0 = -4V + I_B(12000) + V_{EB} + I_E(15000)$$

$$4V = I_B(12000) + 0.7V + I_C(1/\alpha_{DC})(15000)$$

$$4V = I_B(12000) + 0.7V + [\beta_{DC} I_B][(1 + \beta_{DC}) / \beta_{DC}](15000)$$

$$3.3V = I_B[(12000) + (1 + 180.7)(15000)]$$


$$I_B = 1.2\mu A$$

$$I_C = 180.7 I_B = 218\mu A$$


$$I_E = (181.7/180.7) I_C = 219\mu A$$

Development of the Large Signal Model of a BJT (Ebers-Moll Model)

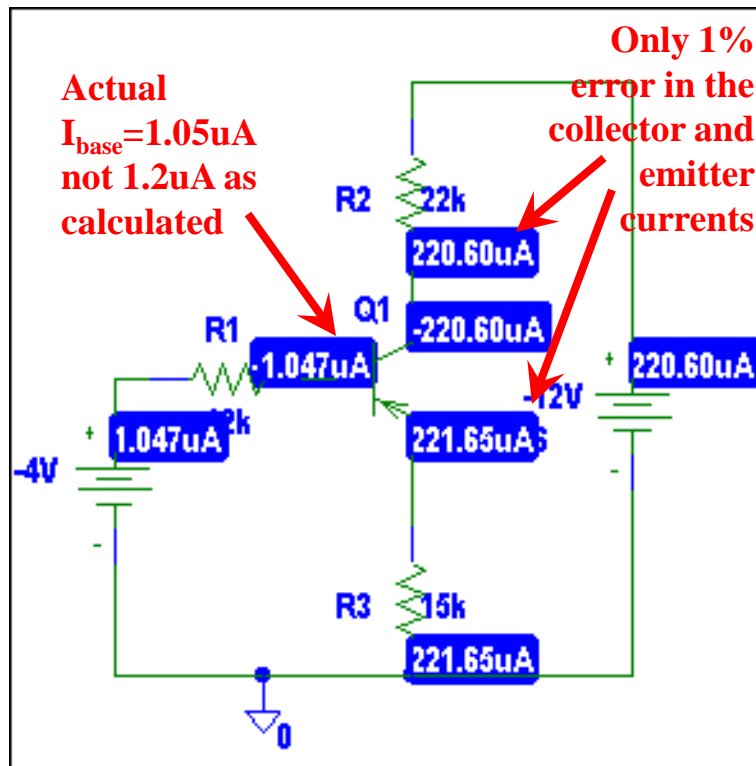Compare our results using the CVD/Beta model to the full Ebers-Moll solution used in PSPICE...



Current into various nodes

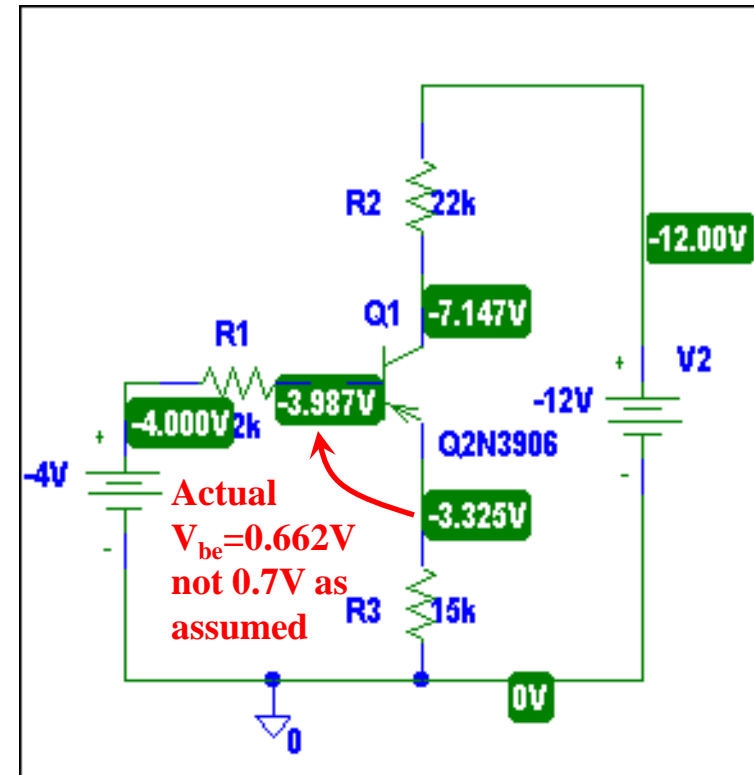


Voltage at various nodes

Development of the Large Signal Model of a BJT (Ebers-Moll Model)



Common Base

Optional

THEORY

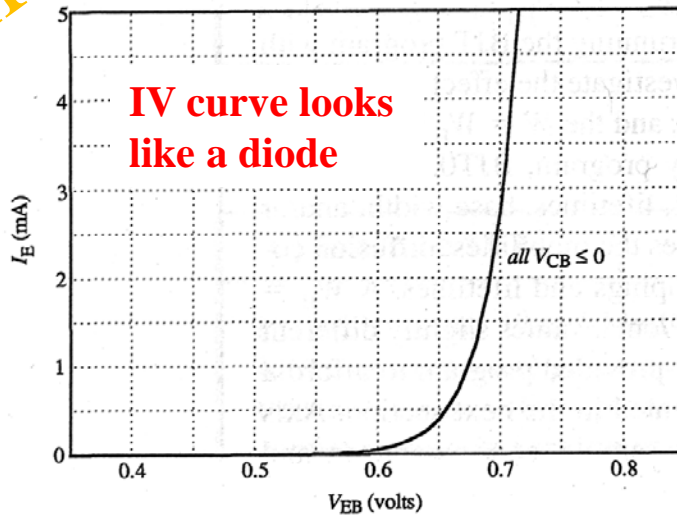


EXPERIMENT

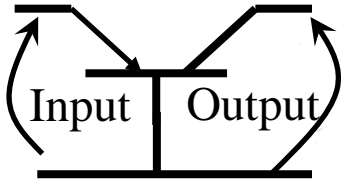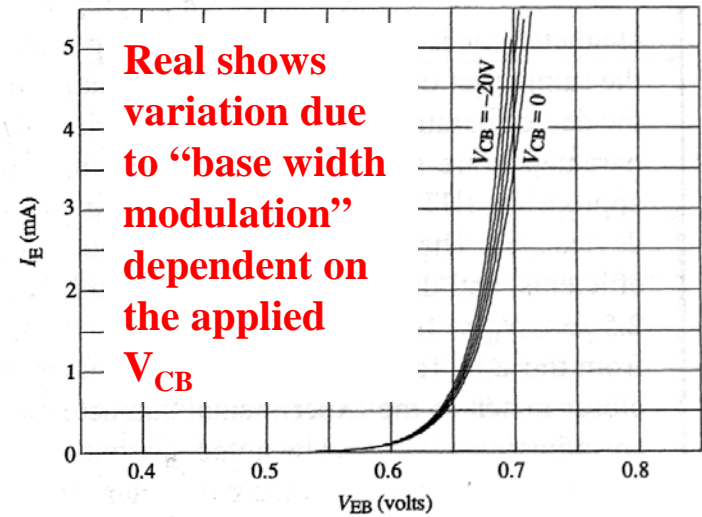


Input Output

I_E and I_C and V_{EB} ($-V_{CB}$)

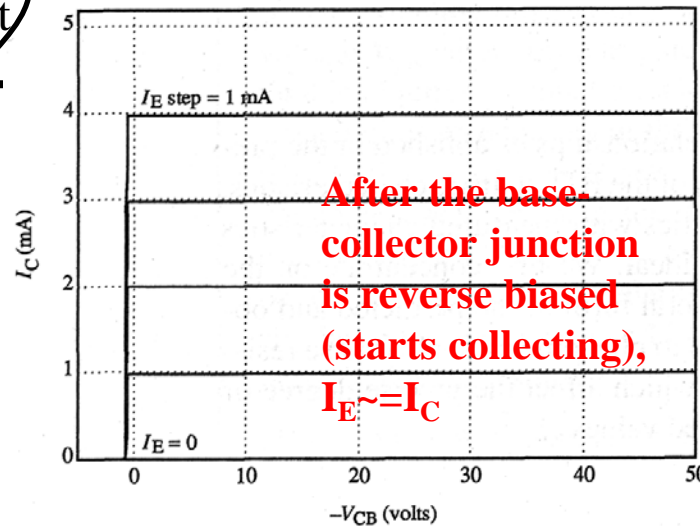

(c)

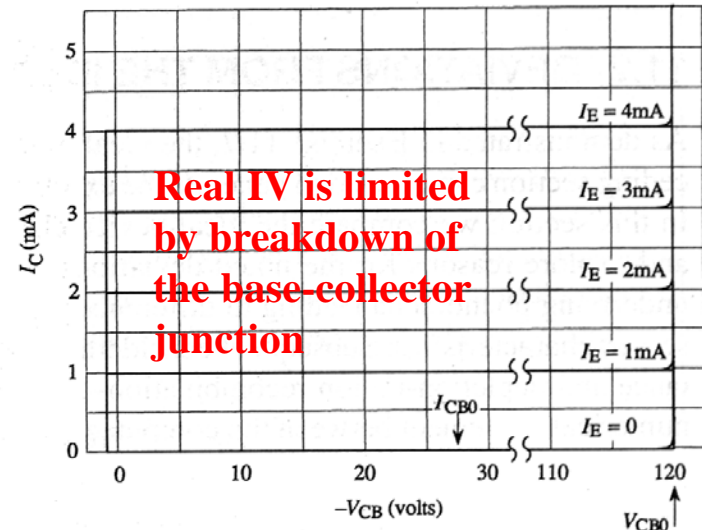


(d)

Development of the Large Signal Model of a BJT (Ebers-Moll Model)



Common Emitter

Optional

THEORY


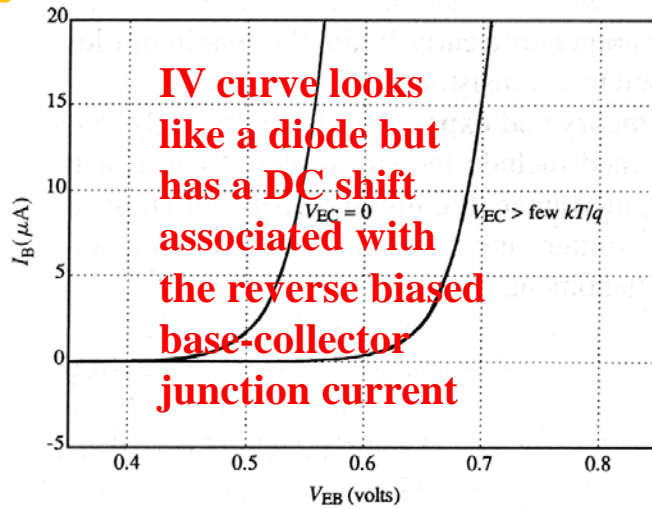


EXPERIMENT

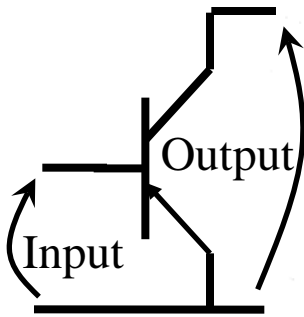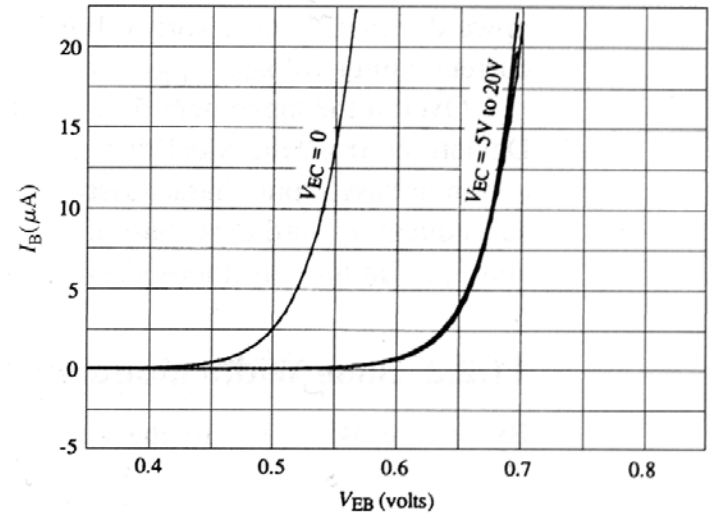

Input Output

I_B and I_C and V_{EB} and V_{EC}

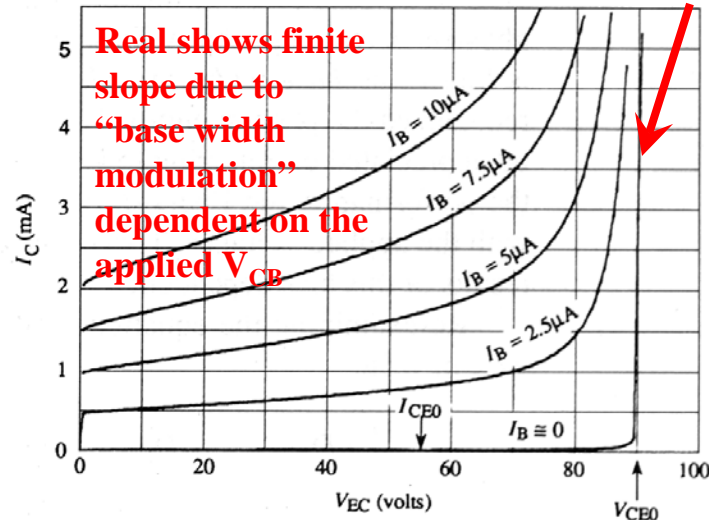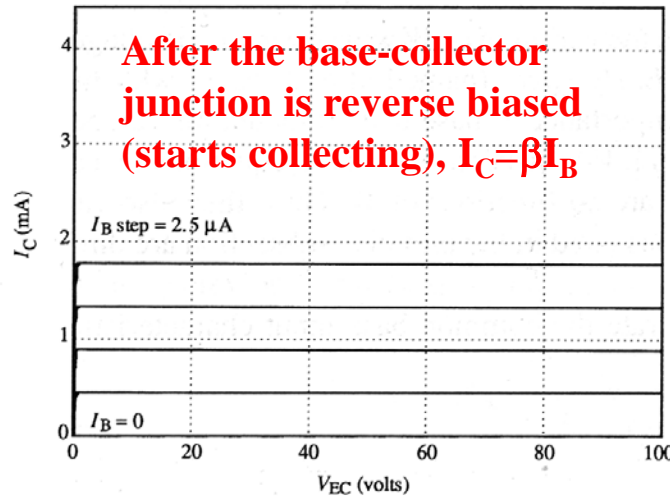

Development of the Large Signal Model of a BJT (Ebers-Moll Model)

Optional

$$I_E = qA \left[\frac{D_E n_{E0}}{L_E} + \frac{D_B p_{B0}}{L_B} \frac{\cosh(W/L_B)}{\sinh(W/L_B)} \right] \left(e^{V_{EB}/V_T} - 1 \right) - qA \left[\frac{D_B p_{B0}}{L_B} \frac{1}{\sinh(W/L_B)} \right] \left(e^{V_{CB}/V_T} - 1 \right)$$

*

$$I_C = qA \left[\frac{D_B p_{B0}}{L_B} \frac{1}{\sinh(W/L_B)} \right] \left(e^{V_{EB}/V_T} - 1 \right) - qA \left[\frac{D_C n_{C0}}{L_C} + \frac{D_B p_{B0}}{L_B} \frac{\cosh(W/L_B)}{\sinh(W/L_B)} \right] \left(e^{V_{CB}/V_T} - 1 \right)$$

$$I_E = I_{F0} \left(e^{V_{EB}/V_T} - 1 \right) - A \left(e^{V_{CB}/V_T} - 1 \right)$$

$$I_C = A \left(e^{V_{EB}/V_T} - 1 \right) - I_{R0} \left(e^{V_{CB}/V_T} - 1 \right)$$

Development of the Large Signal Model of a BJT (Ebers-Moll Model)

Optional

$$I_E = I_{F0} \left(e^{V_{EB}/V_T} - 1 \right) - A \left(e^{V_{CB}/V_T} - 1 \right)$$

$$I_C = A \left(e^{V_{EB}/V_T} - 1 \right) - I_{R0} \left(e^{V_{CB}/V_T} - 1 \right)$$

When $V_{CB}=0$,

$$I_E = I_{F0} \left(e^{V_{EB}/V_T} - 1 \right) \quad \text{and} \quad I_C = A \left(e^{V_{EB}/V_T} - 1 \right)$$


but,

$$I_{F0} > A \quad (\text{see } *)$$


Thus,

$$I_E = I_{F0} \left(e^{V_{EB}/V_T} - 1 \right) \quad \text{and} \quad I_C = \alpha_F I_{F0} \left(e^{V_{EB}/V_T} - 1 \right) = I_C = \alpha_F I_E$$
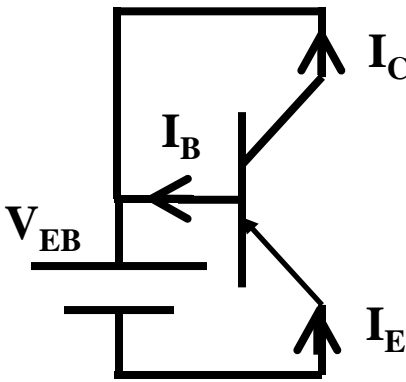
$$\text{but, } I_C = \alpha_F I_E \rightarrow \alpha_F = \alpha_{DC} \quad \text{common base current gain}$$



Looks like a diode

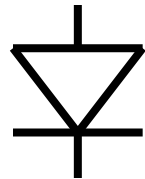

The collector current is the fraction of the emitter current “collected”


Development of the Large Signal Model of a BJT (Ebers-Moll Model)

Optional

$$I_E = I_{F0} \left(e^{V_{EB}/V_T} - 1 \right) - A \left(e^{V_{CB}/V_T} - 1 \right)$$

$$I_C = A \left(e^{V_{EB}/V_T} - 1 \right) - I_{R0} \left(e^{V_{CB}/V_T} - 1 \right)$$

When $V_{EB}=0$,

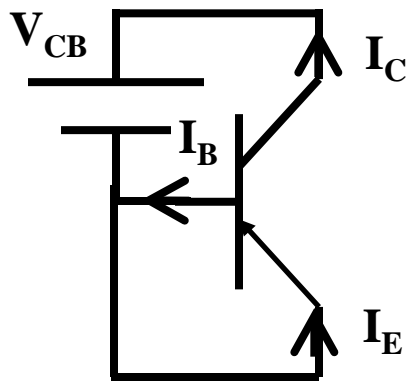

$$I_E = -A \left(e^{V_{CB}/V_T} - 1 \right) \quad \text{and} \quad I_C = -I_{R0} \left(e^{V_{CB}/V_T} - 1 \right)$$

but,


$$I_{R0} > A \quad (\text{see } *)$$

Thus,

$$I_E = -\alpha_R I_{R0} \left(e^{V_{CB}/V_T} - 1 \right) \quad \text{and} \quad I_C = -I_{R0} \left(e^{V_{CB}/V_T} - 1 \right)$$

$$\text{but, } I_E = \alpha_R I_C \rightarrow \alpha_R \neq \alpha_{DC}$$

Looks like a diode

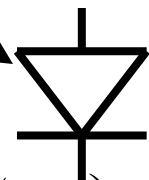

In Inverse Active mode, the emitter current is the fraction of the collector current “collected”