

Lecture 27

Amplifier Configurations

Reading:

CE/CS: Jaeger 13.6, 13.9, 13.10, 13.11


CC/CD: Jaeger 14.1, 14.3

CB(CG: Jaeger 14.1, 14.4

and Notes

Amplifier Configurations

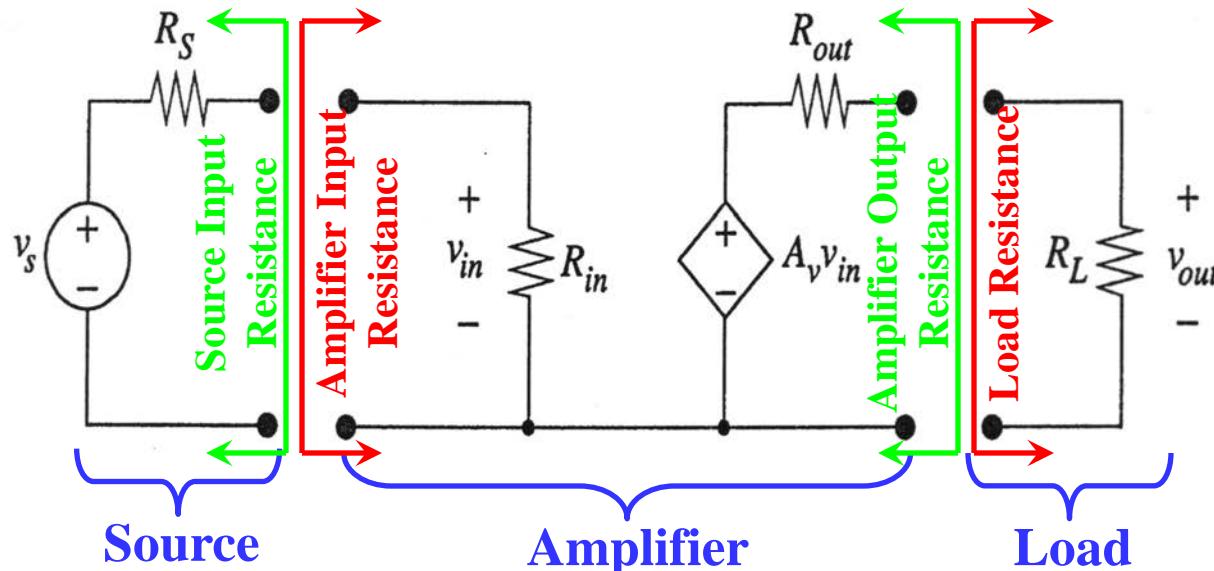Voltage Amplifier: Voltage input and Voltage output




- Any signal source has a finite “source resistance”, R_s .
- The amplifier is often asked to drive current into a load of finite impedance, R_L (examples: 8 ohm speaker, 50 ohm transmission line, etc...)

The controlled source is a Voltage-controlled-Voltage Source

A_v =Open Circuit Voltage Gain can be found by applying a voltage source with $R_s=0$, and measuring the open circuit output voltage (no load or $R_L=\infty$)

Amplifier Configurations

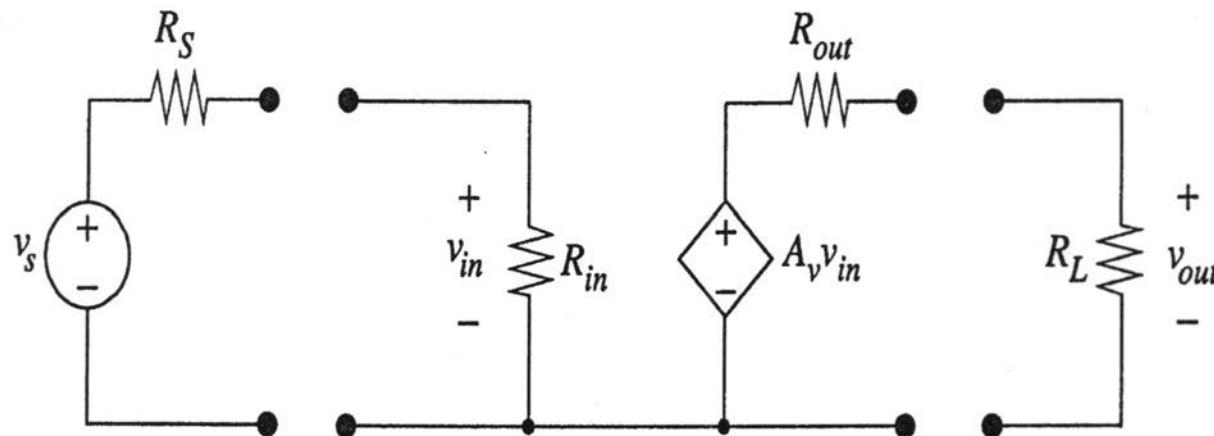
Why is the input and output resistance important?



- Only the voltage v_{in} is amplified to $A_v v_{in}$.
- Since R_s and R_{in} form a voltage divider that determines v_{in} , you want R_{in} as large as possible (for a voltage amplifier) for maximum voltage gain.
- Since R_L and R_{out} form a voltage divider that determines v_{out} , you want R_{out} as small as possible (for a voltage amplifier) for maximum voltage gain.

Amplifier Configurations

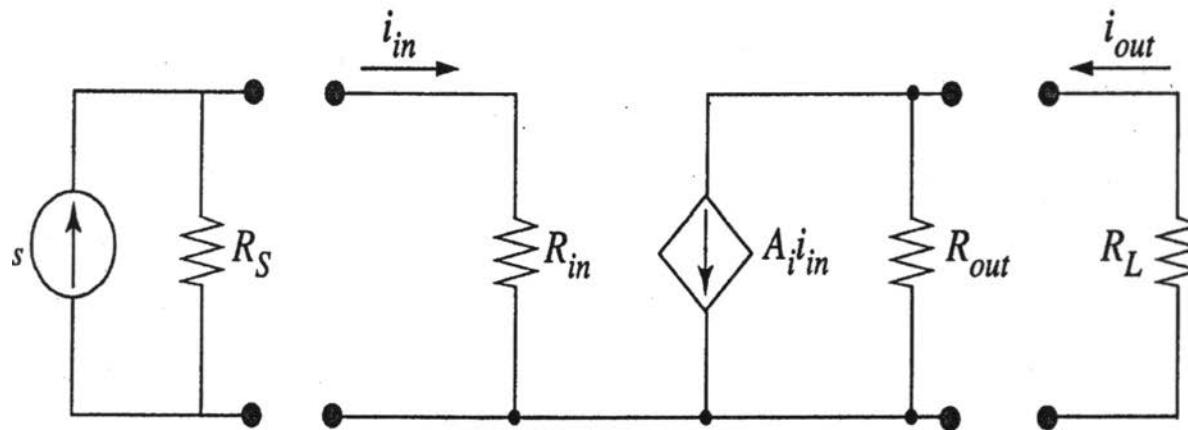Current Amplifier: Current input and Current output




The controlled source is a Current-controlled-Current Source

A_i =Short Circuit Current Gain can be found by applying a current source with $R_s = \infty$, and measuring the short circuit output current (No Load or $R_L = 0$)

- Only the current i_{in} is amplified to $A_i i_{in}$.
- Since R_s and R_{in} form a current divider that determines i_{in} , you want R_{in} as small as possible (for a current amplifier) for maximum current gain.
- Since R_L and R_{out} form a current divider that determines i_{out} , you want R_{out} as large as possible (for a current amplifier) for maximum current gain.

Amplifier Configurations

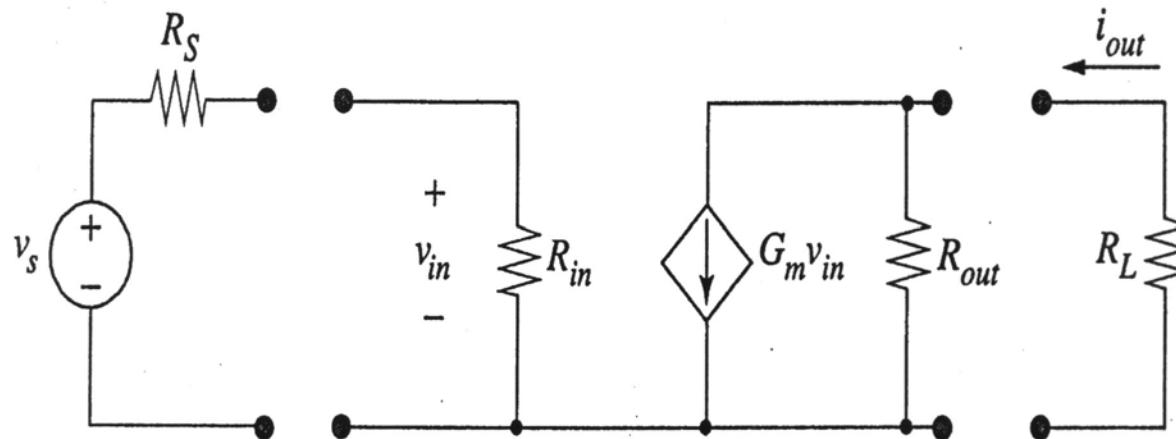Transconductance Amplifier: Voltage input and Current output




The controlled source is a Voltage-controlled-Current Source

G_m =Transconductance Gain can be found by applying a voltage source with $R_s=0$, and measuring the short circuit output current
(No Load or $R_L=0$)

- Only the voltage v_{in} is amplified to $i_{out}=G_m v_{in}$.
- Since R_s and R_{in} form a voltage divider that determines v_{in} , you want R_{in} as large as possible for maximum transconductance gain.
- Since R_L and R_{out} form a current divider that determines i_{out} , you want R_{out} as large as possible for maximum transconductance gain.

Amplifier Configurations

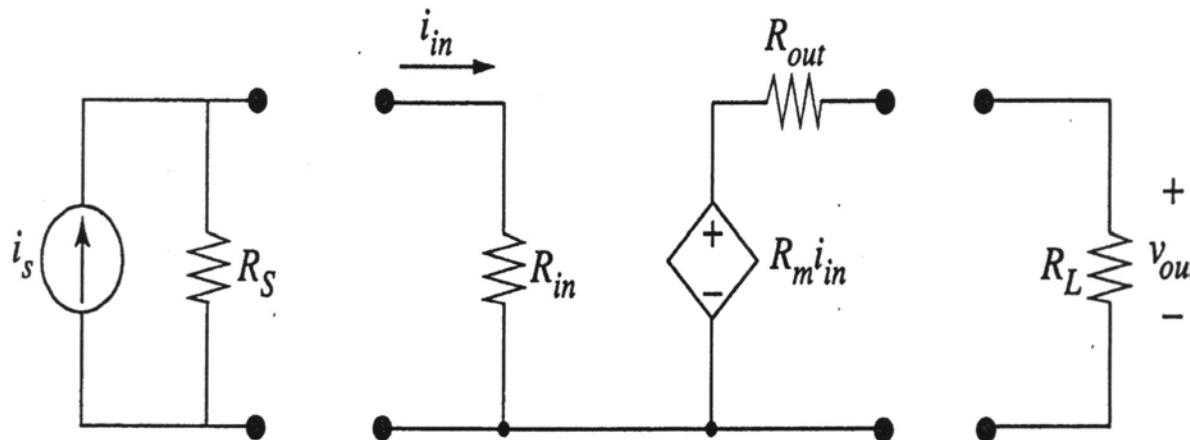Transresistance Amplifier: Current input and Voltage output



The controlled source is a Current-controlled-Voltage Source

R_m =Transresistance Gain can be found by applying a current source with $R_s=\text{infinity}$, and measuring the open circuit output voltage ($R_L=\text{infinity}$)

- Only the current i_{in} is amplified to $v_{out}=R_m i_{in}$
- Since R_s and R_{in} form a current divider that determines i_{in} , you want R_{in} as small as possible for maximum transresistance gain.
- Since R_L and R_{out} form a voltage divider that determines v_{out} , you want R_{out} as small as possible for maximum transresistance gain.

Amplifier Configurations

Input Resistance

With the load resistance attached...

Apply a test input voltage and measure the input current, $R_{in} = v_t/i_t$

Or

Apply a test input current and measure the input voltage, $R_{in} = v_t/i_t$

Output Resistance

With all input voltage sources shorted and all input current sources opened...

Apply a test voltage to the output and measure the output current, $R_{out} = v_t/i_t$

Or


Apply a test current to the output and measure the output voltage, $R_{out} = v_t/i_t$

Final Summary of Transistor Amplifier Analysis


- 1.) a.) Determine DC operating point. Make sure the transistors are biased into active mode (forward active for BJTs and Saturation for MOSFET. Do not confuse the two terms as saturation means a completely different thing for a BJT) and b.) calculate small signal parameters g_m , r_π , r_o etc...
- 2.) Convert to the AC only model.
 - DC Voltage sources are replaced with shorts to ground
 - DC Current sources are replaced with open circuits
 - Large capacitors are replaced with short circuits
 - Large inductors are replaced with open circuits
- 3.) Use a Thevenin circuit where necessary on each leg of transistor
- 4.) Replace transistor with small signal model
- 5.) Simplify the circuit as much as necessary and solve for gain.
- 6.) Solve for Input Resistance: With the load resistance attached... a.) Apply a test input voltage and measure the input current, $R_{in} = v_t/i_t$ or b.) Apply a test input current and measure the input voltage, $R_{in} = v_t/i_t$
- 7.) Solve for Output Resistance: With all input voltage sources shorted and all input current sources opened... a.) Apply a test voltage to the output and measure the output current, $R_{out} = v_t/i_t$ or b.) Apply a test current to the output and measure the output voltage, $R_{out} = v_t/i_t$

Transistor Amplifier Configurations

Common Emitter and Common Source

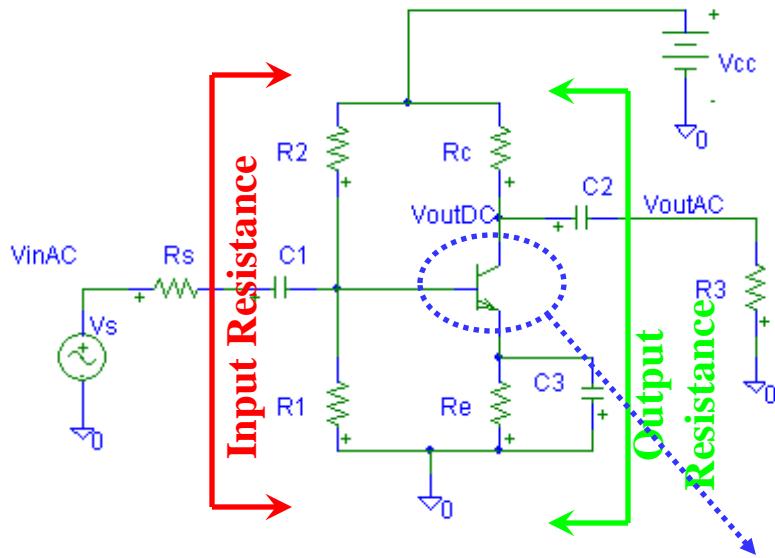

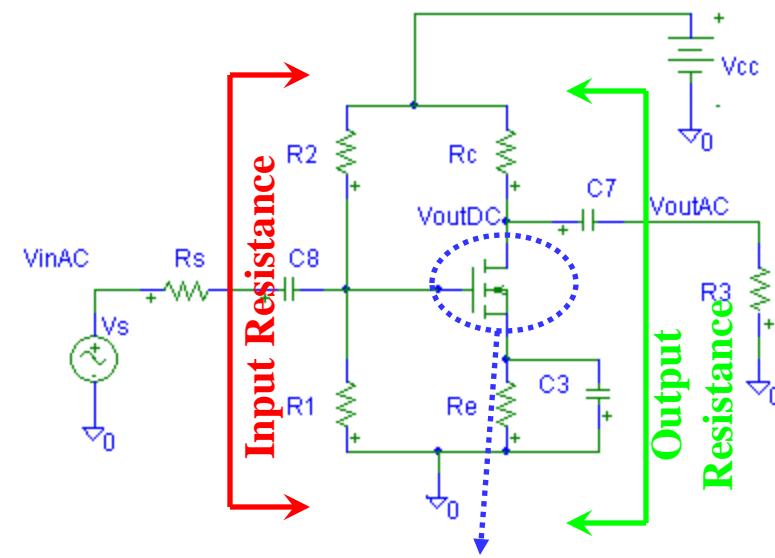Can be modeled as a current amplifier,
 $I_C = \beta I_B$, or a transconductance amplifier ,
 $i_C = K v_{BE}$




Modeled as transconductance amplifier, $i_{DS} = K v_{GS}$

Overall Amplifier Configuration

- Emitter/Source is neither an input nor an output
- Input is between base-emitter or gate-source
- Output is between collector-emitter and drain-source
- Is a transconductance amplifier (see small signal models we have used in previous examples)

Transistor Amplifier Configurations

Common Emitter and Common Source

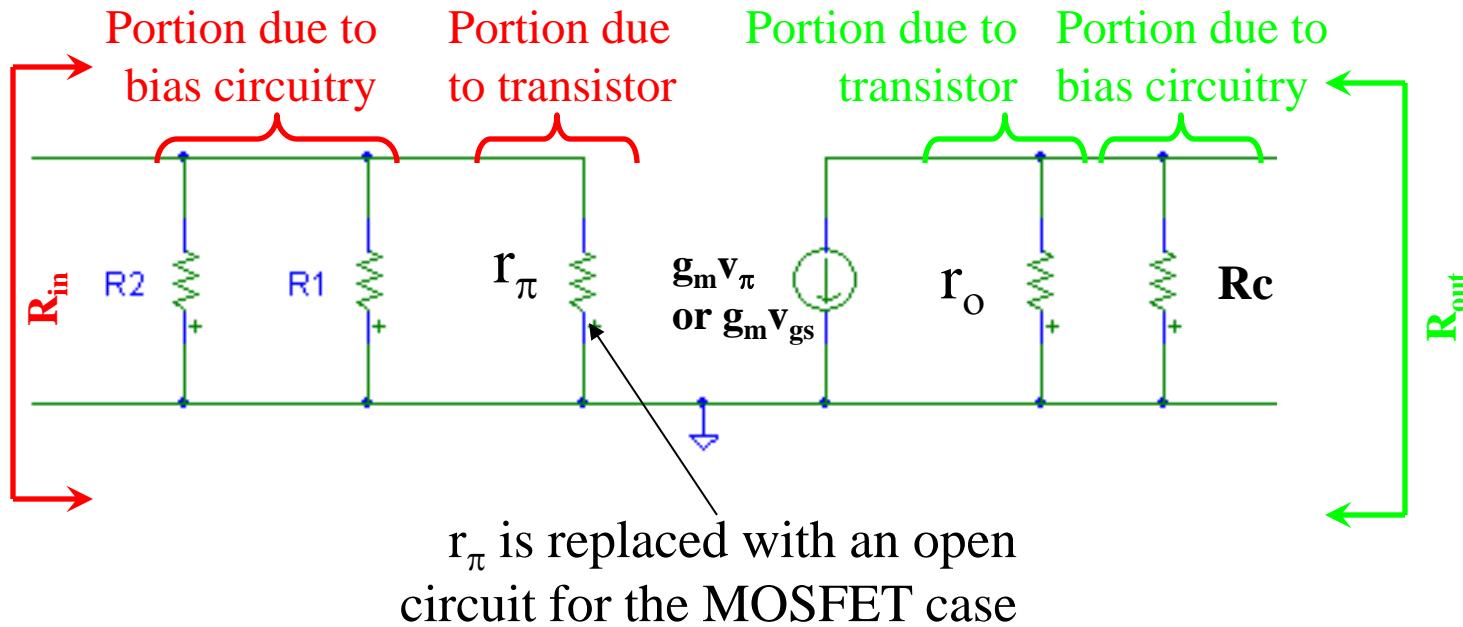

Previously, we have analyzed voltage gain. Now let us look at the amplifier input and output resistance (these are small signal parameters):

$$R_{in} = R_2 \parallel R_1 \parallel r_\pi \text{ for the BJT} \quad \text{or} \quad R_{in} = R_2 \parallel R_1 \text{ for the MOSFET}$$

$$R_{out} = r_o \parallel R_c \text{ for the BJT or MOSFET}$$

Transistor Amplifier Configurations

Summary of Common Emitter and Common Source Characteristics

- Very Large Voltage Gain
- Inverting Voltage Gain (due to $-g_m r_o$)
- High Input Impedance
- High Output Impedance



These properties make the CE/CS configuration very good for high gain stages of amplifiers.

Now let us consider the other two configurations of transistor amplifiers:

- Common Gate/Common Base
- Common Drain/Common Collector

Transistor Amplifier Configurations

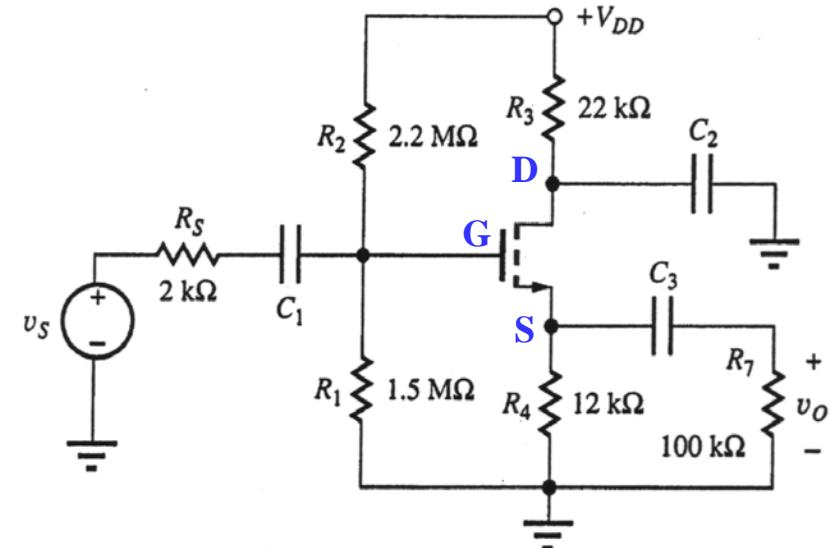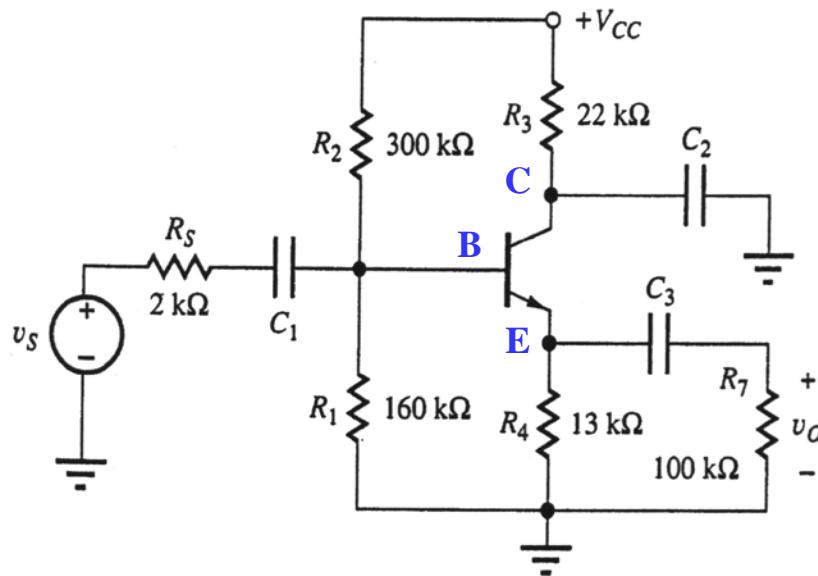Common Collector and Common Drain DC Circuit



Collector (or Drain) is neither an input or output

Input is Base (or Gate)


Output is Emitter (or Source)

Transistor Amplifier Configurations

Common Collector


DC Circuit converted to AC Equivalent (reduced)

DC
Circuit

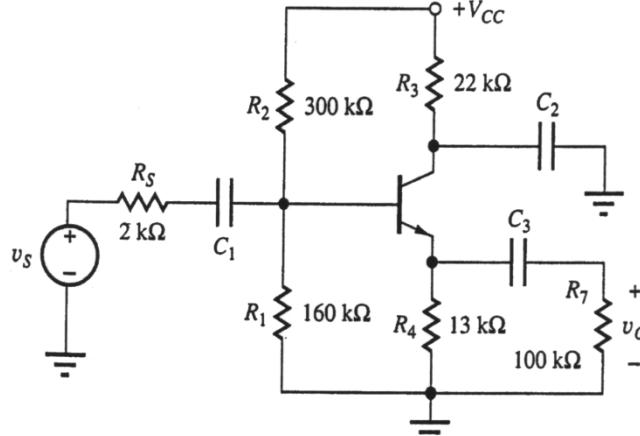

Note the extra
ground due to C_2

AC
Circuit

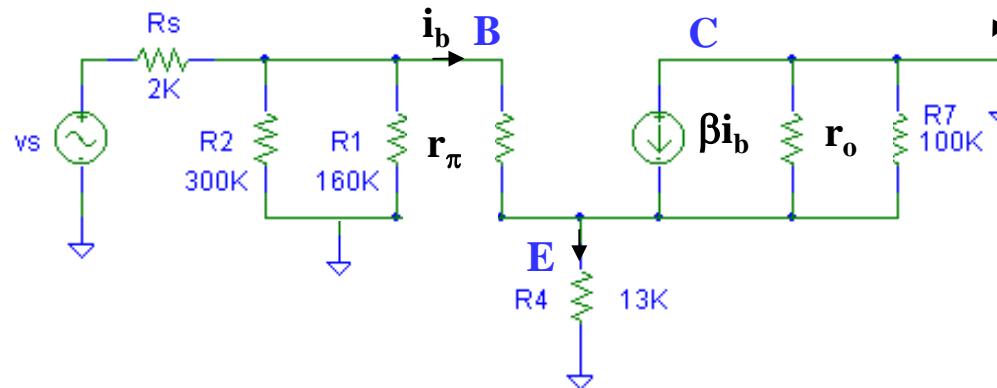


Transistor Amplifier Configurations



Common Collector

DC Circuit converted to AC Equivalent (reduced)

AC
Circuit

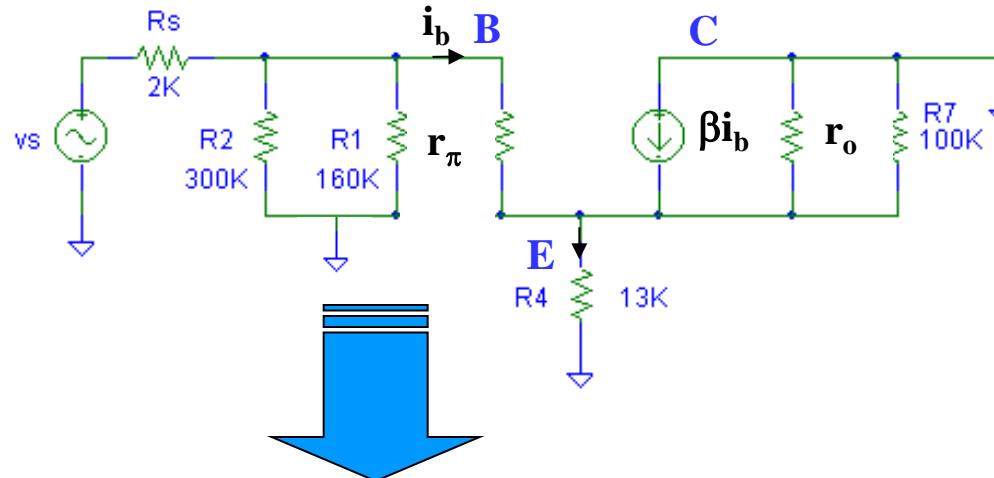

AC Circuit
(reduced)

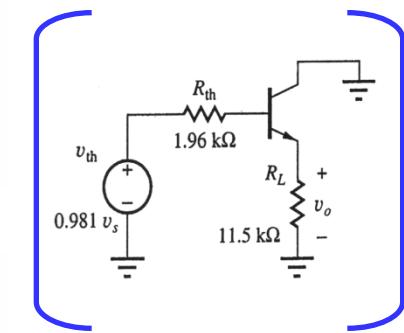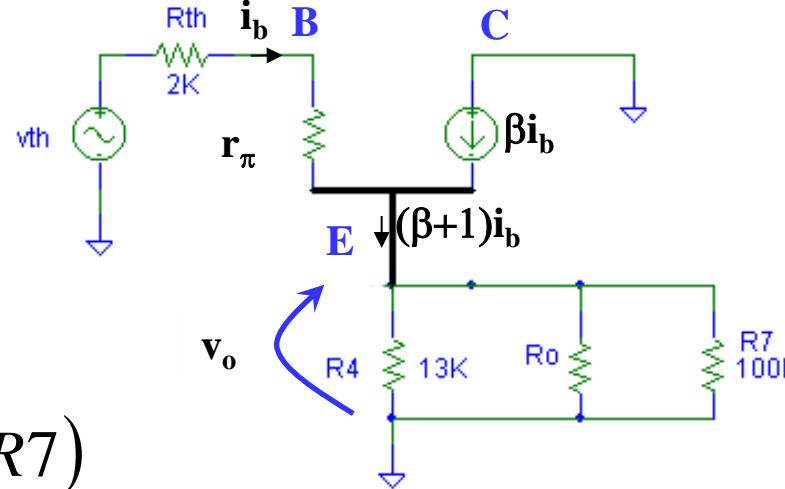

$$v_o = (\beta_o + 1)i_b (R4 \parallel r_o \parallel R7)$$

$$v_{th} = i_b (R_{th} + r_\pi + (\beta_o + 1)(R4 \parallel r_o \parallel R7))$$

Transistor Amplifier Configurations

Common Collector

AC Voltage Gain

$$v_o = (\beta_o + 1)i_b(R4 \parallel r_o \parallel R7)$$

$$v_{th} = i_b(R_{th} + r_\pi + (\beta_o + 1)(R4 \parallel r_o \parallel R7))$$

$$v_{th} = v_s \frac{R2 \parallel R1}{R2 \parallel R1 + R_s}$$

$$A_v = \frac{v_o}{v_{th}} = \left(\frac{R2 \parallel R1}{R2 \parallel R1 + R_s} \right) \left(\frac{(\beta_o + 1)i_b(R4 \parallel r_o \parallel R7)}{i_b(R_{th} + r_\pi + (\beta_o + 1)(R4 \parallel r_o \parallel R7))} \right)$$

$$A_v = \left(\frac{R2 \parallel R1}{R2 \parallel R1 + R_s} \right) \left(\frac{(\beta_o + 1)R_L}{(R_{th} + r_\pi + (\beta_o + 1)R_L)} \right) \text{ where } R_L = (R4 \parallel r_o \parallel R7)$$


multiplying numerator and denominator by $\frac{g_m}{(\beta_o + 1)}$

$$A_v = \left(\frac{R2 \parallel R1}{R2 \parallel R1 + R_s} \right) \left(\frac{g_m R_L}{g_m \left(\frac{R_{th}}{(\beta_o + 1)} + R_L \right) + \frac{g_m r_\pi}{(\beta_o + 1)}} \right)$$

$$A_v = \left(\frac{R2 \parallel R1}{R2 \parallel R1 + R_s} \right) \left(\frac{g_m R_L}{g_m \left(\frac{R_{th}}{(\beta_o + 1)} + R_L \right) + \alpha_o} \right)$$

But for $(R2 \parallel R1) \gg R_s$ and $g_m R_L \gg 1$
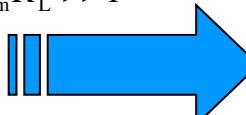
$$A_v \approx \frac{g_m R_L}{1 + g_m R_L} \approx 1 \left[\frac{V}{V} \right]$$





Gain is positive and ~ 1


Transistor Amplifier Configurations

Common Drain Conversion from DC to AC Equivalent Circuit

DC
Circuit

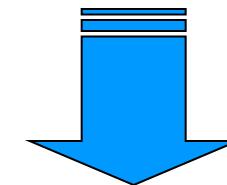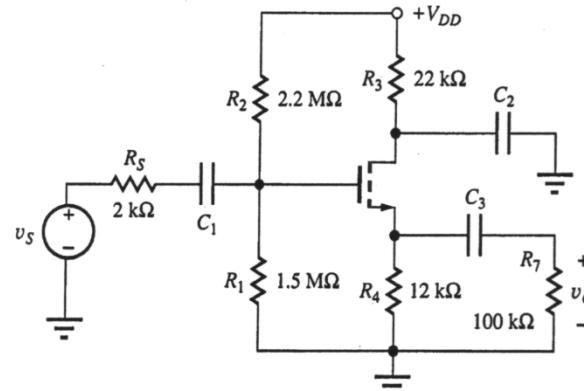

AC
Circuit

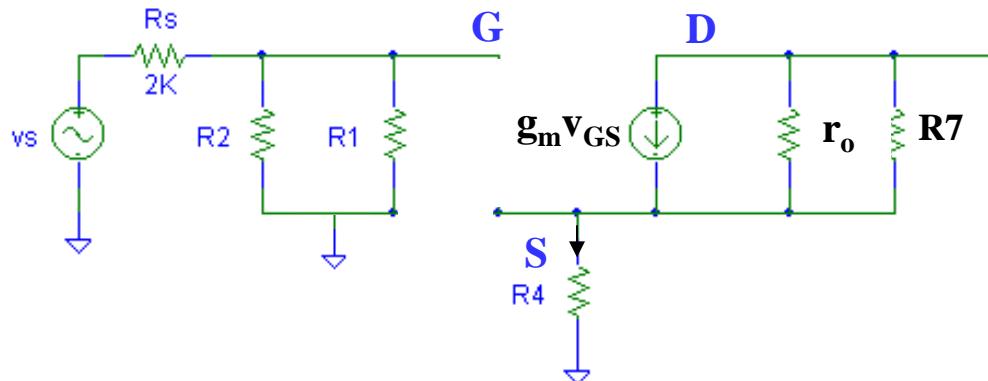


Transistor Amplifier Configurations



Common Emitter and Common Source

DC Circuit converted to AC Equivalent (reduced)

AC
Circuit

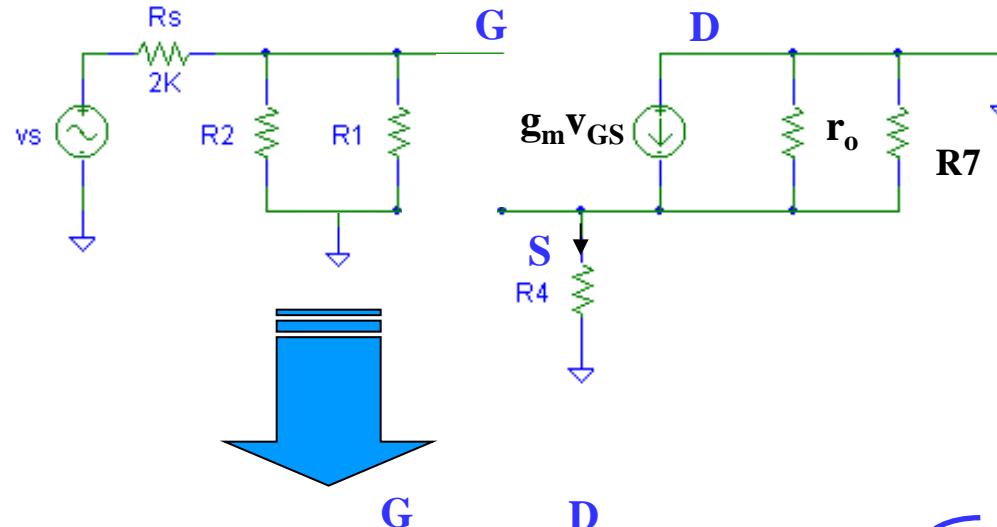

AC Circuit
(reduced)

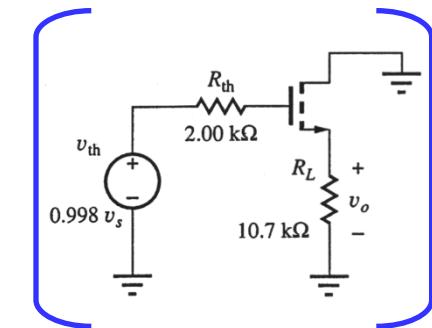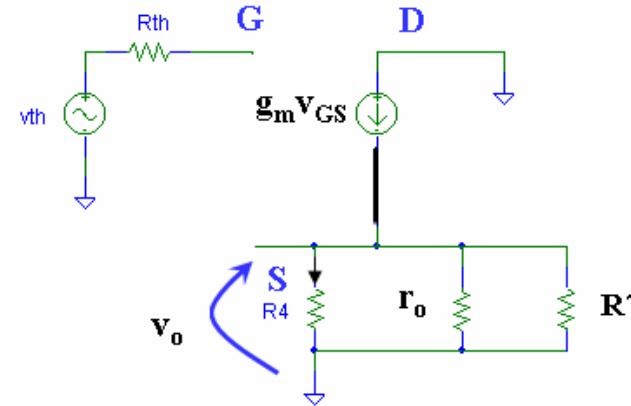

Transistor Amplifier Configurations

Common Drain AC Voltage Gain

$$v_o = g_m v_{GS} (R4 \parallel r_o \parallel R7)$$

$$v_{th} = v_{GS} + g_m v_{GS} (R4 \parallel r_o \parallel R7) = v_{GS} (1 + g_m (R4 \parallel r_o \parallel R7))$$

$$v_{th} = v_s \frac{R2 \parallel R1}{R2 \parallel R1 + R_s}$$

$$A_v = \frac{v_o}{v_{GS}} \frac{v_{GS}}{v_{th}} \frac{v_{th}}{v_s} = \left(\frac{R2 \parallel R1}{R2 \parallel R1 + R_s} \right) \left(\frac{g_m (R4 \parallel r_o \parallel R7)}{(1 + g_m (R4 \parallel r_o \parallel R7))} \right)$$

$$A_v = \left(\frac{R2 \parallel R1}{R2 \parallel R1 + R_s} \right) \left(\frac{g_m R_L}{(1 + g_m R_L)} \right) \text{ where } R_L = (R4 \parallel r_o \parallel R7)$$


But for $(R2 \parallel R1) \gg R_s$ and $g_m R_L \gg 1$

$$A_v \cong \frac{g_m R_L}{1 + g_m R_L} \cong 1 \left[\frac{V}{V} \right]$$

Gain is positive and ~ 1

Transistor Amplifier Configurations

Common Collector/Drain Input Resistance

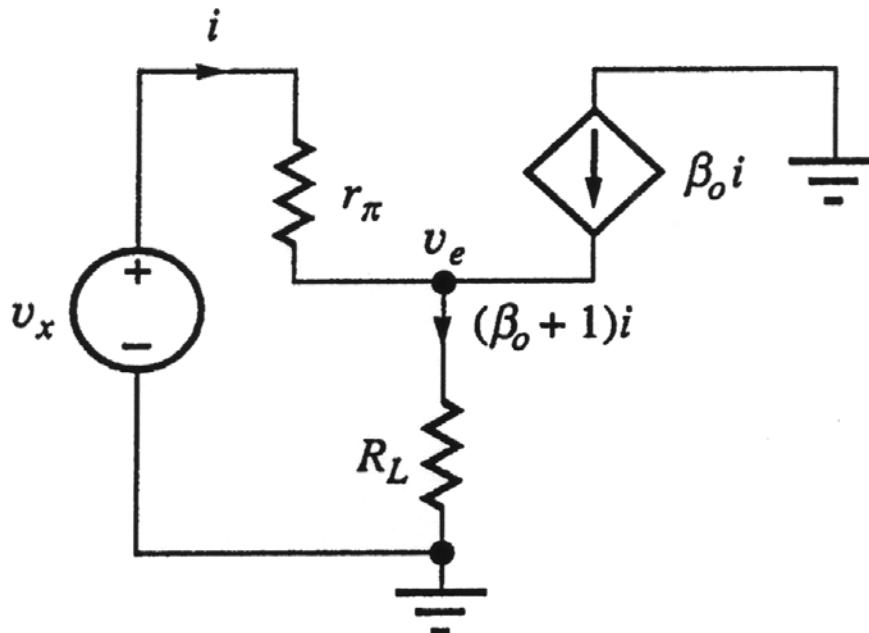

Input Resistance: With the load resistance attached apply a test input voltage and measure the input current, $R_{in} = v_x/i$ (where $i = i_x$)


$$R_{in,BJT} = \frac{v_x}{i} = r_\pi + (\beta_o + 1)R_L$$

Resistance in the emitter circuit is “multiplied” by transistor to increase the input resistance

$$R_{in,MOSFET} = \frac{v_x}{i} = \frac{v_x}{0} = \infty$$

Transistor Amplifier Configurations

Common Collector Output Resistance

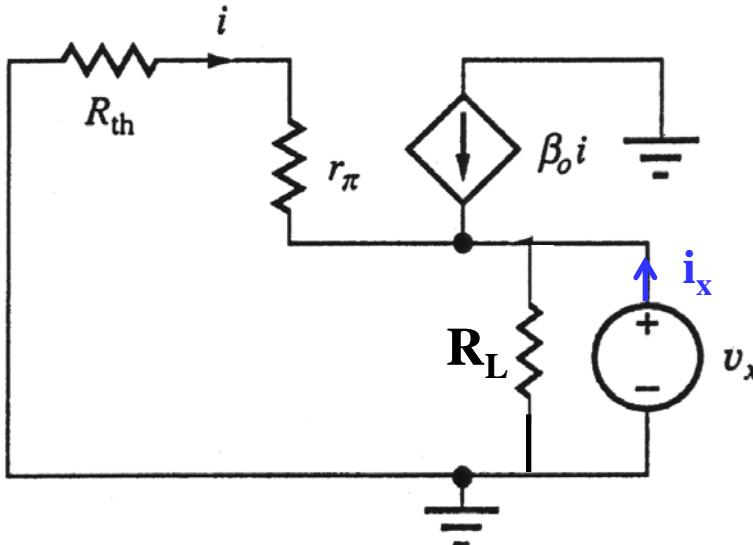

Output Resistance: With all input voltage sources shorted and all input current sources opened, apply a test voltage to the output and measure the output current, $R_{out} = v_x / i_x$


$$i_x = -i - \beta_o i + \frac{v_x}{R_L} = \frac{v_x}{r_\pi + R_{th}} - \beta_o i + \frac{v_x}{r_o} = \frac{v_x}{r_\pi + R_{th}} - \beta_o \left(-\frac{v_x}{r_\pi + R_{th}} \right) + \frac{v_x}{R_L}$$

$$R_{out,BJT} = \frac{v_x}{i_x} = \frac{1}{\frac{1}{r_\pi + R_{th}} + \frac{1}{R_L}} \quad \text{where } R_L = r_o \parallel R_4$$

Two resistors in parallel: R_L , and Resistance in the base circuit is “multiplied” by transistor to decrease the output resistance

Transistor Amplifier Configurations

Common Drain Output Resistance

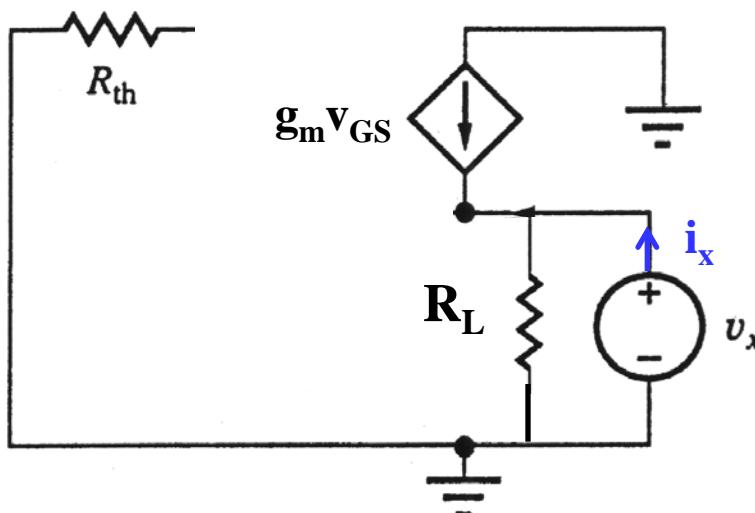

Output Resistance: With all input voltage sources shorted and all input current sources opened, apply a test voltage to the output and measure the output current, $R_{out} = v_x/i$

$$i_x = -g_m v_{GS} + \frac{v_x}{r_o} = g_m v_x + \frac{v_x}{R_L}$$

$$R_{out,MOSFET} = \frac{v_x}{i_x} = \frac{1}{g_m + \frac{1}{R_L}} \quad \text{where } R_L = r_o \parallel R_4$$

Two resistors in parallel: R_L and inverse transconductance

Transistor Amplifier Configurations


Summary of Common Collector and Common Drain Characteristics

- Unity Voltage Gain
- Non-Inverting Voltage Gain
- Very High Input Impedance
- Low Output Impedance

These properties make the CC/CD configuration very good for impedance transformation, I.E. “buffering” high impedances to low impedances. CC/CD configurations are good for output stages of amplifiers due to their very low output impedance, I.E., very little voltage drop in the output resistance of the amp.

Transistor Amplifier Configurations

Common Collector/Drain Current Gain

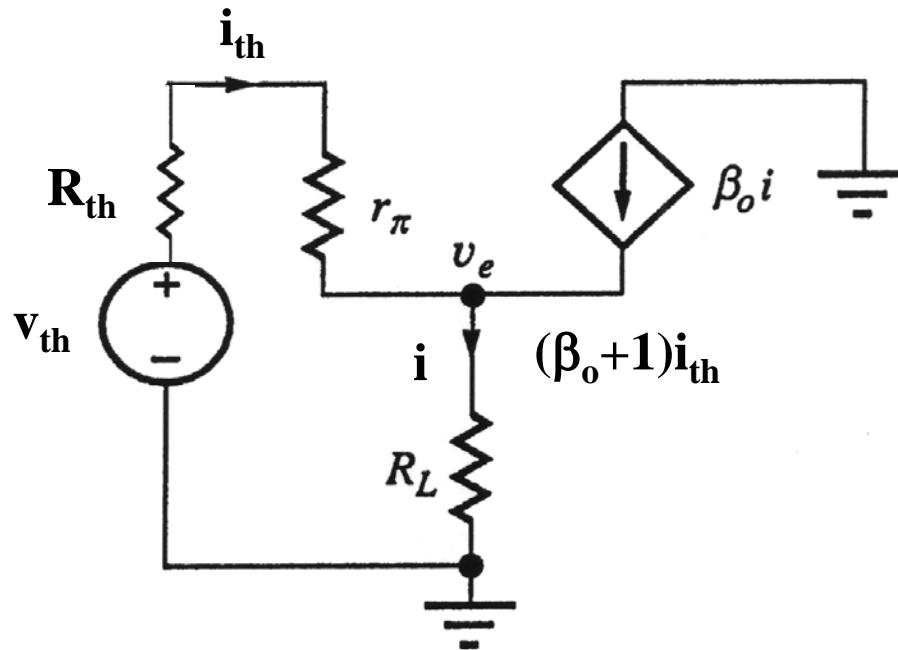



$$A_{i, BJT} = \frac{i}{i_{th}} = \beta_o + 1$$

$$A_{i, MOSFET} = \frac{i}{i_{th}} = \infty$$

Note: since R7 was originally defined as the load, the current gain should actually be $(\beta+1) (R4||r_o)/(R4||r_o+R7)$ using a current divider.

Transistor Amplifier Configurations

Common Base and Common Gate DC Circuit

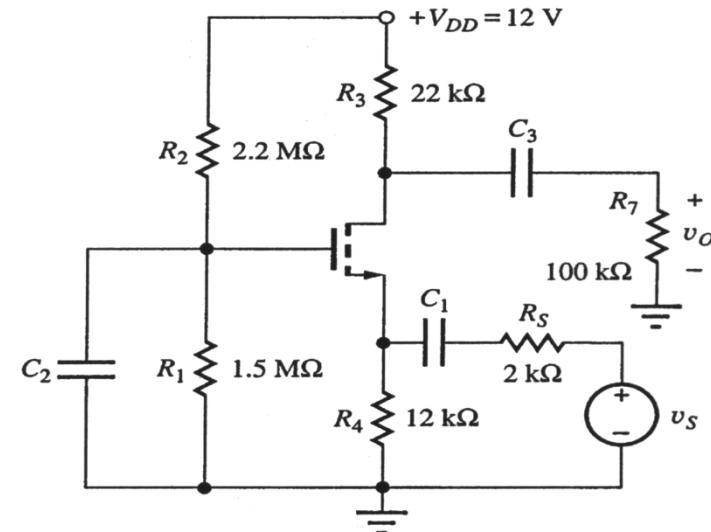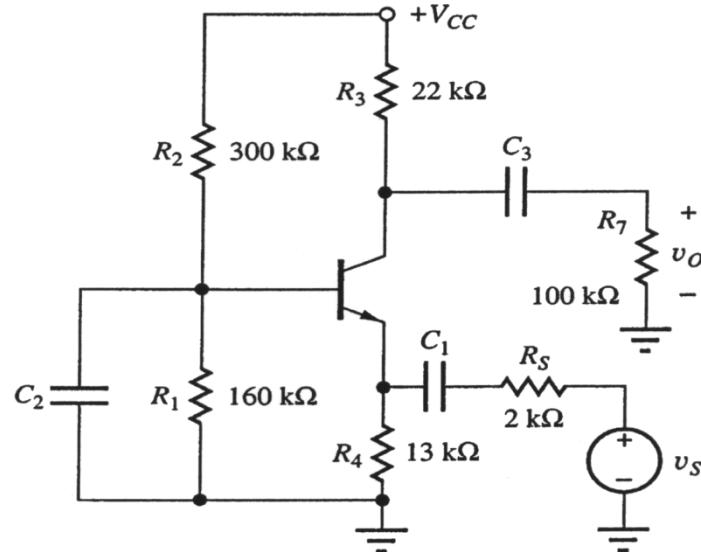

Base (or Gate) is neither an input or output

Input is Emitter (or Source)

Output is Collector (or Drain)

Optional



DC Circuit

AC Circuit


Transistor Amplifier Configurations

Common Base

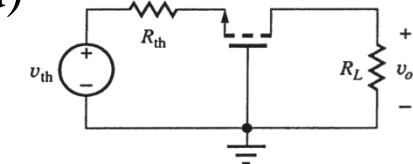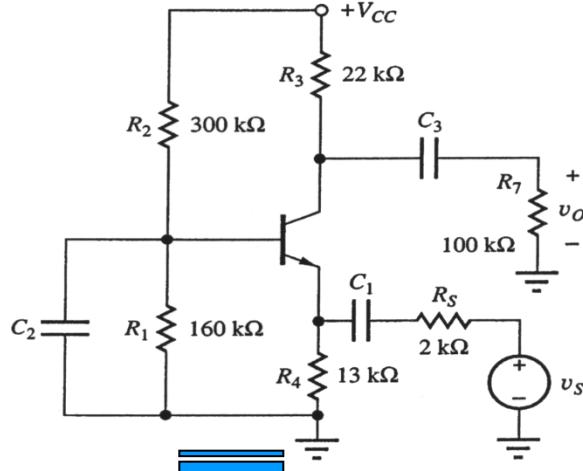DC Circuit converted to AC Equivalent (reduced)



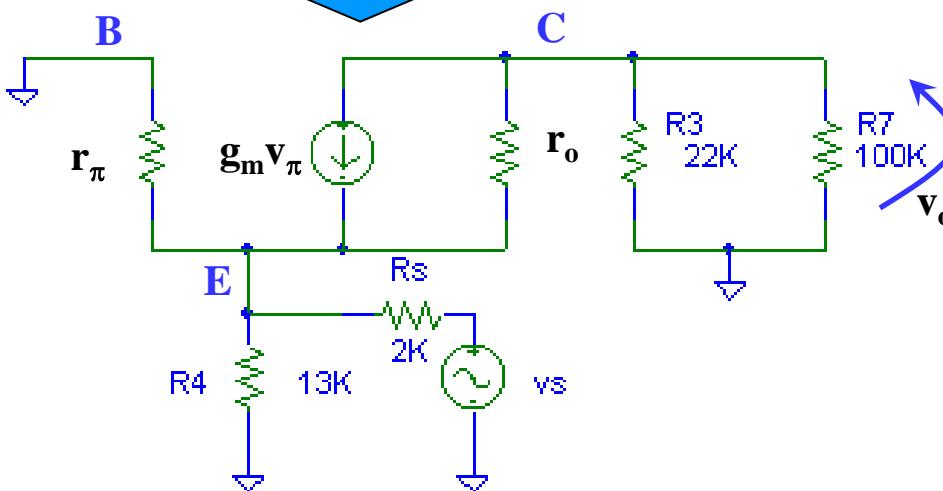Note: Jaeger let's r_o go to infinity which makes the math dramatically easier




AC Circuit


Optional

Transistor Amplifier Configurations

Common Base AC Equivalent (reduced)

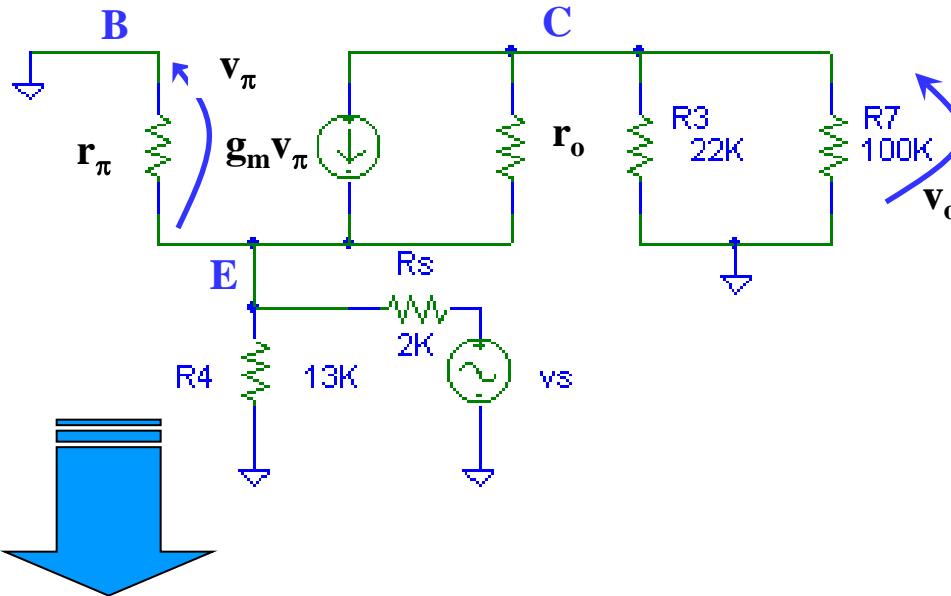

AC
Circuit
(reduced)

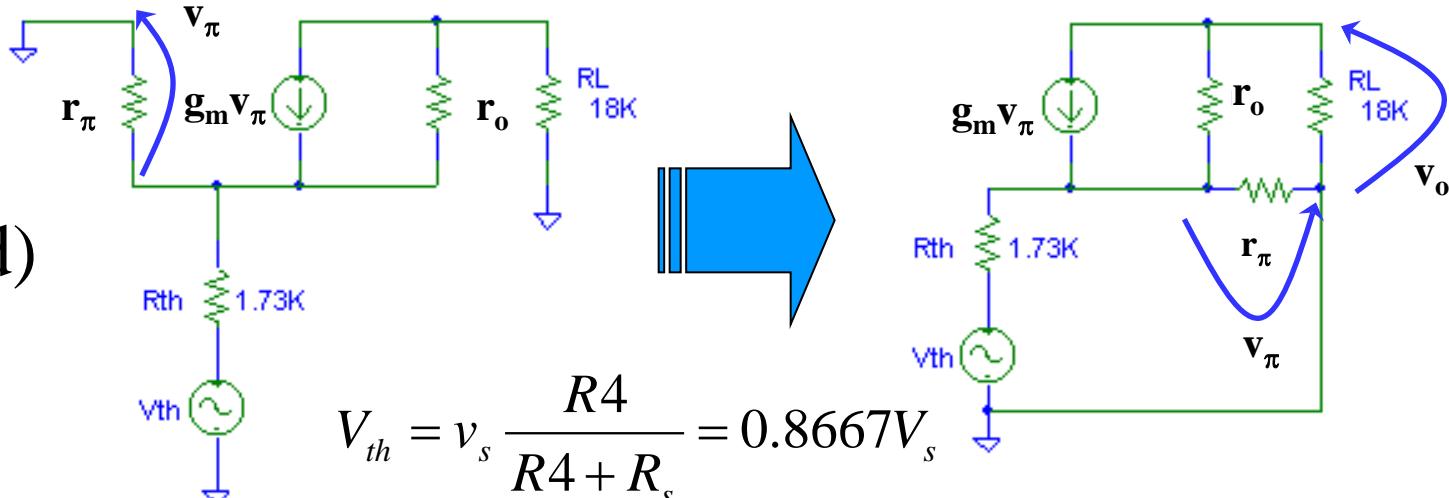


$$V_{th} = v_s \frac{R_4}{R_4 + R_s} = 0.8667 V_s$$

$$R_{th} = R_s \parallel R_4 = 1.73K$$

Optional

Transistor Amplifier Configurations

Common Base Voltage Gain

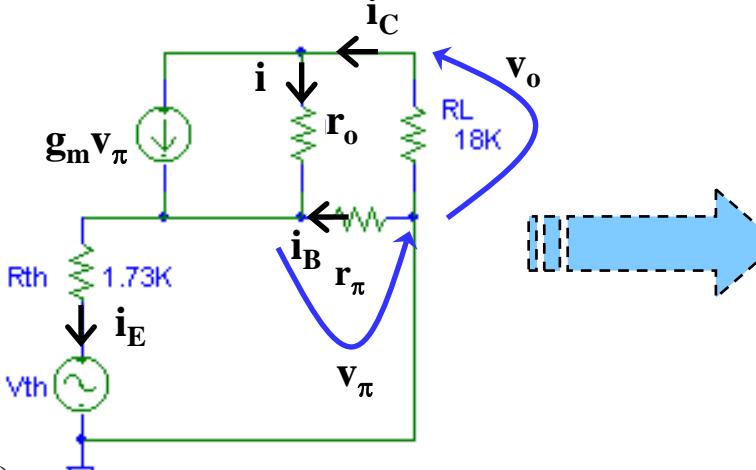

$$i_E = i_C + i_B = g_m v_\pi + i + i_B$$

$$i_E = g_m v_\pi + \left(\frac{v_\pi + v_o}{r_o} \right) + \left(\frac{v_\pi}{r_\pi} \right)$$

$$v_{th} = -i_E R_{th} - i_B r_\pi$$

$$-v_{th} = \left(g_m v_\pi + \left(\frac{v_\pi + v_o}{r_o} \right) + \left(\frac{v_\pi}{r_\pi} \right) \right) R_{th} + \left(\frac{v_\pi}{r_\pi} \right) r_\pi$$

also,

$$v_o = -i_C R_L = -\left(g_m v_\pi + \left(\frac{v_\pi + v_o}{r_o} \right) \right) R_L \quad so, \quad v_o = -v_\pi \left(\frac{g_m + \frac{1}{r_o}}{1 + \frac{R_L}{r_o}} \right) R_L$$

$$-v_{th} = g_m v_\pi + \left(\frac{v_\pi - v_\pi \left(\frac{g_m + \frac{1}{r_o}}{1 + \frac{R_L}{r_o}} \right) R_L}{r_o} \right) + \left(\frac{v_\pi}{r_\pi} \right) R_{th} + v_\pi$$

$$V_{th} = v_s \frac{R4}{R4 + R_s} = 0.8667 V_s$$

$$R_{th} = R_s \parallel R4 = 1.73K$$

Transistor Amplifier Configurations

Common Base Voltage Gain

Optional

$$\begin{aligned}
 -v_{th} &= g_m v_\pi + \left(v_\pi - v_\pi \left(\frac{g_m + \frac{1}{r_o}}{1 + \frac{R_L}{r_o}} \right) R_L \right) + \left(\frac{v_\pi}{r_\pi} \right) R_{th} + v_\pi \quad \Rightarrow \quad -v_{th} = v_\pi \left[g_m + \left(1 - \frac{\left(g_m + \frac{1}{r_o} \right) R_L}{1 + \frac{R_L}{r_o}} \right) \frac{1}{r_o} + \left(\frac{1}{r_\pi} \right) R_{th} + 1 \right] \\
 A_v &= \frac{v_o}{v_\pi} \frac{v_\pi}{v_{th}} \frac{v_{th}}{v_s} = - \left(\frac{g_m + \frac{1}{r_o}}{1 + \frac{R_L}{r_o}} \right) R_L \frac{-1}{\left[g_m + \left(1 - \frac{\left(g_m + \frac{1}{r_o} \right) R_L}{1 + \frac{R_L}{r_o}} \right) \frac{1}{r_o} + \left(\frac{1}{r_\pi} \right) R_{th} + 1 \right]} \left(\frac{R_4}{R_4 + R_s} \right)
 \end{aligned}$$

for $r_o \rightarrow \infty$ and $R_4 \gg R_s$

$$A_v = \frac{v_o}{v_\pi} \frac{v_\pi}{v_{th}} \frac{v_{th}}{v_s} = \frac{g_m R_L}{\left[g_m R_{th} + \left(\frac{R_{th}}{r_\pi} \right) + 1 \right]}$$

Thus,

Optional

Transistor Amplifier Configurations

Common Base Voltage Gain

$$A_v = \frac{g_m R_L}{\left[g_m R_{th} + \left(\frac{R_{th}}{r_\pi} \right) + 1 \right]}$$

$$A_v = \frac{g_m R_L}{\left[R_{th} \left(g_m + \frac{1}{r_\pi} \right) + 1 \right]}$$

$$A_v = \frac{g_m R_L}{\left[R_{th} \left(g_m \frac{g_m r_\pi}{g_m r_\pi} + \frac{1}{r_\pi} \frac{g_m}{g_m} \right) + 1 \right]}$$

$$A_v = \frac{g_m R_L}{\left[R_{th} \left(\frac{g_m}{g_m r_\pi} (g_m r_\pi + 1) \right) + 1 \right]}$$

$$A_v = \frac{g_m R_L}{\left[R_{th} \left(\frac{g_m}{\beta_o} (\beta_o + 1) \right) + 1 \right]} \Rightarrow \text{Large } \beta_o$$

$$A_v = \frac{g_m R_L}{1 + R_{th} g_m}$$




Gain is positive and can be large

Optional

Transistor Amplifier Configurations

Common Base Input Resistance

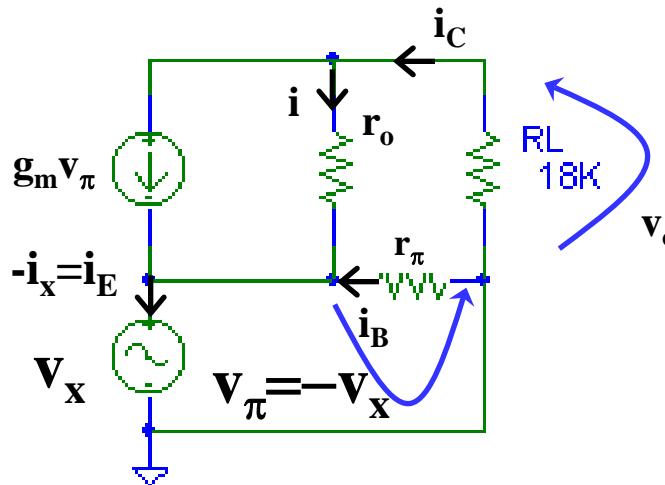

Input Resistance: With the load resistance attached apply a test input voltage and measure the input current, $R_{in} = v_x/i$

From before,

$$i_E = g_m v_\pi + \left(\frac{v_\pi + v_o}{r_o} \right) + \left(\frac{v_\pi}{r_\pi} \right) \quad \text{and}, \quad v_o = -v_\pi \left(\frac{g_m + \frac{1}{r_o}}{1 + \frac{R_L}{r_o}} \right) R_L$$

$$i_x = -i_E \quad \text{and} \quad v_x = -v_\pi$$

$$i_x = g_m v_x + \left(\frac{v_x - v_o}{r_o} \right) + \left(\frac{v_x}{r_\pi} \right) \quad \text{and}, \quad v_o = v_x \left(\frac{g_m + \frac{1}{r_o}}{1 + \frac{R_L}{r_o}} \right) R_L$$

Transistor Amplifier Configurations

Optional

Common Base Input Resistance

$$i_x = g_m v_x + \left(\frac{v_x - v_x \left(\frac{g_m + \frac{1}{r_o}}{1 + \frac{R_L}{r_o}} R_L \right)}{r_o} \right) + \left(\frac{v_x}{r_\pi} \right)$$

$$i_x = v_x \left[g_m + \left(\frac{1 - \left(\frac{g_m + \frac{1}{r_o}}{1 + \frac{R_L}{r_o}} R_L \right)}{r_o} \right) + \left(\frac{1}{r_\pi} \right) \right]$$

$$R_{in,BJT} = \frac{v_x}{i_x} = \frac{1}{g_m + \left(\frac{1 - \left(\frac{g_m + \frac{1}{r_o}}{1 + \frac{R_L}{r_o}} R_L \right)}{r_o} \right) + \left(\frac{1}{r_\pi} \right)}$$

Letting $r_o \rightarrow \infty$

$$R_{in,BJT} = \frac{v_x}{i_x} = \frac{1}{g_m + \left(\frac{1}{r_\pi} \right)}$$

$$R_{in,BJT} = \frac{r_\pi}{g_m r_\pi + 1}$$

$$= \frac{r_\pi}{\beta_o + 1} \frac{\beta_o}{\beta_o}$$


$$= \frac{\alpha_o}{g_m} \approx \frac{1}{g_m}$$

Input Resistance is very small!

Optional

Transistor Amplifier Configurations

Common Base Output Resistance

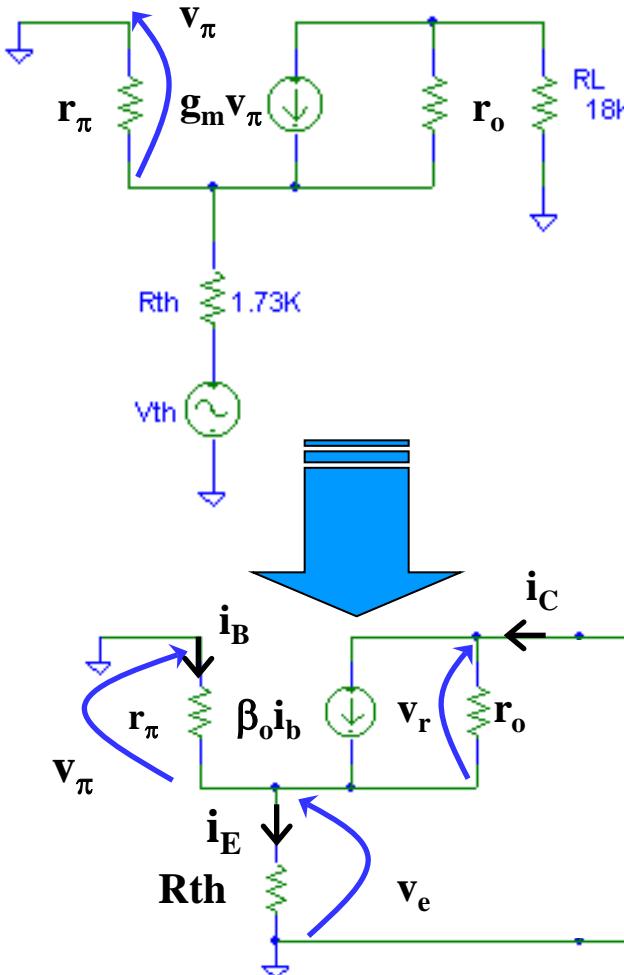

Replace R_L by a voltage source, v_x

Result follows exactly after discussion in Jaeger, pages 668-670, and 683-684.

Optional

Transistor Amplifier Configurations

Common Base Output Resistance

$$\begin{aligned} v_x &= v_r + v_e \\ &= (i_x - \beta_o i_b) r_o + v_e \end{aligned}$$

but,


$$v_e = i_x [r_\pi \parallel R_{th}] = i_x \frac{r_\pi R_{th}}{r_\pi + R_{th}}$$

$$i_b = -i_x \frac{R_{th}}{r_\pi + R_{th}} \quad \text{thus,}$$

$$v_x = i_x r_o - \beta_o \left(-i_x \frac{R_{th}}{r_\pi + R_{th}} \right) r_o + i_x \frac{r_\pi R_{th}}{r_\pi + R_{th}}$$

$$\therefore R_{out,BJT} = \frac{v_x}{i_x} = r_o + \beta_o \left(\frac{R_{th}}{r_\pi + R_{th}} \right) r_o + \frac{r_\pi R_{th}}{r_\pi + R_{th}}$$

Very Large Even Larger

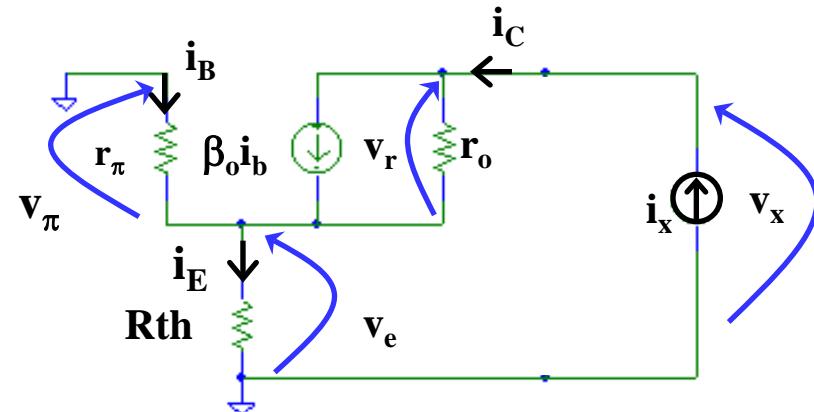


Output Resistance is HUGE!

Transistor Amplifier Configurations

Common Base Current Gain

Optional

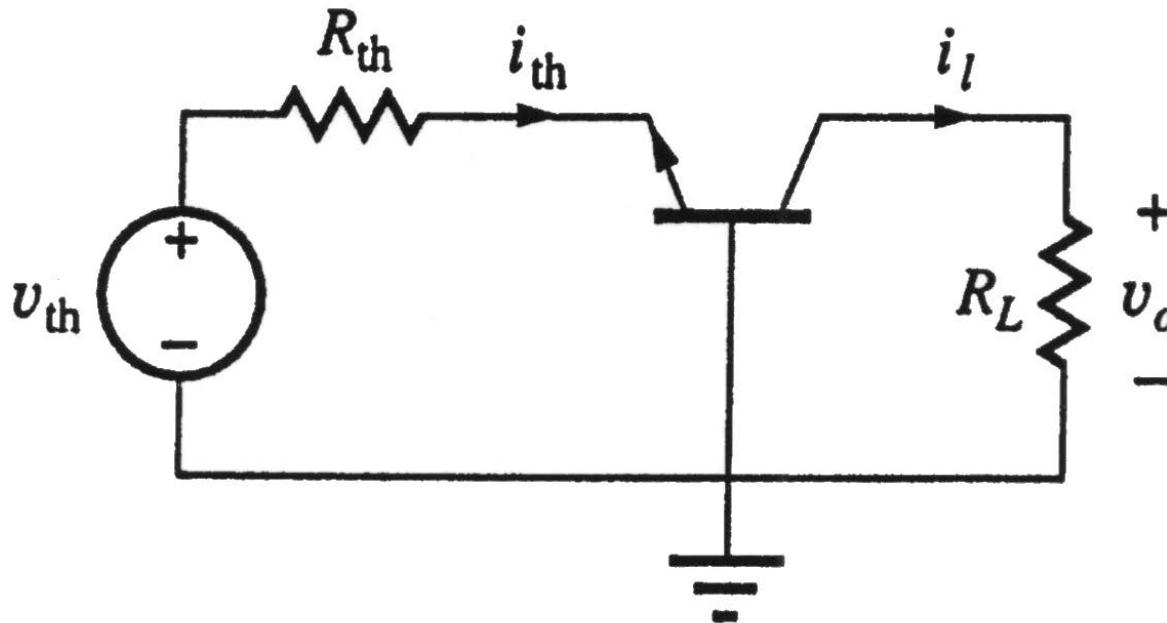

$$A_i = \frac{i_l}{i_{th}} = \alpha_o \approx 1$$

Optional

Transistor Amplifier Configurations

Common Gate Solution

The Common Gate solution can be found by recognizing that the following translations can be made in our small signal model:

$$\beta_o \rightarrow \infty \Rightarrow \alpha_o \rightarrow 1$$

$$r_\pi \rightarrow \infty$$

$$A_{v,BJT} = \frac{g_m R_L}{\left[g_m R_{th} + \left(\frac{R_{th}}{r_\pi} \right) + 1 \right]} \rightarrow A_{v,MOSFET} = \frac{g_m R_L}{g_m R_{th} + 1}$$

$$R_{in,BJT} = \frac{1}{g_m + \left(\frac{1}{r_\pi} \right)} \rightarrow R_{in,MOSFET} = \frac{1}{g_m}$$

$$R_{out,BJT} = r_o + \beta_o \left(\frac{R_{th}}{r_\pi + R_{th}} \right) r_o + \frac{r_\pi R_{th}}{r_\pi + R_{th}} = r_o + g_m r_\pi \left(\frac{R_{th}}{r_\pi + R_{th}} \right) r_o + \frac{r_\pi R_{th}}{r_\pi + R_{th}} \rightarrow R_{out,MOSFET} = r_o (1 + g_m R_{th}) + R_{th}$$

$$A_{i,BJT} = \alpha_o \approx 1 \rightarrow A_{i,BJT} = \alpha_o = 1$$

Transistor Amplifier Configurations


Summary of Common Base and Common Gate Characteristics

- High Voltage Gain
- Non-Inverting Voltage Gain
- Very Low Input Impedance
- Very High Output Impedance

The input and output impedances are the opposite of what is typically needed for a voltage amplifier. Thus, Common Emitter/Source amplifiers are normally used instead of Common Base/Gate. The input and output impedances are useful for current amplifiers but the current gain is at best unity. Thus a current buffer is one useful application for the Common Base/Gate


Multistage Amplifier Configurations

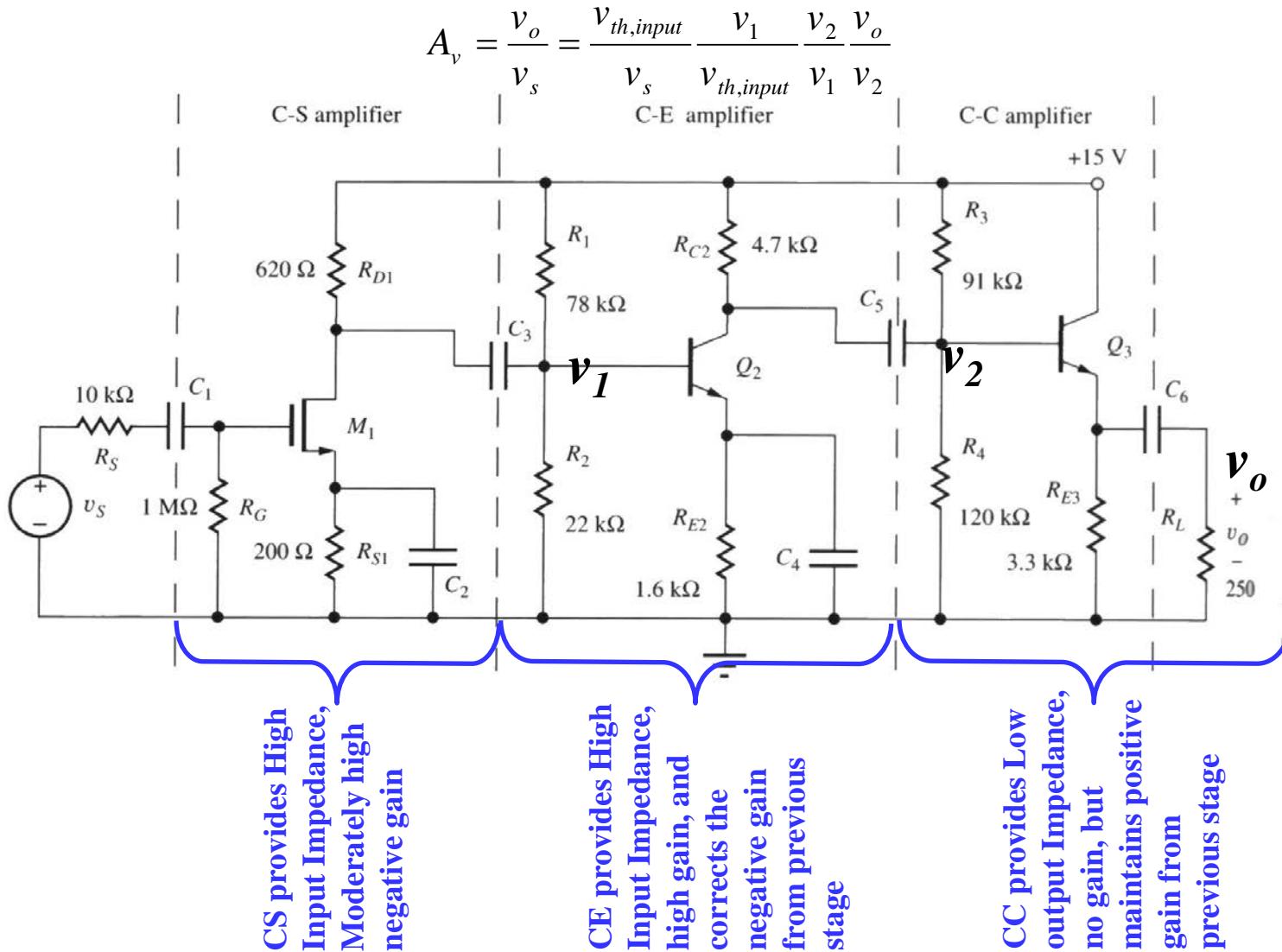You can combine or *Cascade* configurations to produce “High Performance” amplifiers with High input impedance, low output impedance and huge voltage gains.




Multistage Amplifier Configurations

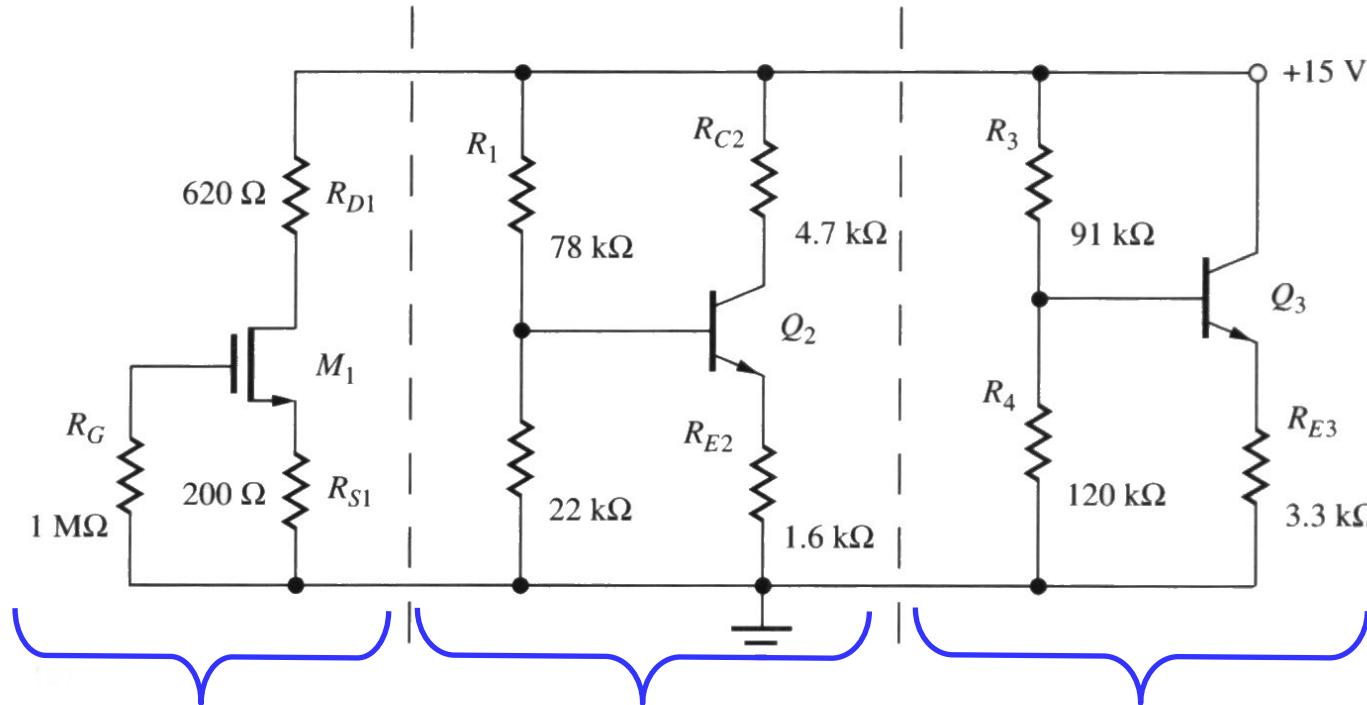For **AC-Coupled** amplifiers (capacitors between stages), the DC solution reduces to three parallel and independent circuits!





Multistage Amplifier Configurations

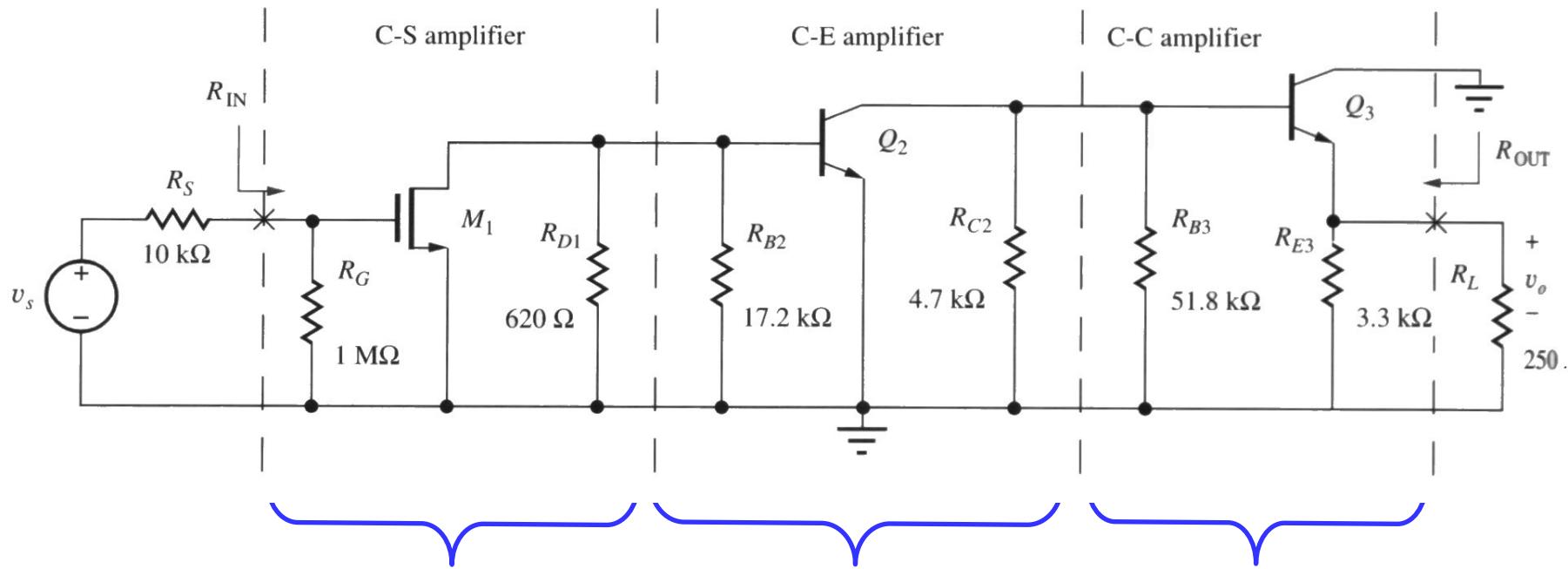For **AC-Coupled** amplifiers (capacitors between stages), the AC solution reduces to three circuits, each of which has a load dependent on the input resistance of the next stage!
Continued....




Multistage Amplifier Configurations

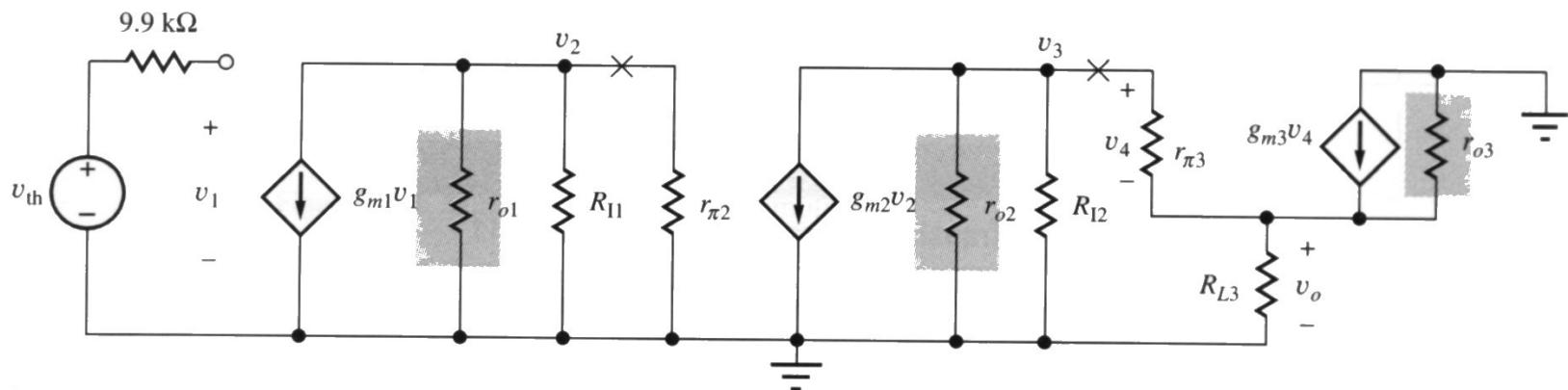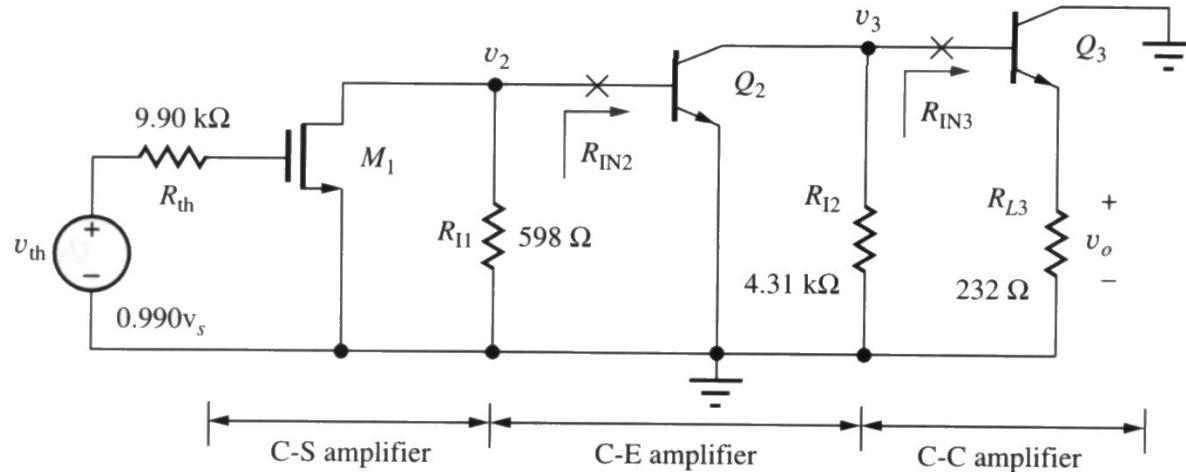Continued....(For **AC-Coupled** amplifiers (capacitors between stages), the AC solution reduces to three circuits, each of which has a load dependent on the input resistance of the next stage!)



Multistage Amplifier Configurations

Continued...

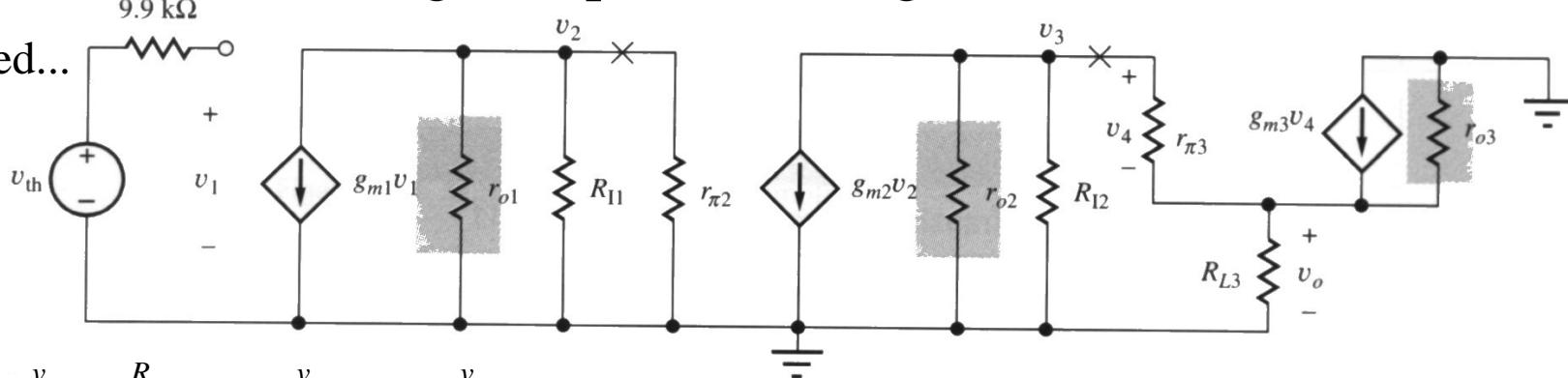

$$\frac{v_{th}}{v_s} = \frac{R_G}{R_S + R_G} - \frac{v_1}{v_{th}} = 1 \quad \frac{v_2}{v_1} = -g_{m1}(r_{o1} \parallel R_{11} \parallel r_{\pi2})$$

$$\frac{v_3}{v_2} = -g_{m2}(r_{o2} \parallel R_{12} \parallel R_{inQ4})$$

We just found this!

$$\frac{v_3}{v_2} = -g_{m2}(r_{o2} \parallel R_{12} \parallel (r_{\pi3} + (\beta + 1)(r_{o3} \parallel R_{L3})))$$

$$v_3 = v_o + v_4$$

$$v_o = v_4 \left(\frac{1}{r_{\pi3}} + g_{m3} \right) (r_{o3} \parallel R_{L3})$$


$$v_o = (v_3 - v_o) \left(\frac{1}{r_{\pi3}} + g_{m3} \right) (r_{o3} \parallel R_{L3})$$

$$\frac{v_o}{v_3} = \frac{\left(\frac{1}{r_{\pi3}} + g_{m3} \right) (r_{o3} \parallel R_{L3})}{1 + \left(\frac{1}{r_{\pi3}} + g_{m3} \right) (r_{o3} \parallel R_{L3})}$$

$$A_v = \frac{v_o}{v_s} = \frac{v_{th}}{v_s} \frac{v_1}{v_{th}} \frac{v_2}{v_1} \frac{v_3}{v_2} \frac{v_o}{v_3} = (1) (-g_{m1}(r_{o1} \parallel R_{11} \parallel r_{\pi2})) (-g_{m2}(r_{o2} \parallel R_{12} \parallel (r_{\pi3} + (\beta + 1)R_{L3}))) \left(\frac{\left(\frac{1}{r_{\pi3}} + g_{m3} \right) (r_{o3} \parallel R_{L3})}{1 + \left(\frac{1}{r_{\pi3}} + g_{m3} \right) (r_{o3} \parallel R_{L3})} \right)$$

Multistage Amplifier Configurations

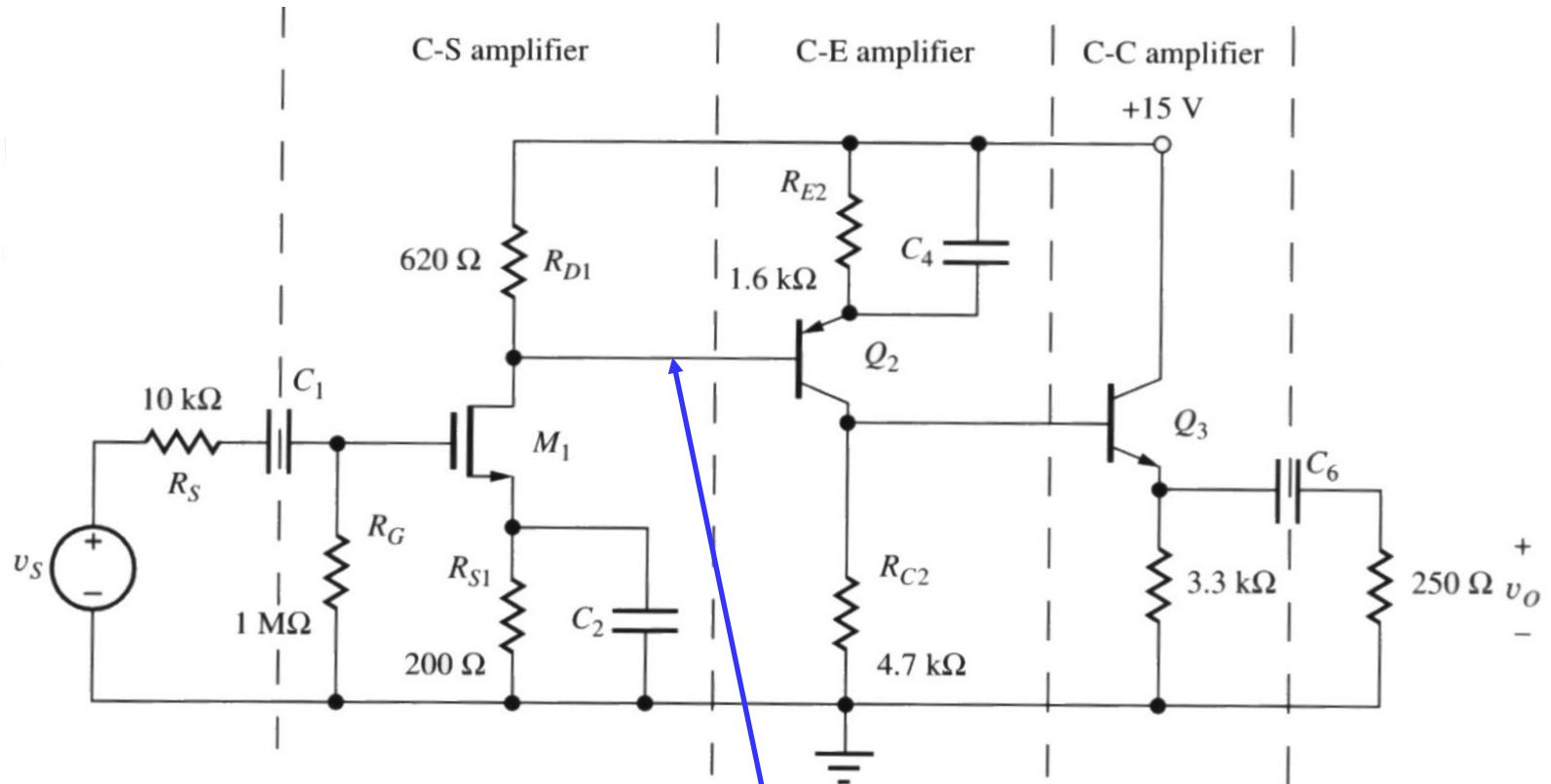AC-Coupled amplifiers (capacitors between stages), have one major limitation. They do not amplify low frequencies or DC voltages. To accomplish this, we must **DC-Couple** the stages as shown. Note: for this to be a DC coupled amp, C1 and C6 should also be replaced as shorts.



Since the bias here is usually $\sim(2/3)V_{cc}$ ($V_{cc} = 15\text{ V}$ in this example), it is easier to use a PNP for the second stage so that $V_{EB} + I_E R_{E2} \sim (2/3)V_{cc}$