

Lecture 28


Operational Amplifiers

Reading: Jaeger 11.1-11.5 and Notes


Operational Amplifier

- Operational Amplifier or “Op-Amp” is a multistage amplifier that is used for general electrical signal manipulation.
- The numbers of applications possible with Op-amps are two numerous to list.
- Most everyone agrees: “Op-Amp analysis is significantly easier than transistor analysis.”
- Though they are often internally complex, their use in circuits most often simplifies the overall design.
- The circuit is modeled by an ideal voltage amplifier.

Circuit Symbol

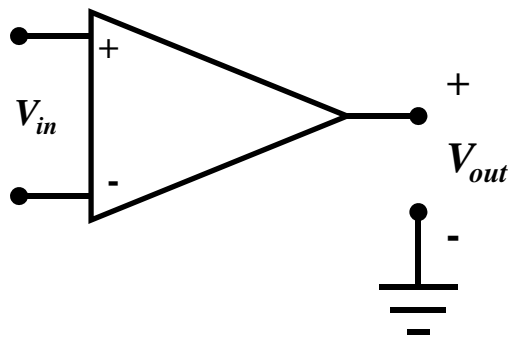


Model

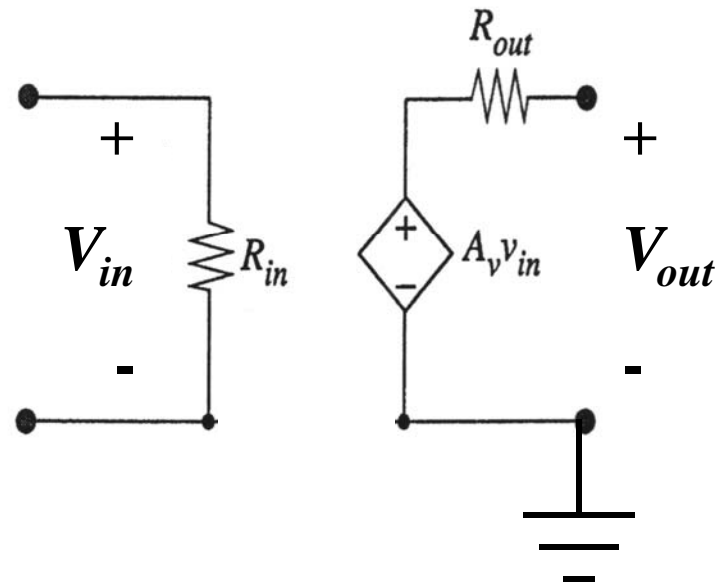

Ideal Operational Amplifier

- $R_{in} = \text{Infinity}$,
- Voltage Gain, $A_v = \text{Infinity}$ at all frequencies
- $R_{out} = 0$

Model

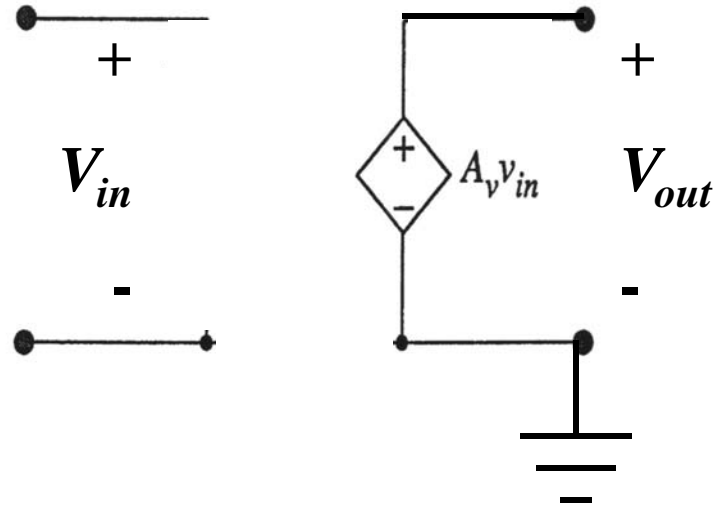


Ideal Operational Amplifier

- Infinite gain means that the device is useless without adding “Feedback” to control the overall gain to a finite value.

- Consider the circuit to the right with $v_{in}=0$

$$v_{out} = A_v (v_+ - v_-)$$

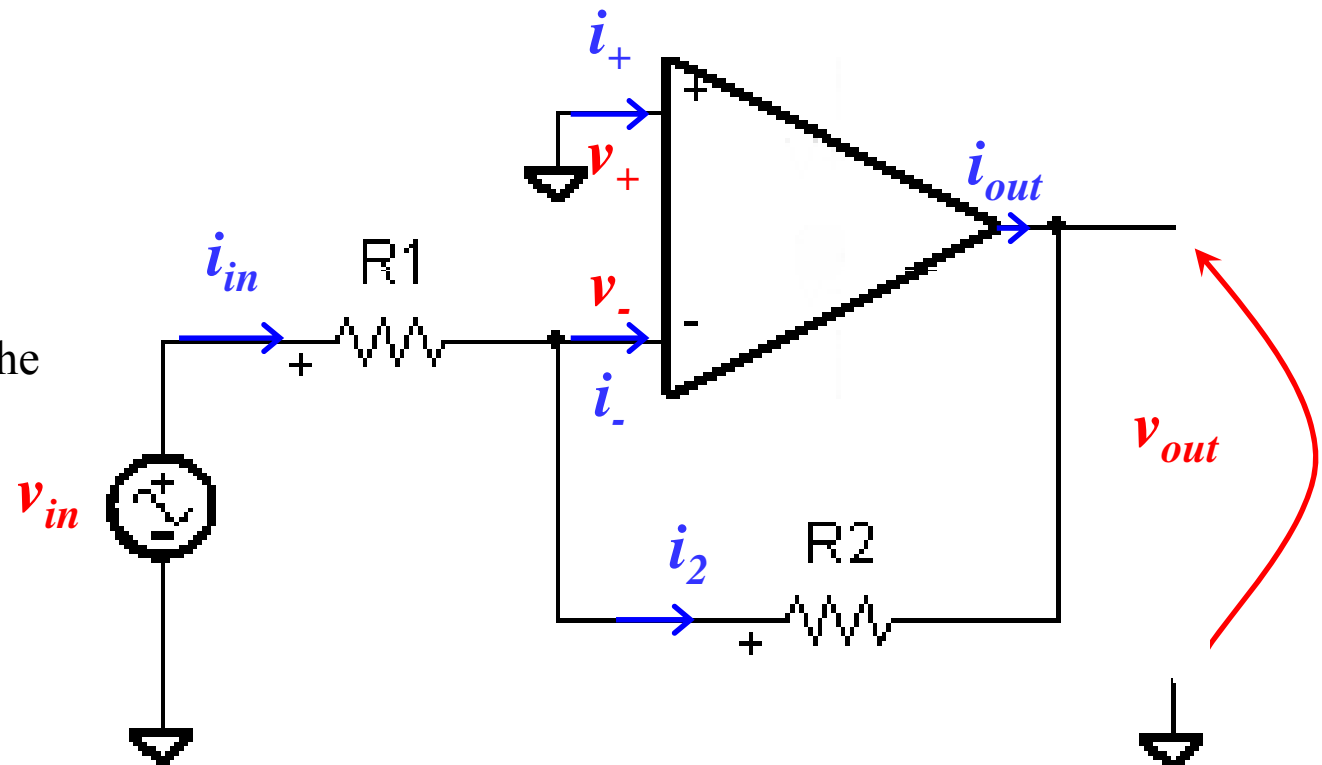

If $A_v \rightarrow \infty$, the above equation is only satisfied for $(v_+ - v_-) = 0$

- Feedback forces the two input voltages to be equal! This is known as a “virtual ground”.
- R1 and R2 form a “Feedback Network”

Inverting Amplifier

• Finite voltage gain results from an infinite voltage gain amplifier with “negative feedback” (feedback that takes a fraction of the output voltage and mixes it back into the negative summation node).

$$1) \quad v_{in} - i_{in}R_1 - i_2R_2 - v_o = 0$$

$$2) \quad i_{in} = i_- + i_2 = i_2 \text{ due to infinite input resistance}$$

$$i_{in} = \frac{v_{in} - v_-}{R_1}$$

but $v_- = 0$ due to the virtual ground


$$3) \quad i_{in} = \frac{v_{in}}{R_1}$$

Combining 1, 2 and 3,

$$v_{in} - \frac{v_{in}}{R_1}R_1 - \frac{v_{in}}{R_1}R_2 - v_o = 0$$

$$\frac{v_o}{v_{in}} = -\frac{R_2}{R_1}$$

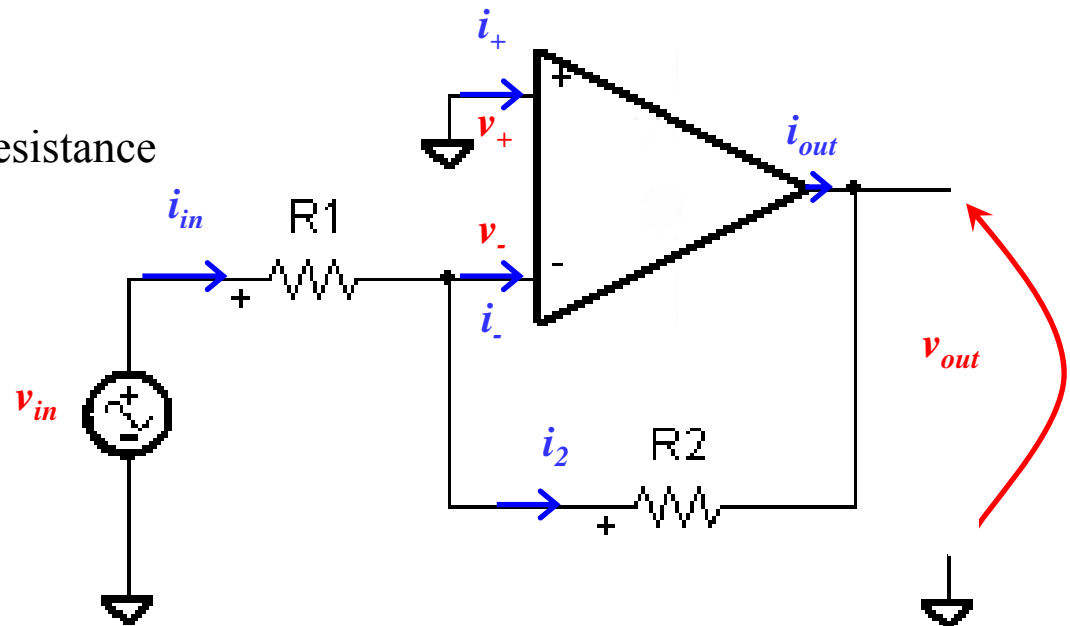
Overall circuit gain is finite, negative (for this feedback configuration) and set by the feedback resistor network.



Inverting Amplifier

- Input Resistance:

$$R_{in} = \frac{v_{in}}{i_{in}} = R_1$$

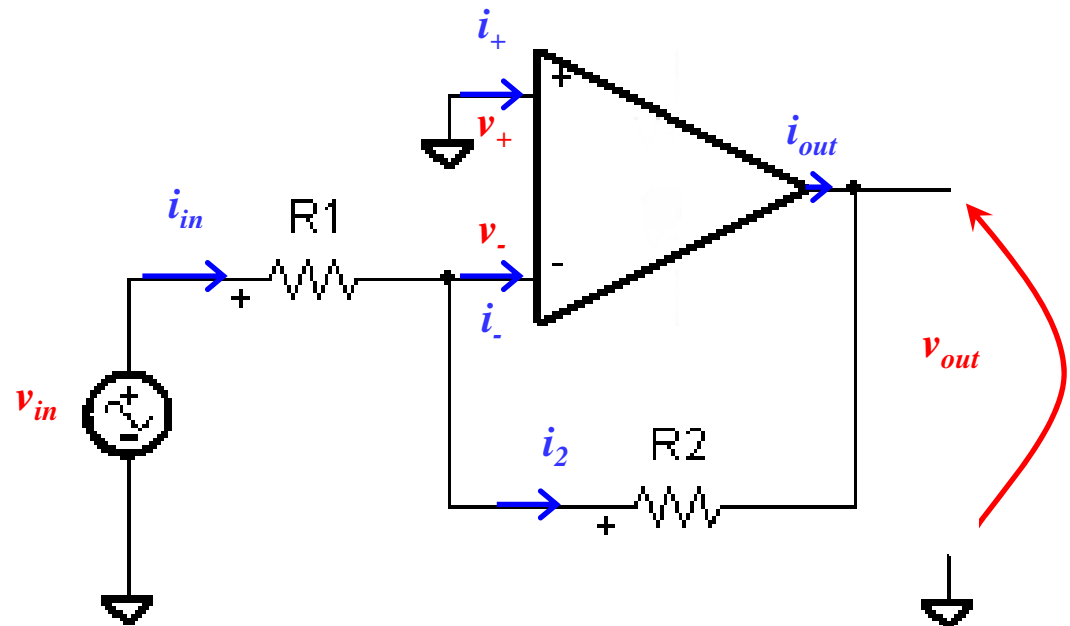

Inverting Amplifier

- Output Resistance:

$$V_t = i_1 R_3 + i_2 R_1$$

but,

$$i_1 = 0 \text{ since } v_- = 0$$


and

$$i_1 = i_2$$


thus,

$$V_t = 0 + 0$$

$$R_{out} = \frac{V_t}{i_t} = 0$$

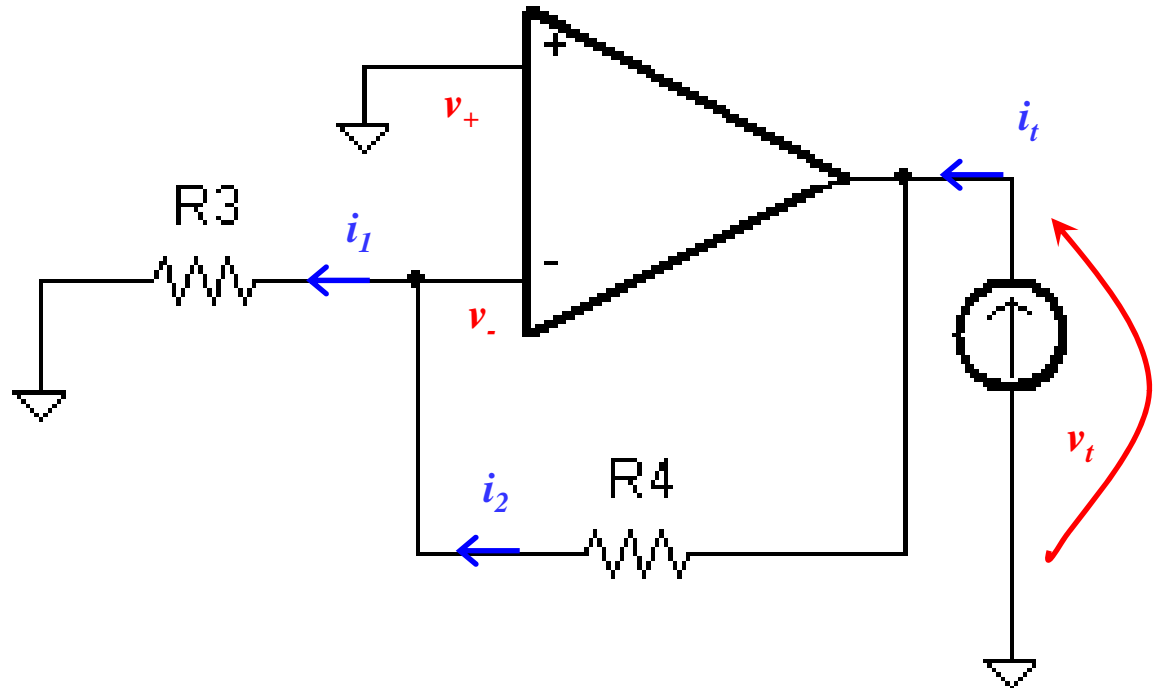

Non-Inverting Amplifier

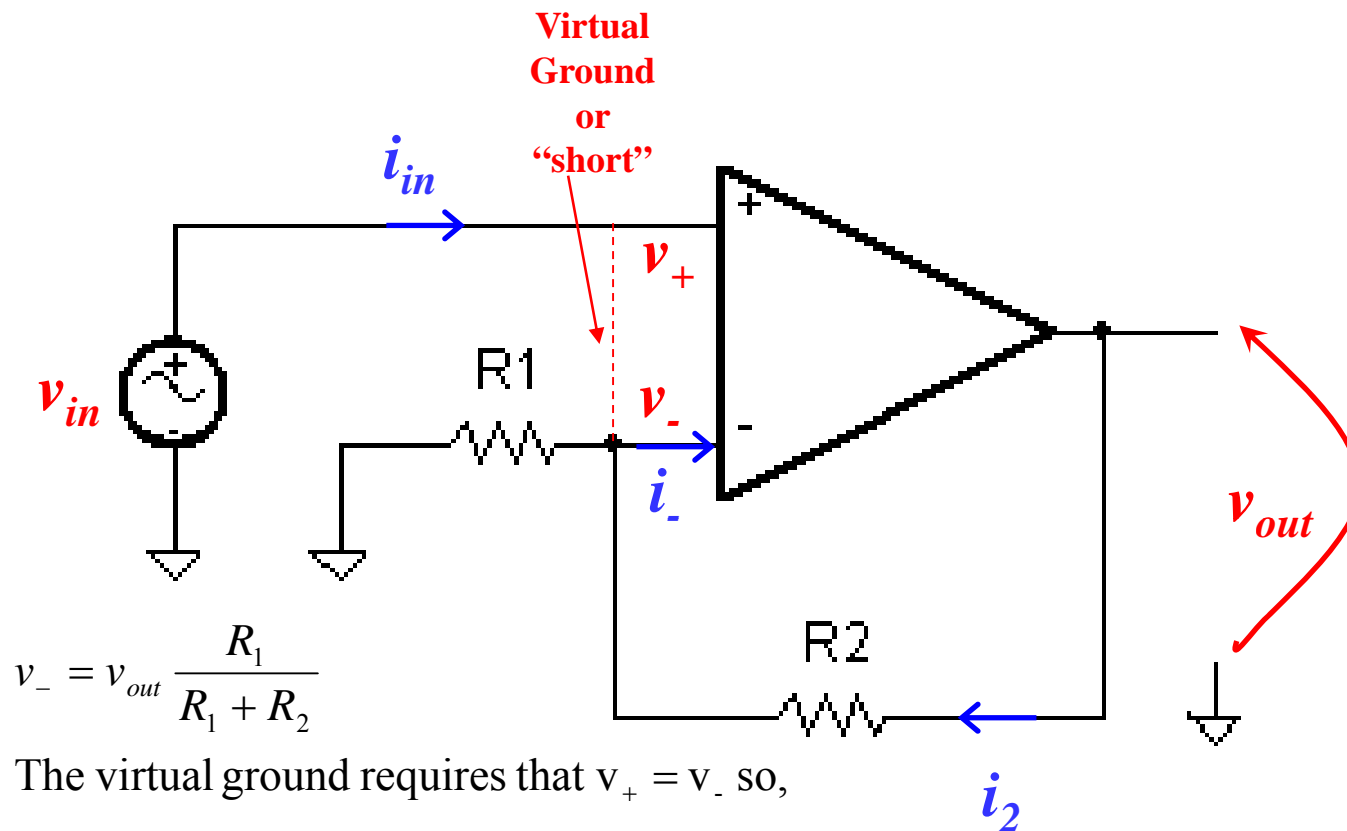

$$v_- = v_{out} \frac{R_1}{R_1 + R_2}$$

The virtual ground requires that $v_+ = v_-$ so,

$$v_{in} = v_-$$

so,


$$\frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_-} = \frac{R_1 + R_2}{R_1}$$

$$A_v = \frac{v_{out}}{v_{in}} = 1 + \frac{R_2}{R_1}$$

$$R_{in} = \frac{v_{in}}{i_{in}} = \frac{v_{in}}{0} = \infty$$

$$R_{out} = 0 \quad (\text{Same circuit as for Non - inverting case})$$

Unity Gain Buffer or “Voltage Follower”

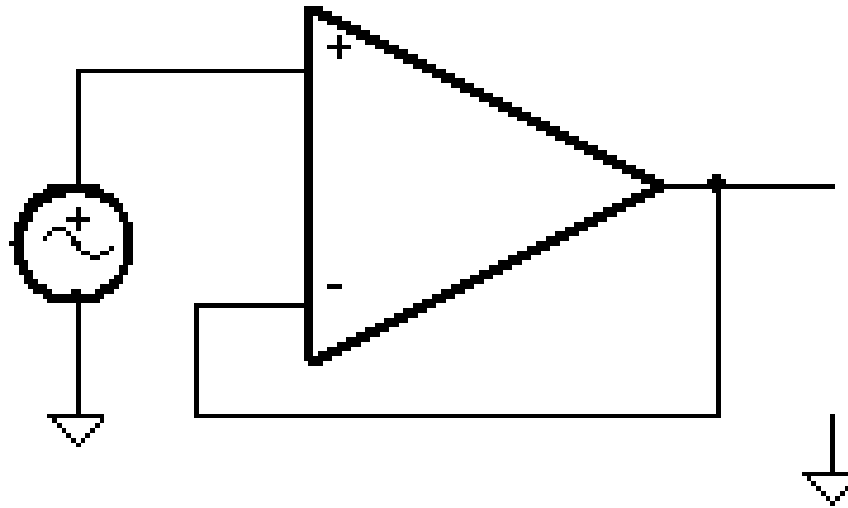

Same as Non – inverting amplifier except $R_2 = 0$ and $R_1 = \infty$

$$A_v = \frac{v_{out}}{v_{in}} = 1 + \frac{R_2}{R_1} \Rightarrow A_v = 1$$

$$R_{in} = \frac{v_{in}}{i_{in}} = \frac{v_{in}}{0} = \infty$$

$R_{out} = 0$ (Same circuit as for Non - inverting case)

- Can be used to isolate a high impedance circuit from a low impedance circuit

Summing Amplifier


$$i_2 = i_{in,a} + i_{in,b} + i_{in,c}$$

$$-\frac{v_{out}}{R2} = \frac{v_{in,a}}{R1a} + \frac{v_{in,b}}{R1b} + \frac{v_{in,c}}{R1c}$$


$$v_{out} = -v_{in,a} \frac{R2}{R1a} - v_{in,b} \frac{R2}{R1b} - v_{in,c} \frac{R2}{R1c}$$

$$v_{out} = -\left(v_{in,a} \frac{R2}{R1a} + v_{in,b} \frac{R2}{R1b} + v_{in,c} \frac{R2}{R1c} \right)$$

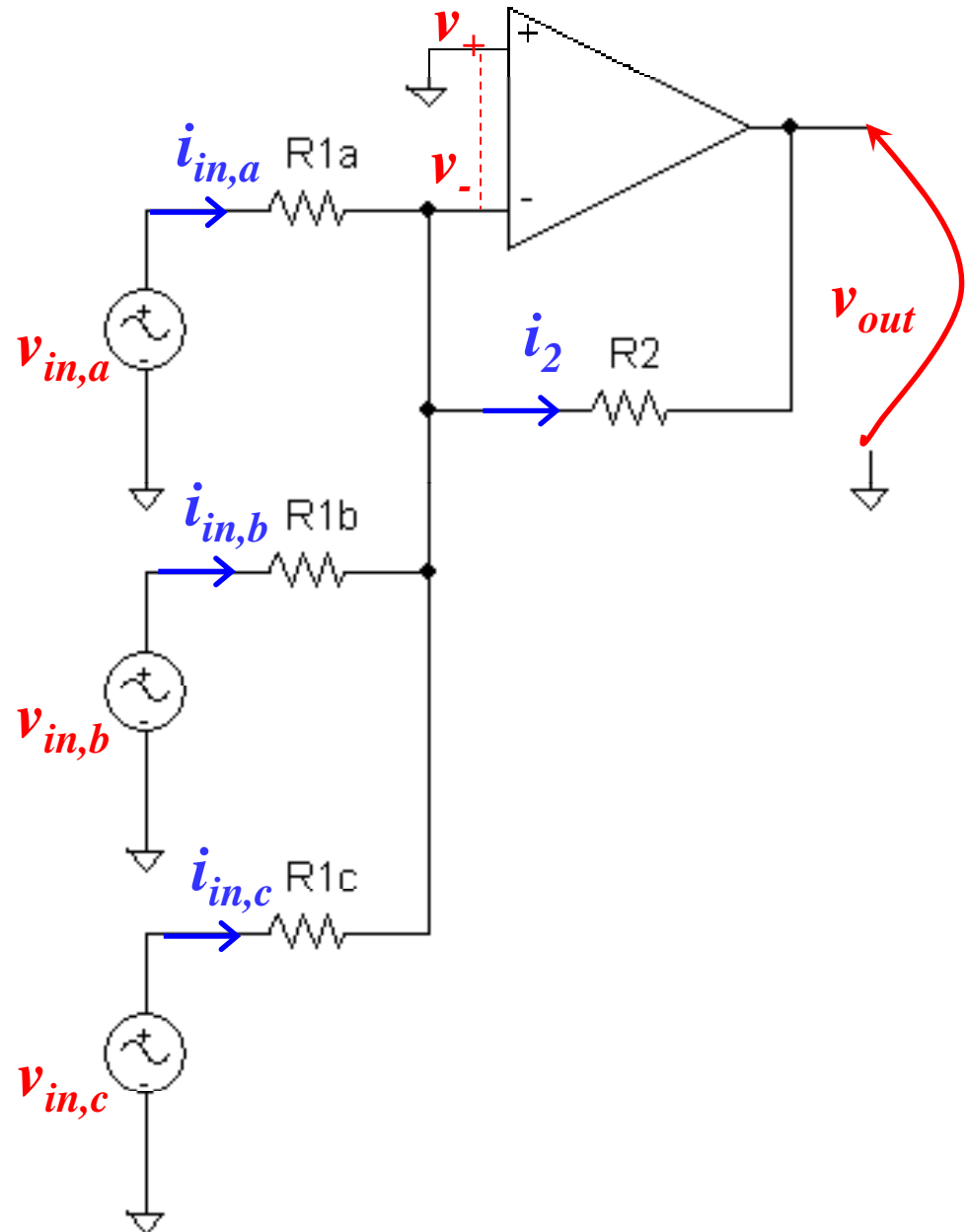- Output is a scaled sum of inputs.
- Scaling can be controlled by ratios of resistors




Difference Amplifier

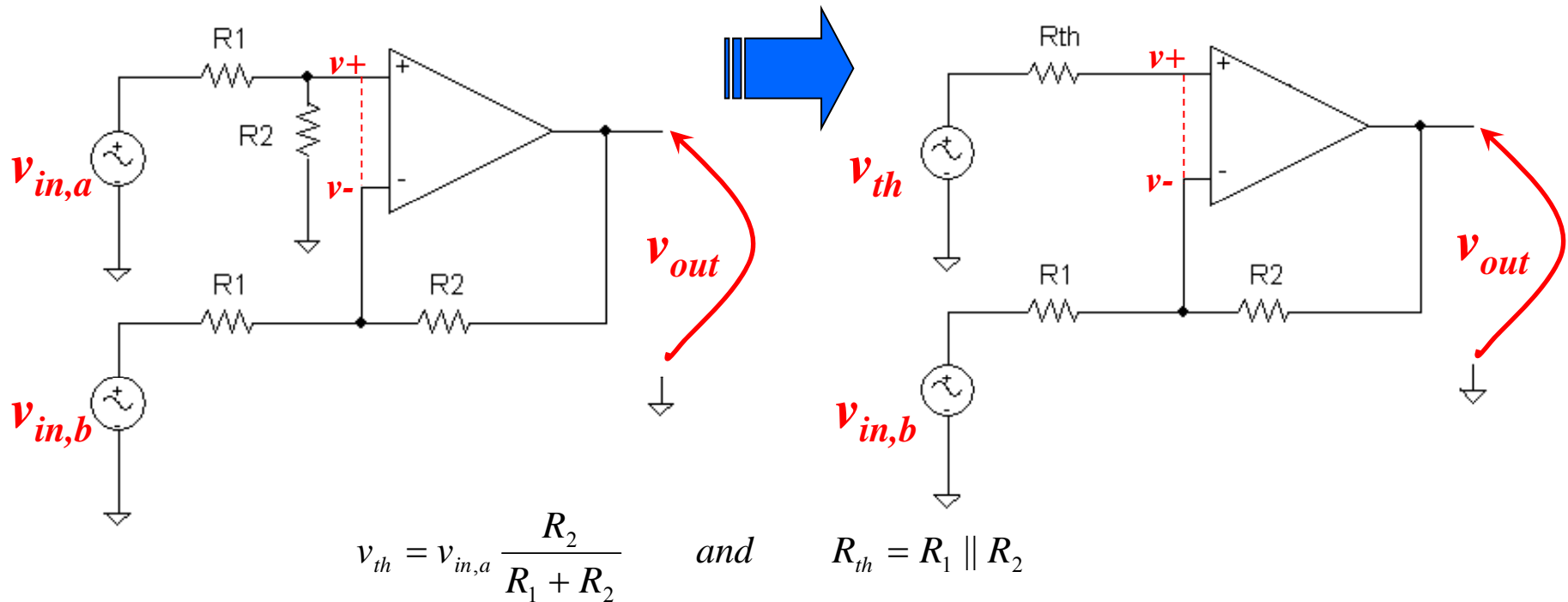

Using Superposition we can combine the results of the Inverting and Non-inverting solutions:

$v_{in,b}=0$	$v_{in,a}=0$
$v_{out} = v_{th} \left(1 + \frac{R_2}{R_1} \right)$	$v_{out} = -v_{in,b} \frac{R_2}{R_1}$
$v_{out} = v_{in,a} \frac{R_2}{R_1 + R_2} \left(1 + \frac{R_2}{R_1} \right)$	
$v_{out} = v_{in,a} \frac{R_2}{R_1}$	

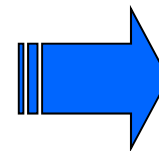

$$v_{out} = v_{in,a} \frac{R_2}{R_1} - v_{in,b} \frac{R_2}{R_1}$$

$$v_{out} = (v_{in,a} - v_{in,b}) \frac{R_2}{R_1}$$

This circuit amplifies the difference of two signals

Non-Ideal (Real World) Operational Amplifiers

Finite Open-Loop Gain

- Real op-amps do not have “infinite” “open loop (without feedback)” gain.
- Voltage gains are typically large but finite: $\sim 10^4$ - 10^6 V/V
- Finite gain causes a deviation from ideal amplifier behavior

$$v_- = v_{out} \frac{R_1}{R_1 + R_2} = \beta v_{out}$$

where $\beta = \frac{R_1}{R_1 + R_2}$ is known as the feedback factor


$$v_{out} = A_{openloop} (v_+ - v_-) = A_{openloop} (v_+ - \beta v_{out})$$

so since $v_+ = v_{in}$,

$$A_{v, closed\ loop} = \frac{v_{out}}{v_{in}} = \frac{A_{openloop}}{1 + \beta A_{openloop}}, \text{ where } \beta A_{openloop} \text{ is the loop gain}$$

If $\beta A_{openloop} \gg 1$
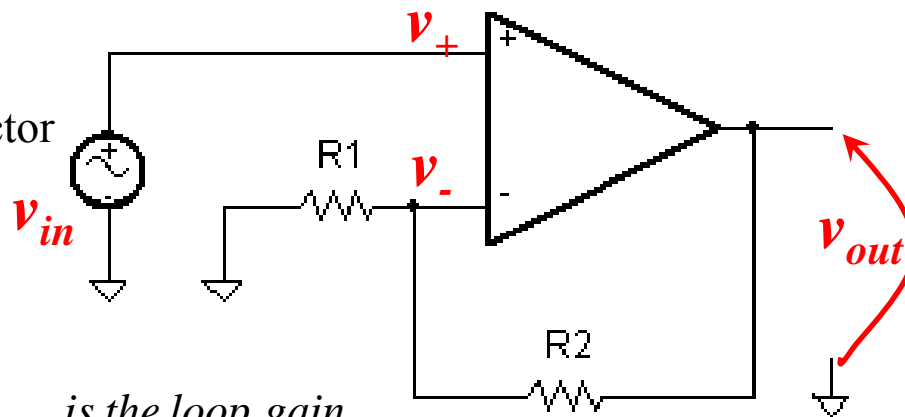
$$A_{v, closed\ loop} = \frac{1}{\beta} = 1 + \frac{R_2}{R_1} \Rightarrow \text{approaches the infinite gain result}$$




Non-Ideal (Real World) Operational Amplifiers


Finite Open-Loop Gain

- Finite open-loop gain means the Virtual Ground is not perfect!
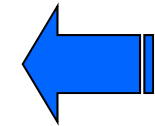
$$v_+ - v_- = v_{in} - \beta v_{out} = v_{in} - \beta \left(\frac{A_{openloop}}{1 + \beta A_{openloop}} \right) v_{in} = \frac{v_{in}}{1 + \beta A_{openloop}}$$



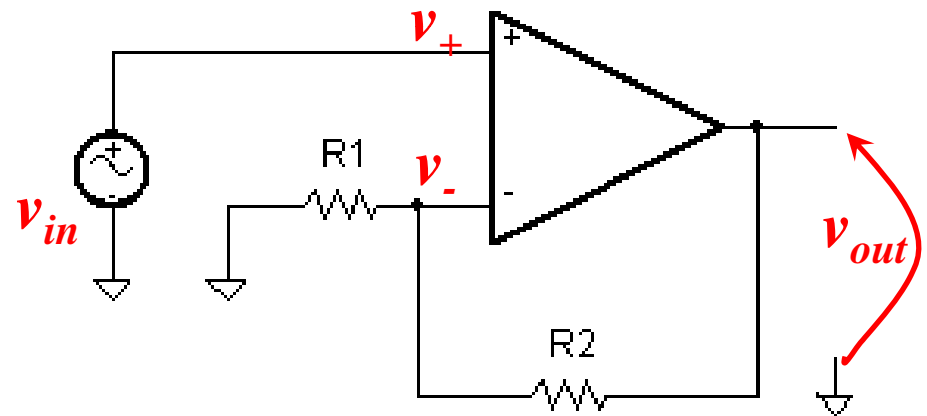**Small but finite
offset between +
and - terminals**




- The Gain Error (GE) that results from the Non-infinite open-loop gain can be quantified as:

$$GE = \left(\frac{1}{\beta} \right) - \left(\frac{A_{openloop}}{1 + \beta A_{openloop}} \right) v_{in} = \frac{v_{in}}{\beta (1 + \beta A_{openloop})}$$

Non-Ideal (Real World) Operational Amplifiers

Finite Output Impedance

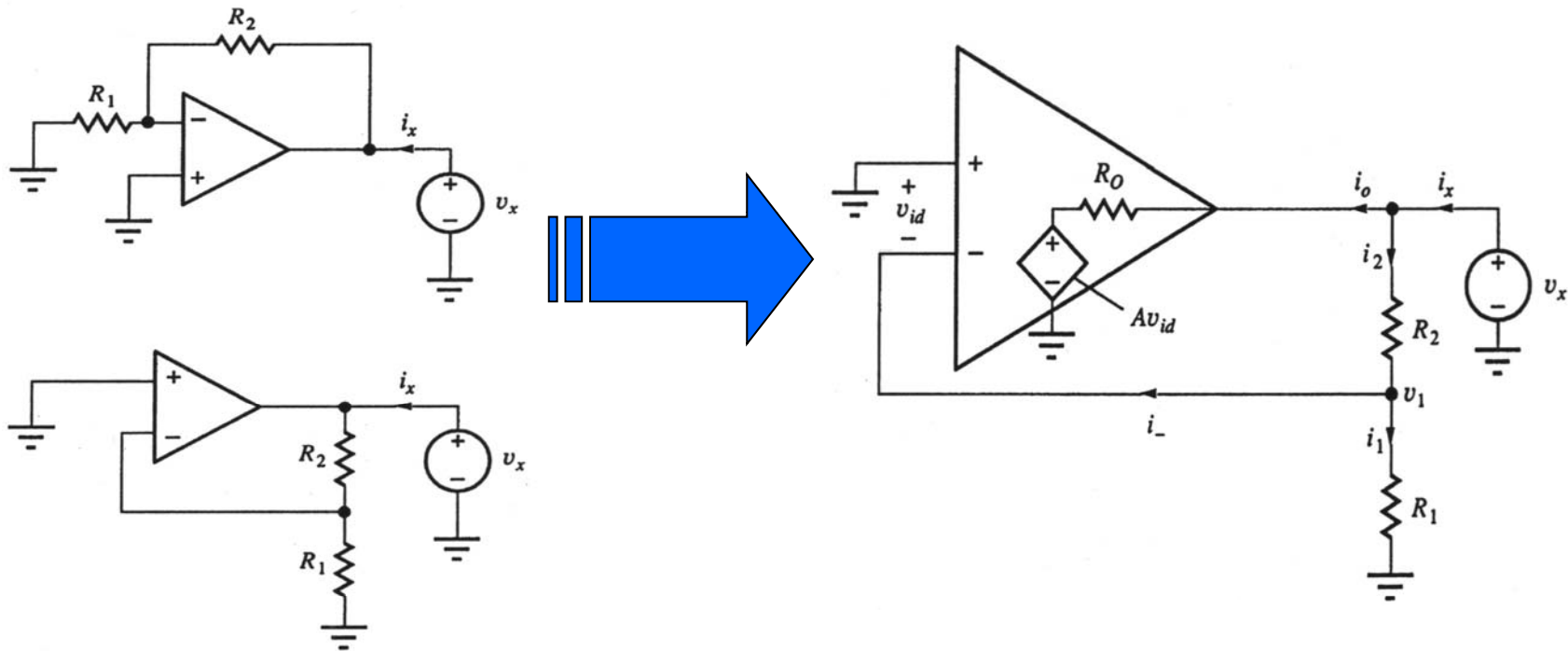- Real Op-Amps have a small but finite output impedance, R_o .
- We want to find the Output impedance of the various circuits we have examined.
- All the configurations have a common circuit for calculating the output impedance.



Non-Ideal (Real World) Operational Amplifiers

Finite Output Impedance

$$R_{out} = \frac{v_x}{i_x}$$

$$i_x = i_o + i_2$$

$$i_o = \frac{v_x - A_{v,openloop}(v_+ - v_-)}{R_o}$$


$$v_x = i_2(R_1 + R_2) \Rightarrow i_2 = \frac{v_x}{(R_1 + R_2)}$$

$$v_- = \frac{R_1}{(R_1 + R_2)} v_x = \beta v_x$$

$$(R_{out})^{-1} = \frac{i_x}{v_x} = \frac{1 + A_{v,openloop}\beta}{R_o} + \frac{1}{(R_1 + R_2)}$$

$$R_{out} = \left(\frac{R_o}{1 + A_{v,openloop}\beta} \right) \parallel (R_1 + R_2)$$

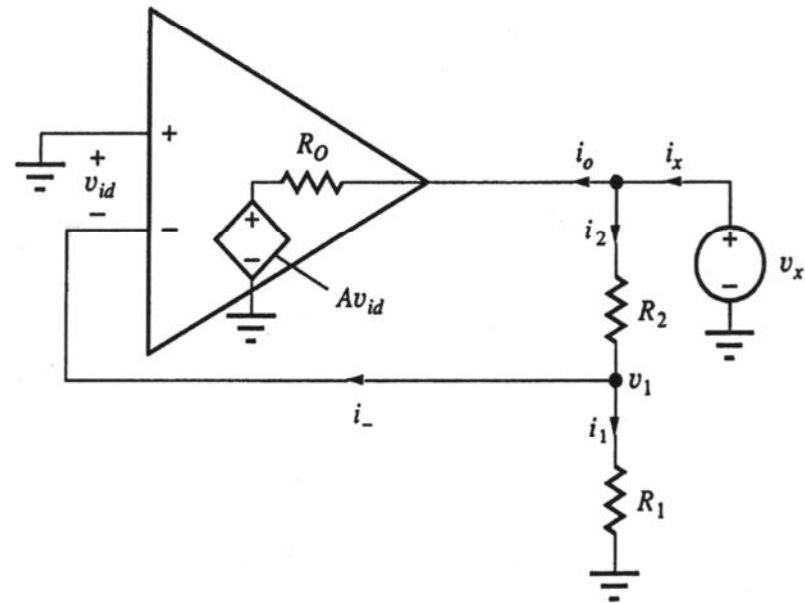R_o is very small so this term is EXTREMELY small!
FEEDBACK REDUCES OUTPUT IMPEDANCE!



Non-Ideal (Real World) Operational Amplifiers

Finite Input Impedance: Non-Inverting Case

- Real Op-Amps have a large but finite input resistance, R_{ID}

$$i_x = \frac{v_x - v_-}{R_{ID}}$$

Neglecting the current i_x compared to i_1 and i_2 (due to $R_{ID} \gg R_1$ or R_2)

$$v_- = i_1 R_1 \approx i_2 R_1$$


$$v_- = \frac{R_1}{R_1 + R_2} v_{out} = \beta v_{out} = A_{v,openloop} \beta (v_x - v_-)$$

$$v_- = \frac{A_{v,openloop} \beta}{1 + A_{v,openloop} \beta} v_x$$

$$i_x = \frac{v_x - \left(\frac{A_{v,openloop} \beta}{1 + A_{v,openloop} \beta} v_x \right)}{R_{ID}} = \frac{v_x}{(1 + A_{v,openloop} \beta) R_{ID}}$$

$$R_{in} = \underbrace{(1 + A_{v,openloop} \beta)}_{\text{Feedback}} R_{ID}$$

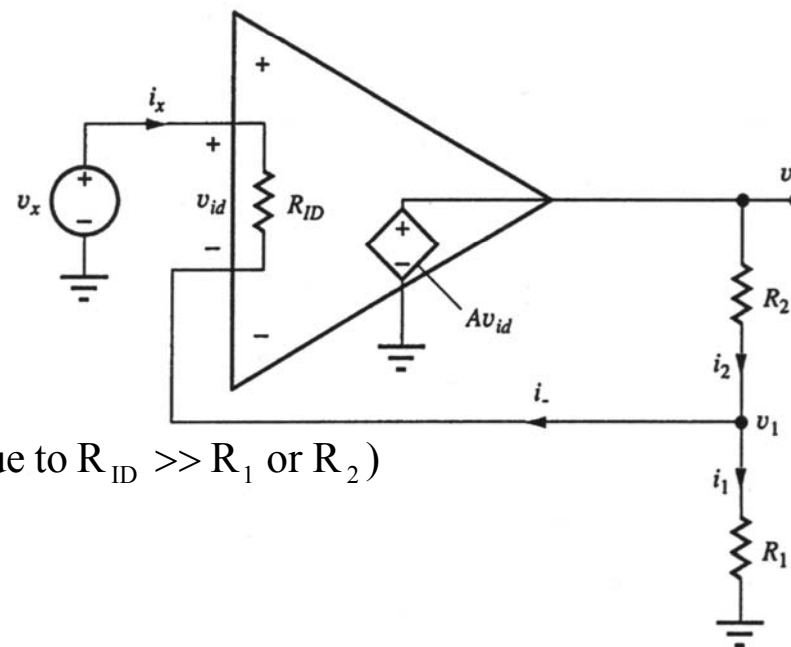R_{ID} is very large so R_{in} is EXTREMELY large!



**FEEDBACK
INCREASES INPUT
IMPEDANCE!**

Non-Ideal (Real World) Operational Amplifiers

Finite Input Impedance: Inverting Case

• Real Op-Amps have a large but finite input resistance, R_{ID}

• $R_{in} = R_1 + R'_{in}$

• Find R'_{in} by forming a new test circuit

$$i_1 = i_- + i_2 = \frac{v_1}{R_{ID}} + \frac{v_1 - v_{out}}{R_2} = \frac{v_1}{R_{ID}} + \frac{v_1 + A_{v,openloop} v_1}{R_2}$$

$$(R'_{in})^{-1} = \frac{i_1}{v_1} = \frac{1}{R_{ID}} + \frac{1 + A_{v,openloop}}{R_2}$$

$$R'_{in} = (R_{ID}) \parallel \left(\frac{R_2}{1 + A_{v,openloop}} \right)$$

Thus,

$$R_{in} = R_1 + (R_{ID}) \parallel \left(\frac{R_2}{1 + A_{v,openloop}} \right)$$

Since $R_{ID} \gg R_2 / (1 + A_{v,openloop})$ and $A_{v,openloop}$ is very large,

$$R_{in} = R_1 + (R_{ID}) \parallel \left(\frac{R_2}{1 + A_{v,openloop}} \right) \Rightarrow R_{in} = R_1 + \left(\frac{R_2}{1 + A_{v,openloop}} \right) \approx R_1$$

