

# **Lecture 33**


## **Digital Logic Gates**

**Reading: Jaeger 6.6-6.9, 7.1-7.5 and Notes**
 
# Resistive Load Inverter

“Pull Up” Resistor provides current to Charge up the Load Capacitor,  $C_L$

Load Capacitor,  $C_L$ , represents the total capacitance of all gates that would be connected to the output (Input capacitance's of the MOSFETS)




Switching transistor will “Pull down” the output voltage by discharging the Load Capacitor,  $C_L$  when the transistor is conducting.

Note:  $V_{BS}=0$
 
## Resistive Load Inverter

Inverter State:  
Input is Low  
Output is High



$$v_o = v_{DS} = V_{DD} - i_D R$$

For  $v_i = v_{GS} = V_{OL} < V_T$


$$i_D = 0 \quad \Rightarrow \quad v_o = V_{DD} = V_{OH}$$

$V_{OL} < V_T$  is our first design criteria!

For a nominal  $V_T = 1$ , we would typically make  
 $V_{OL} \sim 0.25V$  to insure adequate noise margin.
 
## Resistive Load Inverter

Inverter State:  
Input is High  
Output is Low




$$v_o = v_{DS} = V_{DD} - i_D R$$

For  $v_i = v_{GS} = V_{OH} = V_{DD}$  from previous page,  $v_o = V_{OL}$

*Since  $v_{GS} = V_{DD} > v_{DS} \Rightarrow$  we must be in the linear region!*
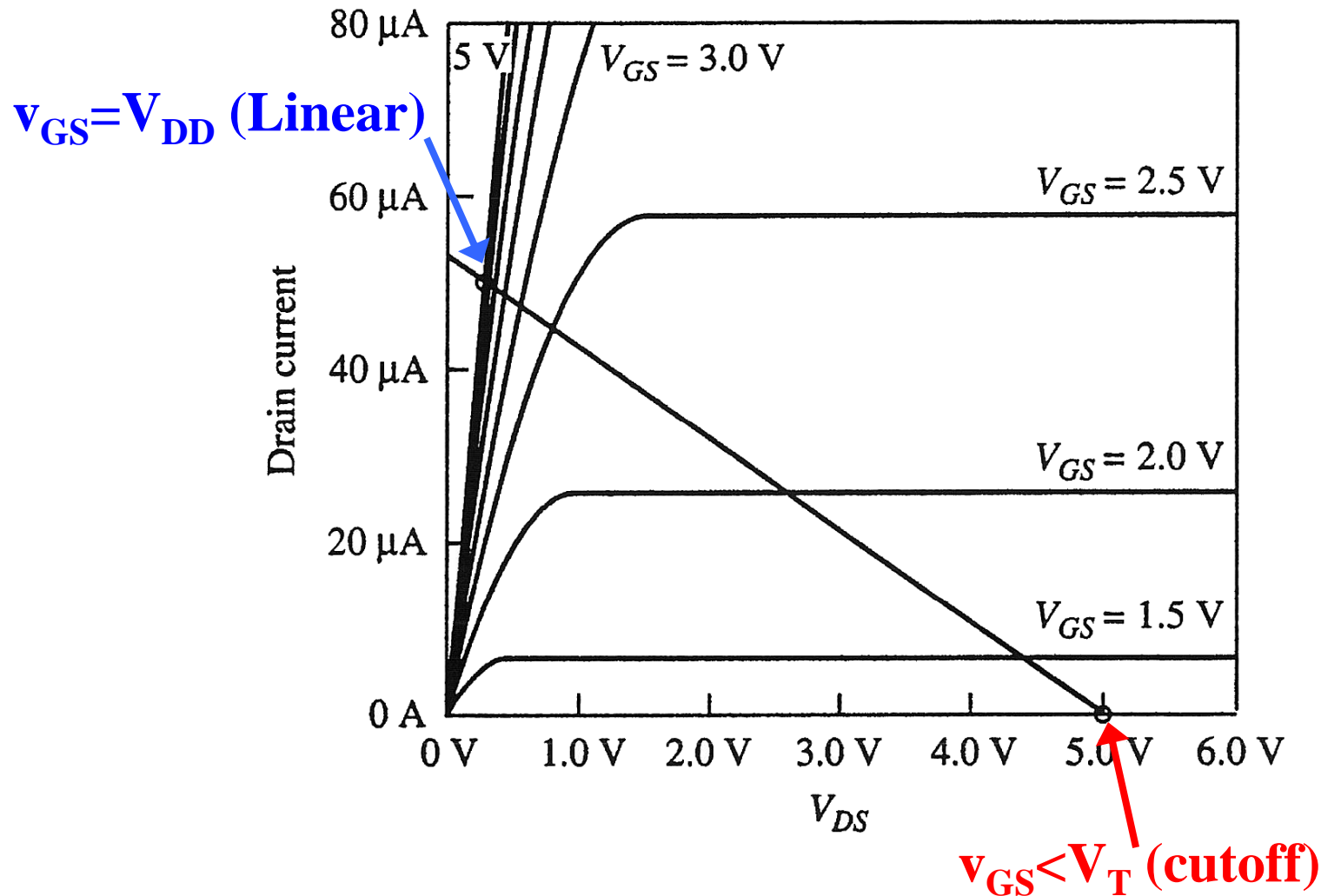
# Resistive Load Inverter

The MOSFET switches between the two operating points,  $v_{GS} < V_T$  (cutoff) and  $v_{GS} = V_{DD}$  (Linear) along a “Resistive” (linear IV characteristic) “Load Line” passing through the saturation region during the transition.



## Resistive Load Inverter

Example: If we wanted the gate to dissipate 0.25 mW using a  $V_{TN}=1V$  and  $K_n'=25e-6 A/V^2$ , and having a  $V_{OL}=0.25V$ , what  $W/L$  ratio would be needed? What load resistance is required?

Since,

$$Power = V_{DD} \times i_{DS}$$

$$0.25e-3 = 5i_{DS}$$

$$i_{DS} = 50\mu A$$


$$i_{DS} = K_n' \left( \frac{W}{L} \right) (v_{GS} - V_{TN} - 0.5v_{DS}) v_{DS}$$

$$50e-6 = 25e-6 \left( \frac{W}{L} \right) (5 - 1 - .125) 0.25$$

$$\left( \frac{W}{L} \right) = \frac{2.06}{1}$$

$$R = \frac{V_{DD} - V_{OL}}{i_{DS}} = \frac{5 - 0.25}{50e-6} = 95 K\Omega$$


# Resistive Load Inverter

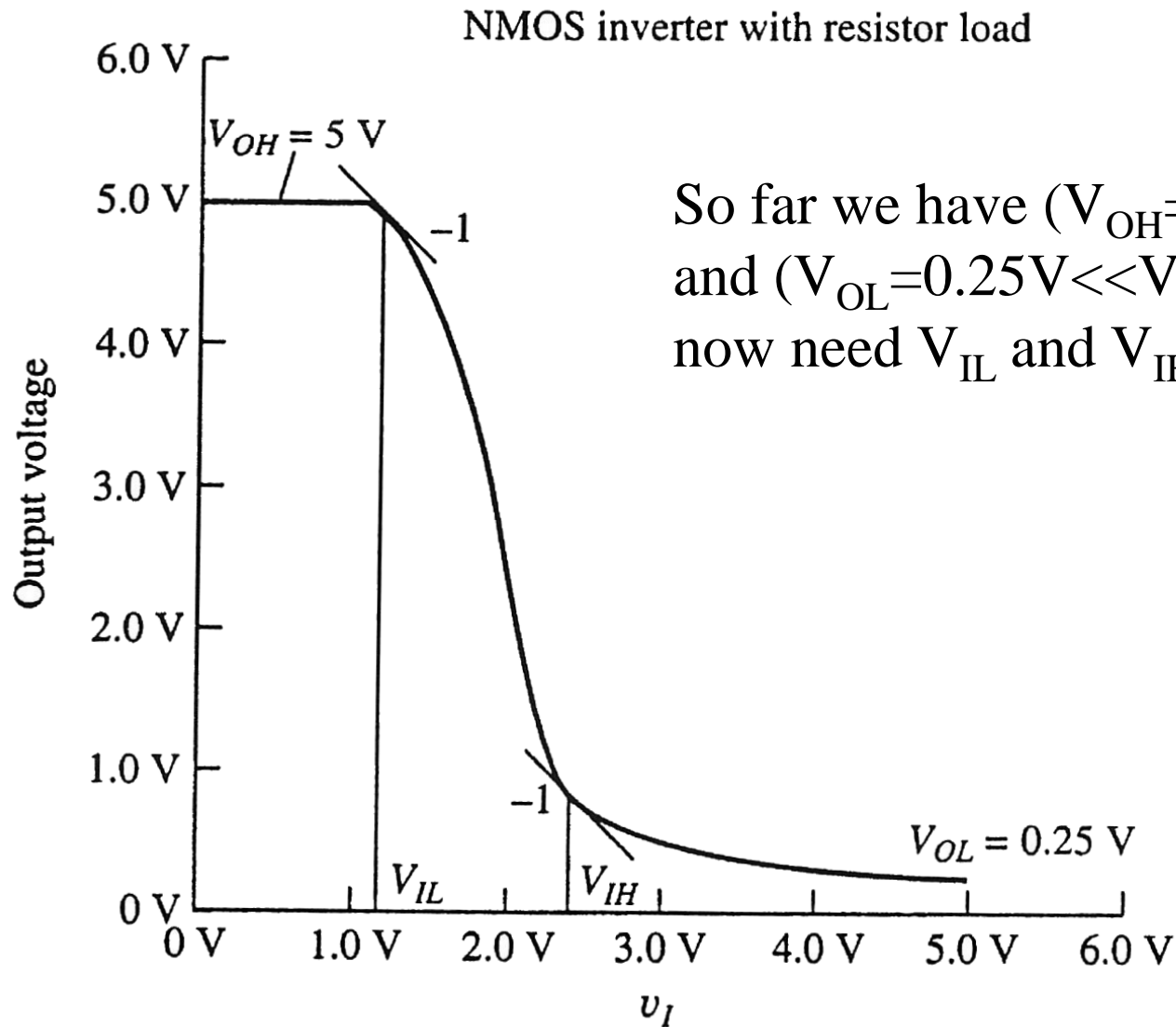

So far we have ( $V_{OH}=5\text{ V}$ )  
and ( $V_{OL}=0.25\text{ V}\ll V_T$ ). We  
now need  $V_{IL}$  and  $V_{IH}$ .

# Resistive Load Inverter

## Calculating $V_{IL}$

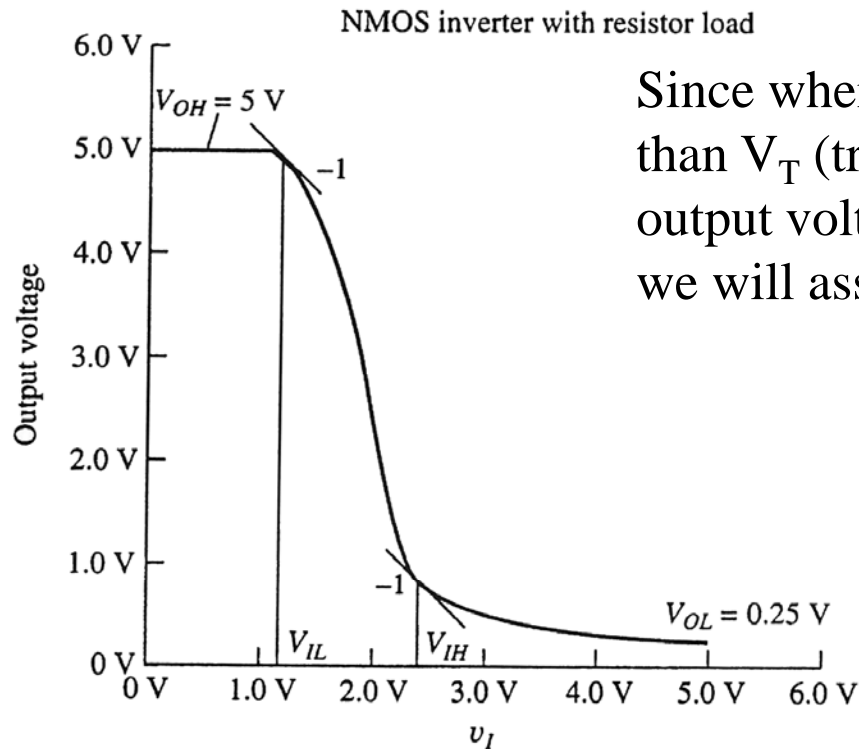

Since when  $v_i = V_{IL}$ ,  $v_{GS}$  is small but clearly greater than  $V_T$  (transistor is conducting as observed from the output voltage being reduced) and since  $v_{DS}$  is large, we will assume saturation.

$$i_{DS} = 0.5K_n (V_{GS} - V_{TN})^2 \quad \text{and} \quad v_o = V_{DD} - i_{DS}R$$

$$v_o = V_{DD} - 0.5K_n (v_i - V_{TN})^2 R$$

$$\left. \frac{dv_o}{dv_i} \right|_{v_i = V_{IL}} = -K_n (v_i - V_{TN}) R = -1$$

$$v_i = V_{IL} = V_{TN} + \frac{1}{K_n R}$$

Also

$$v_o = V_{DD} - \frac{1}{2K_n R}$$

Inverter

Transitional State:

Input is Low

Output is High



## Resistive Load Inverter

Example (cont'd): For our previous example,

$$v_i = V_{IL} = V_{TN} + \frac{1}{K_n R} = 1 + \frac{1}{25 e^{-6} \left( \frac{2.06}{1} \right) 95,000} = 1.2V$$

and,

$$v_o = V_{DD} - \frac{1}{2K_n R} = 5 - \frac{1}{2 \left[ 25 e^{-6} \left( \frac{2.06}{1} \right) \right] 95,000} = 4.9V$$

*Verifying our assumption of Saturation :*

$$v_{GS} - V_{TN} = 1.2 - 1 < v_{DS} = 4.9$$

# Resistive Load Inverter

## Calculating $V_{IH}$

Since when  $v_i = V_{IH}$ ,  $v_{GS}$  is large and since  $v_{DS}$  is small, we will assume linear operation.

$$i_{DS} = K_n (v_{GS} - V_{TN} - 0.5v_{DS})v_{DS} \quad \text{and} \quad v_o = V_{DD} - i_{DS}R$$

$$v_{GS} = v_i \quad \text{and} \quad v_{DS} = v_o$$

$$v_o = V_{DD} - K_n (v_i - V_{TN} - 0.5v_o)v_o R$$

$$\frac{v_o^2}{2} - v_o \left[ v_i - V_{TN} + \frac{1}{K_n R} \right] + \frac{V_{DD}}{K_n R} = 0$$

$$\text{Setting } \left. \frac{dv_o}{dv_i} \right|_{v_i=V_{IH}} = -1 \text{ and solving for } v_i$$

$$v_i = V_{IH} = \boxed{V_{TN} - \frac{1}{K_n R} + 1.63 \sqrt{\frac{V_{DD}}{K_n R}}}$$

and,

$$\boxed{v_o = \sqrt{\frac{2V_{DD}}{3K_n R}}}$$

Inverter  
Transitional State:  
Input is High  
Output is Low

## Resistive Load Inverter

### Calculating $V_{IH}$

Example (cont'd): For our previous example,

$$V_{IH} = V_{TN} - \frac{1}{K_n R} + 1.63 \sqrt{\frac{V_{DD}}{K_n R}} = 2.44V$$

and,

$$v_o = \sqrt{\frac{2V_{DD}}{3K_n R}} = 0.83V$$

Thus, our Noise Margins are:

$$NM_L = V_{IL} - V_{OL} = 1.2 - 0.25 = 0.95V$$

and,


$$NM_H = V_{OH} - V_{IH} = 5 - 2.44 = 2.56V$$

This approach is good for single gate or small numbers of gates on a chip, but the large amount of area required to make the resistors prevent it from being used for very dense digital circuits. ***We need a different approach!***

# Procedure Summary


1. **Select a  $V_{OL}$**  based on a power specification or other design criteria such as noise margin, etc... This is a fairly open parameter.
2. **Determine what  $V_{OH}$**  corresponds to this  $V_{OL}$ . When the switching transistor is off ( $v_i = V_{OL}$ ), what  $V_{OH}$  results at the output?
3. **Design the Switching Transistor for the required  $V_{OL}$** : Determine the L/W ratio needed to achieve this  $V_{OL}$  at the output for this  $V_{OH}$  at the input. To do this you have to properly identify what bias region you are in (linear, cutoff or saturation). Lower  $V_{OL}$  will require a wider transistor (more conductive) in order to “pull the output low”. Lower  $V_{OH}$  at the input will not “turn on the transistor as hard” and thus will also need a more conductive (wider) switching transistor.
4. **Design the Load Resistor/Transistor for the required  $V_{OL}$** : Determine the required load (resistor or transistor L/W) needed to achieve this  $V_{OL}$  at the output for this  $V_{OH}$  at the input. If the load is a transistor (later) you will need to determine the proper bias mode linear, cutoff or saturation.
5. **Find the Intermediate State 1/0 Edge voltages  $V_{IL}$  and  $V_{IH}$** : For  $V_{IL}$  and  $V_{IH}$  they are each found the same way. 1<sup>st</sup>, determine an appropriate voltage transfer function (relating  $v_i$  to  $v_o$ ) by setting the currents of the two devices equal. To do this, you will need to determine the proper bias mode linear, cutoff or saturation of each device. Next, take the derivative of the voltage transfer equation and set it equal to -1. Calculate the input voltage required for this slope to equal -1. This is by definition  $V_{IL}$  or  $V_{IH}$ . Note that  $V_{IL}$  and  $V_{IH}$  are two separate calculations and will have two different bias modes (i.e. different selections of linear, or saturation equations).

# Our Options

 

Linear Load:  $V_{GG} > V_{DD}$  so  
 $V_{GS-L} > V_{DS-L}$

 Requires an extra power supply and is therefore, expensive!




Saturated Enhancement Load:

$$V_{GS-L} - V_{TN} < V_{DS-L}$$


$$-V_{TN} < 0$$

Always Saturated (when on)

 

Depletion Load:

## Saturated Enhancement Load

 

$$V_{GS-L} = V_{DS-L}$$

Inverter State:  
Input is Low  
Output is High


As before, for  $v_i = v_{GS} = V_{OL} < V_T$

$$i_{DS-S} = 0$$

$V_{OL} < V_T$  is our first design criteria!

For a nominal  $V_T = 1$ , we would typically make  $V_{OL} \sim 0.25V$  to insure adequate noise margin.

## Saturated Enhancement Load

 

$$V_{GS-L} = V_{DS-L}$$

For  $v_i = v_{GS} = V_{OH}$ ,  $M_S$  and  $M_L$  conduct their maximum amount of current.

$$v_O = V_{OL} = 0.25V \text{ so,}$$

$$V_{DS-L} = V_{DD} - v_O = 4.75V$$

$$i_{DS-L} = \frac{K'_n}{2} \left( \frac{W}{L} \right) \Big|_L (v_{GS-L} - V_{TN})^2$$

Using the same power design spec (0.25mW) and device parameters as before,

$$i_{DS-L} = 50\mu A, \text{ so}$$

Inverter State:


Input is High

Output is Low

$$50e-6 = 12.5e-6 \left( \frac{W}{L} \right) \Big|_L (4.75 - 1)^2$$

$$\left( \frac{W}{L} \right) \Big|_L = 0.284$$

## Saturated Enhancement Load

 


$$\left(\frac{W}{L}\right)\bigg|_L = 0.284$$

Since we normally reference the width to length ratio in terms of its “smallest dimension that we can fabricate” (as of 2001 this is  $\sim 0.07$   $\mu\text{m}$  in the lab,  $0.18$   $\mu\text{m}$  in production) we can express this in an alternative form. For our discussion, we will assume (for mathematical simplicity) that this smallest feature size is  $1\mu\text{m}$ . Thus,

$$\left(\frac{W}{L}\right)\bigg|_L = \frac{1}{3.52}$$



## Saturated Enhancement Load

 

Inverter State:  
Input is Low  
Output is High

$V_{OH}$ :

When  $M_S$  is off,  $C_L$  charges up through  $M_L$ , reducing  $V_{DS-L}$  until


$$V_{TN} = V_{GS-L} = V_{DS-L}$$

At this point,  $M_L$  cuts off preventing further charging.

Thus, when  $v_O = V_{OH}$ ,  $v_{GS-L} = V_{DD} - V_{TN}$  or  $V_{OH} = V_{DD} - V_{TN} = 5 - 1 = 4V$

$V_{OH}$  is significantly reduced from its previous (with resistive load) value!

## Saturated Enhancement Load

 

Since  $v_i = V_{GS-S} = V_{OH}$  is the voltage that forces  $M_S$  to turn on and force the output to  $V_{OL}$ , we must provide the same amount of “pull-down current” (50 $\mu$ A) for a lower voltage (4V instead of 5V). Thus, we need to make the transistor wider to conduct more current at the lower voltage. (Remember, the switching transistor is in the linear region for  $v_i = V_{OH}$  so it acts like a resistor. Providing less resistance will provide more drive current.)


Inverter State:  
Input is High  
Output is Low

$$i_{DS-S} = K'_n \left( \frac{W}{L} \right) \Big|_S (v_{GS-S} - V_{TN} - 0.5v_{DS-S}) v_{DS-S}$$

$$50e-6A = 25e-6 \left[ \frac{A}{V^2} \right] \left( \frac{W}{L} \right) \Big|_S (4V - 1V - 0.5(0.25V)) 0.25V$$

$$\left( \frac{W}{L} \right) \Big|_S = \frac{2.78}{1}$$



## Saturated Enhancement Load

 

Combining the results from before we see that our Load Transistor is much longer than it is wide, while our switching transistor is wider than it is long.

$$\left(\frac{W}{L}\right)\bigg|_L = \frac{1}{3.52} \qquad \left(\frac{W}{L}\right)\bigg|_S = \frac{2.78}{1}$$

## Saturated Enhancement Load

  

Since the substrate is common to both transistors, the body-to-source voltage,  $v_{SB}$ , varies as the output voltage varies. Thus, the threshold voltage varies resulting in a variation in  $V_{OH}$

$$V_{OH} = V_{DD} - V_{TN-L}$$

$$V_{OH} = V_{DD} - \left[ V_{TO} + \gamma \left( \sqrt{v_{SB} + 2\phi_F} - \sqrt{2\phi_F} \right) \right]$$

$$V_{OH} = V_{DD} - \left[ V_{TO} + \gamma \left( \sqrt{V_{OH} + 2\phi_F} - \sqrt{2\phi_F} \right) \right]$$

In writing the above equation we have only examined the condition when  $v_{SB} = V_{OH}$ . Since  $v_{SB} = v_O$ , the threshold voltage is continuously varying as the device is switched, introducing an additional level of “non-linearity”

( $v_O = f(v_O)$  and  $i_{DS} = f(v_O)$ ).

## Saturated Enhancement Load

If  $\gamma = 0.5 \sqrt{V}$  and  $2\phi_F = 0.6V$

$$V_{OH} = V_{DD} - \left[ V_{TO} + \gamma \left( \sqrt{V_{OH} + 2\phi_F} - \sqrt{2\phi_F} \right) \right]$$

$$V_{OH} = 5 - \left[ 1 + 0.5 \left( \sqrt{V_{OH} + 0.6} - \sqrt{0.6} \right) \right]$$

or

$$V_{OH}^2 - 9.03V_{OH} + 19.1 = 0$$

$$V_{OH} = 3.39V \text{ or } \del{5.64V}$$

## Saturated Enhancement Load

Since the body effect changes  $V_{TN}$ , we need to readjust the width to length ratios of both transistors:

$M_S$ :  $V_{OH}$  is lower than what we used before, so we need the same current at a lower voltage--make the switching transistor even wider!

$$i_{DS-S} = K'_n \left( \frac{W}{L} \right) \Big|_S (v_{GS-S} - V_{TN} - 0.5v_{DS-S}) v_{DS-S}$$

$$50e - 6A = \dots$$

$$\dots 25e - 6 \left[ \frac{A}{V^2} \right] \left( \frac{W}{L} \right) \Big|_S (3.39V - 1V - 0.5(0.25V)) 0.25V$$

$$\left( \frac{W}{L} \right) \Big|_S = \frac{3.59}{1}$$

Inverter State:  
Input is High  
Output is Low

## Saturated Enhancement Load

$M_L$ : When  $v_i = V_{OH}$ ,  $v_o = V_{OL} = v_{SB} = 0.25V$

Inverter State:  
Input is High  
Output is Low

$$V_{TN-L} = V_{TO} + \gamma \left( \sqrt{v_{SB} + 2\phi_F} - \sqrt{2\phi_F} \right)$$

$$V_{TN-L} = 1 + 0.5 \left( \sqrt{0.25 + 0.6} - \sqrt{0.6} \right)$$

$$V_{TN-L} = 1.07V$$

$$i_{DS-L} = \frac{K'_n}{2} \left( \frac{W}{L} \right) \Big|_L (v_{GS-L} - V_{TN-L})^2$$

$$50e-6 = 12.5e-6 \left( \frac{W}{L} \right) \Big|_L (4.75 - 1.07)^2$$

$$\left( \frac{W}{L} \right) \Big|_L = \frac{1}{3.39}$$

## Saturated Enhancement Load

So the body effect requires that:

### Without the Body Effect

$$\left(\frac{W}{L}\right)\bigg|_L = \frac{1}{3.52}$$

$$\left(\frac{W}{L}\right)\bigg|_S = \frac{2.78}{1}$$

$$V_{OH} = 4.0V$$

$$V_{OL} = 0.25V$$

### With the Body Effect

$$\left(\frac{W}{L}\right)\bigg|_L = \frac{1}{3.39}$$

$$\left(\frac{W}{L}\right)\bigg|_S = \frac{3.53}{1}$$


$$V_{OH} = 3.4V$$

$$V_{OL} = 0.25V$$




# Saturated Enhancement Load

## Saturated load VTC

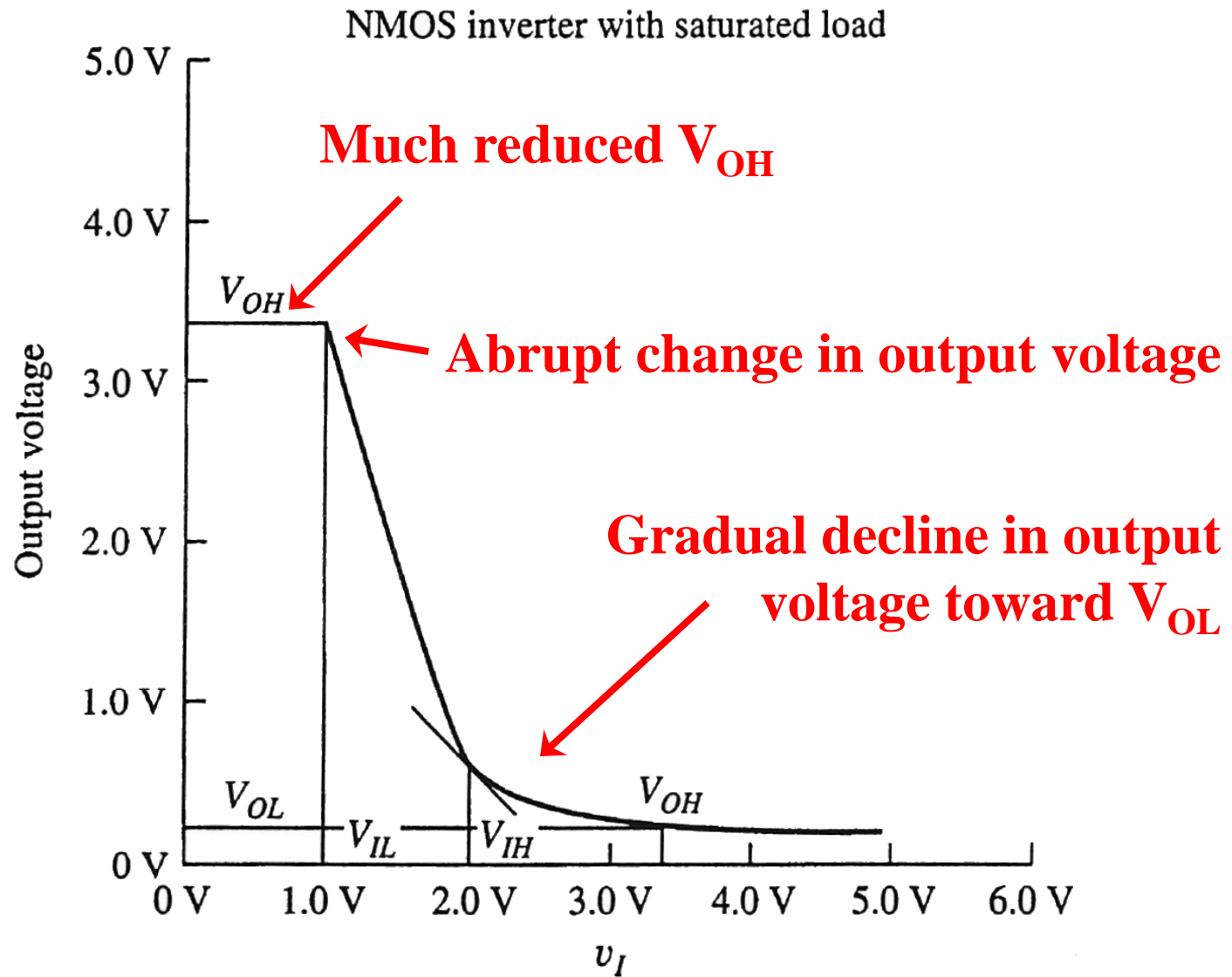

# Saturated Enhancement Load

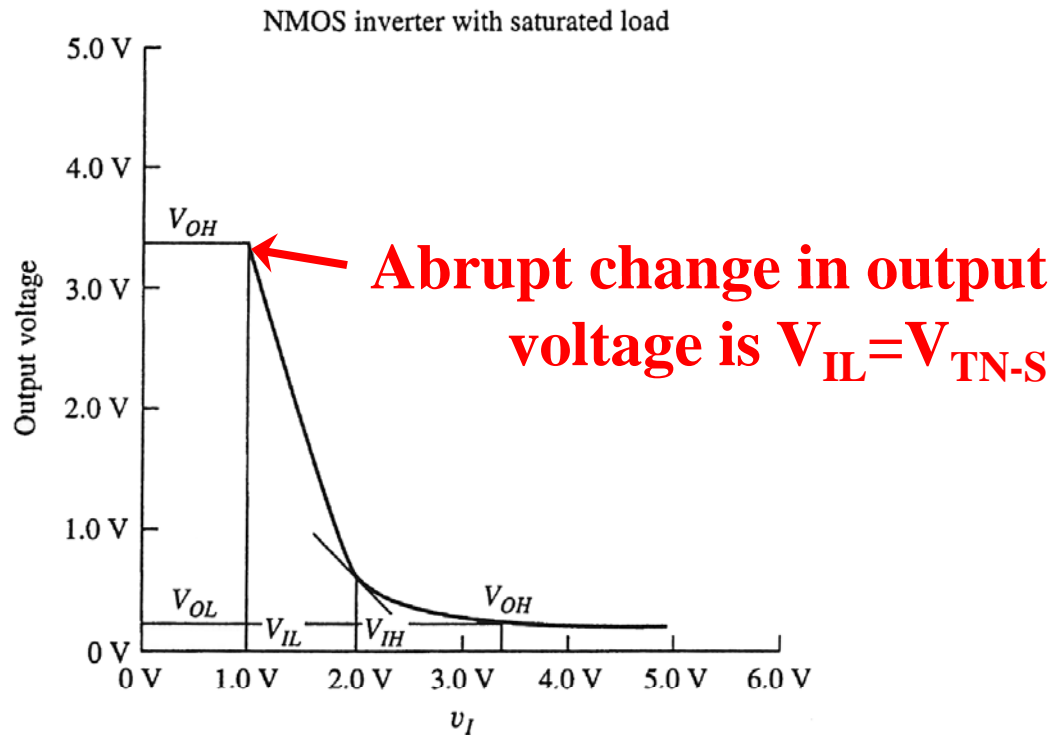

Inverter Transitional State:  
Input is Low  
Output is High

The abrupt nature of this transition is due to  $V_{TN-S} < V_{TN-L}$  due to the body effect. Thus, as  $M_S$  begins to conduct,  $M_L$  is off.

## Saturated Enhancement Load

Find  $V_{IH}$ :

Inverter Transitional State:  
Input is High  
Output is Low

$$i_{DS-S} = i_{DS-L}$$

$$K_{n-S} (v_{GS-S} - V_{TNS} - 0.5v_{DS-S})v_{DS-S} = K_{n-L} (v_{GS-L} - V_{TNL})^2$$

$$K_{n-S} (v_i - V_{TNS} - 0.5v_o)v_o = K_{n-L} (V_{DD} - v_o - V_{TNL})^2$$

solving for  $v_i$ ,

$$v_i = V_{TNS} + 0.5v_o + \frac{K_{n-L}}{2K_{n-S}} \left[ \frac{V_{DD} - V_{TNL}}{v_o} - 2(V_{DD} - V_{TNL}) + v_o \right]$$

$$\text{Assume } \frac{dv_o}{dv_i} = \left( \frac{dv_i}{dv_o} \right)^{-1}$$

Neglect since the change in  $V_{TNL}$  with  $v_o$  is slow

$$\frac{dv_i}{dv_o} = 0.5 + \frac{K_{n-L}}{2K_{n-S}} \left[ 1 - \frac{(V_{DD} - V_{TNL})^2}{v_o^2} \right] + \frac{K_{n-L}}{K_{n-S}} \left( \frac{dV_{TNL}}{dv_o} \right)$$

## Saturated Enhancement Load

Setting this derivative = -1 and solving for  $v_o$ :

$$\frac{dv_i}{dv_o} = 0.5 + \frac{K_{n-L}}{2K_{n-S}} \left[ 1 - \frac{(V_{DD} - V_{TNL})^2}{v_o^2} \right] = -1$$

$$v_o = \frac{(V_{DD} - V_{TNL})}{\sqrt{1 + 3 \frac{(W/L)_S}{(W/L)_L}}}$$

or in our case,

$$v_o = \frac{(5 - 1)}{\sqrt{1 + 3(3.53)(3.39)}} = 0.66V$$

Plugging this back into our expression for  $v_i$ ,

$$v_i = V_{TNS} + 0.5v_o + \frac{K_{n-L}}{2K_{n-S}} \left[ \frac{V_{DD} - V_{TNL}}{v_o} - 2(V_{DD} - V_{TNL}) + v_o \right]$$

$$v_i = 1 + 0.5(0.66) + \frac{1}{2(3.53)(3.39)} \left[ \frac{5 - 1}{0.66} - 2(5 - 1) + 0.66 \right] = 1.97V$$

$$V_{IH} = 1.97V$$

All assumptions can be checked and verified!

## Saturated Enhancement Load

Noise Margins:


$$NM_L = V_{IL} - V_{OL}$$

*and,*

$$NM_H = V_{OH} - V_{IH}$$
 
## Depletion Load

Recall that the depletion mode NMOS transistor has a threshold voltage that is negative, resulting it being on for  $v_{GS}=0$ .




Once again, to insure that  $M_S$  is sufficiently cutoff, we choose  $V_{OL} \ll V_{TN-S}$  or for our example where  $V_{TN-S}=1$  V,  $V_{OL}=0.25$  V. Thus, when  $v_i=V_{OL}$ ,  $M_S$  is off.

Thus, when  $M_S$  is sufficiently cutoff, ( $v_i=V_{OL} \ll V_{TN-S}$ )  $v_O=V_{OH}=V_{DD}$  due to the depletion load conducting for all output voltages allowing  $C_L$  to charge up to the power supply voltage. (I.e. unlike the enhancement case, the load transistor never cuts off).

Thus, the depletion load inverter allows  $V_{OH}$  to equal  $V_{DD}$ , a very nice improvement over the saturated Load case!

## Depletion Load

 

Using  $V_{DD} = 5V$ ,  $V_{OL} = 0.25V$ ,  $V_{TN-L} = -3V$ ,

$I_{DS} = 50\mu A$ ,  $K_n' = 25 \mu A/V^2$ ,  $\gamma = 0.5\sqrt{V}$  and  $2\phi_F = 0.6V$

and noting that when

$v_i = V_{OH}$ ,  $v_o = V_{OL} = 0.25V$  means  $v_{DS-L} = V_{DD} - v_o = 4.75V$  and

$v_{GS-S} = 0 \rightarrow M_L$  is saturated,

Thus,

$$i_{DS-L} = \frac{K_n'}{2} \left( \frac{W}{L} \right) \bigg|_L (v_{GS-L} - V_{TN-L})^2$$

$$i_{DS-L} = \frac{K_n'}{2} \left( \frac{W}{L} \right) \bigg|_L (V_{TN-L})^2$$

but due to the Body - Source voltage effect on  $M_L$ ,

$V_{TN-L} = V_{TNO} + \gamma(\sqrt{v_{SB} + 2\phi_F} - \sqrt{2\phi_F})$  or in our case,


$$V_{TN-L} = -3V + 0.5\sqrt{V}(\sqrt{0.25V + 0.6V} - \sqrt{0.6V}) = -2.93V$$

Thus,

$$\left( \frac{W}{L} \right) \bigg|_L = 0.466 = \frac{1}{2.15}$$

Inverter State:  
Input is High  
Output is Low

## Depletion Load

 

Inverter State:  
Input is High  
Output is Low

Using  $V_{DD} = 5V$ ,  $V_{OL} = 0.25V$ ,  $V_{TN-S} = 1V$ ,

$$I_{DS} = 50\mu A, K_n' = 25 \mu A/V^2, \gamma = 0.5\sqrt{V}$$

and noting that when

$v_i = V_{OH}$ ,  $v_o = V_{OL} = 0.25V$  means  $v_{DS-S} = v_o = 0.25V$  and

$v_{GS-S} = V_{OH} = V_{DD} = 5V \rightarrow M_S$  is in the linear region,

$$i_{DS} = 50\mu A = K_n' \left( \frac{W}{L} \right) \Big|_S (v_{GS-S} - V_{TN-S} - 0.5v_{DS-S}) v_{DS-S}$$

$$50e-6 = 25e-6 \left( \frac{W}{L} \right) \Big|_S (5 - 1 - .125) 0.25$$

$$\left( \frac{W}{L} \right) \Big|_S = \frac{2.06}{1}$$

NOTE : This is the same as in the resistive load case!




## Depletion Load

Inverter Transitional State:

Input is Low

Output is High

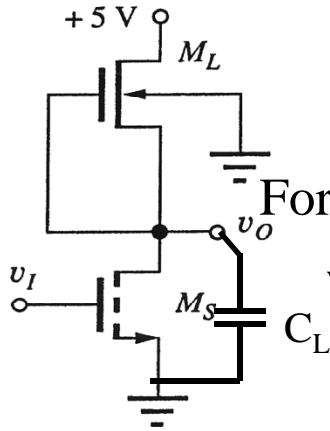

$V_{IL}$ :

For  $v_i$  near  $V_{IL}$ ,  $v_{DS-S}$  will be large and  $v_{DS-L}$  will be small. Thus, we assume:  $M_S$  is saturated and  $M_L$  is in the linear region,

$$i_{DS-S} = i_{DS-L}$$

$$K_{n-S} (v_{GS-S} - V_{TN-S})^2 = K_{n-L} (v_{GS-L} - V_{TN-L} - 0.5v_{DS-L})v_{DS-L}$$

$$K_{n-S} (v_i - V_{TN-S})^2 = K_{n-L} (0 - V_{TN-L} - 0.5(V_{DD} - v_o))(V_{DD} - v_o)$$

Solving for  $v_o$ ,


$$v_o = V_{DD} + V_{TN-L} + \sqrt{V_{TN-L}^2 - K_R (v_i - V_{TN-S})^2}$$

$$\text{where } K_R = \frac{K_{n-S}}{K_{n-L}}$$

$$\text{So, } \frac{dv_o}{dv_i} = \frac{\cancel{dV_{TN-L}}}{\cancel{dv_i}} + \frac{1}{2} \left[ V_{TN-L}^2 - K_R (v_i - V_{TN-S})^2 \right]^{-\frac{1}{2}} \left[ 2V_{TN-L} \frac{\cancel{dV_{TN-L}}}{\cancel{dv_i}} - 2K_R (v_i - V_{TN-S}) \right]$$

$$\frac{dv_o}{dv_i} = \frac{-K_R (v_i - V_{TN-S})}{\sqrt{V_{TN-L}^2 - K_R (v_i - V_{TN-S})^2}}$$

# Depletion Load

 

$V_{IL}$ :

Setting this derivative equal to -1 and solving for  $v_i = V_{IL}$ ,

$$\frac{dv_o}{dv_i} = \frac{-K_R (v_i - V_{TN-S})}{\sqrt{V_{TN-L}^2 - K_R (v_i - V_{TN-S})^2}} = -1$$

$$v_i = V_{IL} = V_{TN-S} - \frac{V_{TN-L}}{\sqrt{K_R^2 + K_R}}$$

Note : that  $V_{TN-L}$  is a function of  $V_{SB}$  ( $V_{TN-S}$  is not!)

Assume a value of  $v_O$  ( $\sim V_{DD}$ )


$$V_{TN-L} = V_{TNO} + \gamma \left( \sqrt{v_{SB} + 2\phi_F} - \sqrt{2\phi_F} \right) \text{ using } v_{SB} = v_O$$

$$v_i = V_{IL} = V_{TN-S} - \frac{V_{TN-L}}{\sqrt{K_R^2 + K_R}}$$

$$v_o = V_{DD} + V_{TN-L} + \sqrt{V_{TN-L}^2 - K_R (v_i - V_{TN-S})^2}$$

Iterate until convergence!

## Depletion Load

 

$V_{IL}$ :

For our numerical example:


$$V_{TN-L} = -2.23 \text{ V} \quad (> -3 \text{ V})$$

$$V_{IL} = 1.50 \text{ V}$$

$$v_O = 4.74 \text{ V}$$

Also, our assumptions regarding transistor operation conditions are correct.

# Depletion Load

 

$V_{IH}$ :

For  $v_i$  near  $V_{IH}$ ,  $v_{DS-S}$  will be small and  $v_{DS-L}$  will be large. Thus, we assume:  $M_L$  is saturated and  $M_S$  is in the linear region,

$$i_{DS-L} = i_{DS-S}$$

$$K_{n-L} (v_{GS-L} - V_{TN-L})^2 = K_{n-S} (v_{GS-S} - V_{TN-S} - 0.5v_{DS-S})v_{DS-S}$$

$$K_{n-L} (0 - V_{TN-L})^2 = K_{n-S} (v_i - V_{TN-S} - 0.5(v_o))(v_o)$$


$$\text{Solving for } v_i, \quad v_i = V_{TN-S} + \frac{v_o}{2} + \frac{K_L}{2K_S} \frac{V_{TN-L}^2}{v_o}$$

$$\text{Assuming, } \frac{dv_o}{dv_i} = \left[ \frac{dv_i}{dv_o} \right]^{-1}$$

$$\frac{dv_i}{dv_o} = \frac{1}{2} - \frac{K_L}{2K_S} \frac{V_{TN-L}^2}{(v_o)^2} + \frac{2K_L}{2K_S} \frac{V_{TN-L}}{v_o} \left( \frac{\cancel{dV_{TN-L}}}{\cancel{dv_o}} \right)$$

$$\frac{dv_i}{dv_o} = \frac{1}{2} - \frac{1}{2K_R} \frac{V_{TN-L}^2}{(v_o)^2}, \quad \text{where } K_R = \frac{K_{n-S}}{K_{n-L}}$$

## Depletion Load

 

$V_{IH}$ : Setting the derivative equal to -1 and solving for  $v_O$ ,

$$\frac{dv_i}{dv_o} = \frac{1}{2} - \frac{1}{2K_R} \frac{V_{TN-L}^2}{(v_o)^2} = -1$$

$$v_o = -\frac{V_{TN-L}}{\sqrt{3K_R}}$$

Thus,

$$v_i = V_{TN-S} + \frac{v_o}{2} + \frac{K_L}{2K_S} \frac{V_{TN-L}^2}{v_o}$$


Inverter Transitional State:  
Input is High  
Output is Low

$$v_i = V_{TN-S} + \frac{\left(-\frac{V_{TN-L}}{\sqrt{3K_R}}\right)}{2} + \frac{K_L}{2K_S} \frac{V_{TN-L}^2}{\left(-\frac{V_{TN-L}}{\sqrt{3K_R}}\right)}$$

$$v_i = V_{TN-S} - \left(\frac{V_{TN-L}}{2\sqrt{3K_R}}\right) - \frac{1}{2K_R} \frac{V_{TN-L}^2 \sqrt{3K_R}}{V_{TN-L}}$$

Cont'd...

## Depletion Load

 

$V_{IH}$ : Cont'd...

$$v_i = V_{TN-S} - \left( \frac{V_{TN-L}}{2\sqrt{3K_R}} \right) - \frac{1}{2K_R} \frac{V_{TN-L}^2 \sqrt{3K_R}}{V_{TN-L}}$$


$$v_i = V_{TN-S} - \frac{V_{TN-L}}{2\sqrt{3K_R}} \left( \frac{K_R}{K_R} \right) - \frac{V_{TN-L} \sqrt{3K_R}}{2K_R} \left( \frac{\sqrt{3K_R}}{\sqrt{3K_R}} \right)$$

$$v_i = V_{TN-S} - \frac{V_{TN-L} K_R + V_{TN-L} 3K_R}{2K_R \sqrt{3K_R}}$$

$$v_i = V_{TN-S} - \frac{2V_{TN-L}}{\sqrt{3K_R}}$$

$$v_i = V_{IH} = V_{TN-S} + 2v_O$$

# Depletion Load

 

$V_{IH}$ : Cont'd...

Assume a value of  $V_{TN-L}$  ( $\sim V_{TNO-L}$ )

$$v_O = -\frac{V_{TN-L}}{\sqrt{3K_R}}$$

$$V_{IH} = V_{TN-S} + 2v_O$$

$$V_{TN-L} = V_{TNO} + \gamma \left( \sqrt{v_{SB} + 2\phi_F} - \sqrt{2\phi_F} \right) \text{ using } v_{SB} = v_O$$

**Iterate until convergence!**


For our numerical example:

$$V_{TN-L} = -2.80 \text{ V}, V_{IH} = 2.53 \text{ V}, v_O = 0.77 \text{ V}$$

Also, our assumptions regarding transistor operation conditions are correct.


# Depletion Load

## VTC

 




# NMOS NOR Gate

 

If either input,  $v_{i-a}$  or  $v_{i-b}$  goes high ( $v_i = V_{OH}$ ),  $v_o$  goes low ( $v_o = V_{OL}$ )

## NMOS NAND Gate

 

If both inputs,  $v_{i-a}$  or  $v_{i-b}$  goes high ( $v_i = V_{OH}$ ),  $v_o$  goes low ( $v_o = V_{OL}$ )

# Depletion Load

The Depletion Load NMOS gate...


... takes up much less area, leading to higher density (more complex and faster) circuitry.

... has a  $V_{OH} = V_{DD}$


... switches faster leading to higher frequency operation.

... dominated microprocessor design until “CMOS” or Combination-MOS replaced it.

# CMOS Logic Gates

 


 NMOS Logic Gates “waste” power by having a current flow from  $V_{DD}$  to ground during the “0” output state. All we really need during this state is a current path to discharge  $C_L$ . Analogous to a Class A output stage.




CMOS Logic Gates eliminate this DC or “Static” power dissipation. CMOS logic gates only dissipate power during a switching event. Once in a state, no power is used. Analogous to a class B output stage (push pull).

# CMOS Logic Gates

 


- CMOS Inverter uses one NMOS and 1 PMOS transistor.
- Each Transistor is design to have  $V_{TN} = -V_{TP}$  (recall for PMOS,  $V_{TP} < 0$ )
- Since the Body can be connected to source for the NMOS and VDD for the PMOS, there is no problem with the body effect *FOR THE CMOS INVERTER (ONLY)*

## CMOS Logic Gates

 

 - For  $v_i > V_{TN}$  and  $v_i > V_{DD} + V_{TP}$   
(example: if  $v_i = 5V$ ,  $V_{TN} = 1V$  and  $V_{TP} = -1V$  this is satisfied)
- $v_{GS-P} > V_{TP}$  ( $v_{SG-P} < -V_{TP}$ ),  $v_{GS-N} > V_{TN}$
- $M_P$  is OFF,  $M_N$  is ON
- Load Capacitor discharges all the way down to ground




- For  $v_i < V_{TN}$  and  $v_i < V_{DD} + V_{TP}$   
(example: if  $v_i = 0V$ ,  $V_{TN} = 1V$  and  $V_{TP} = -1V$  this is satisfied)
- $v_{GS-P} < V_{TP}$  ( $v_{SG-P} > -V_{TP}$ ),  $v_{GS-N} < V_{TN}$
- $M_P$  is ON,  $M_N$  is OFF
- Load Capacitor charges all the way up to  $V_{DD}$ .

Thus,  $V_{OL} = 0V$  and  $V_{OH} = V_{DD}$

and there is ***NO STEADY STATE DC CURRENT FLOW***
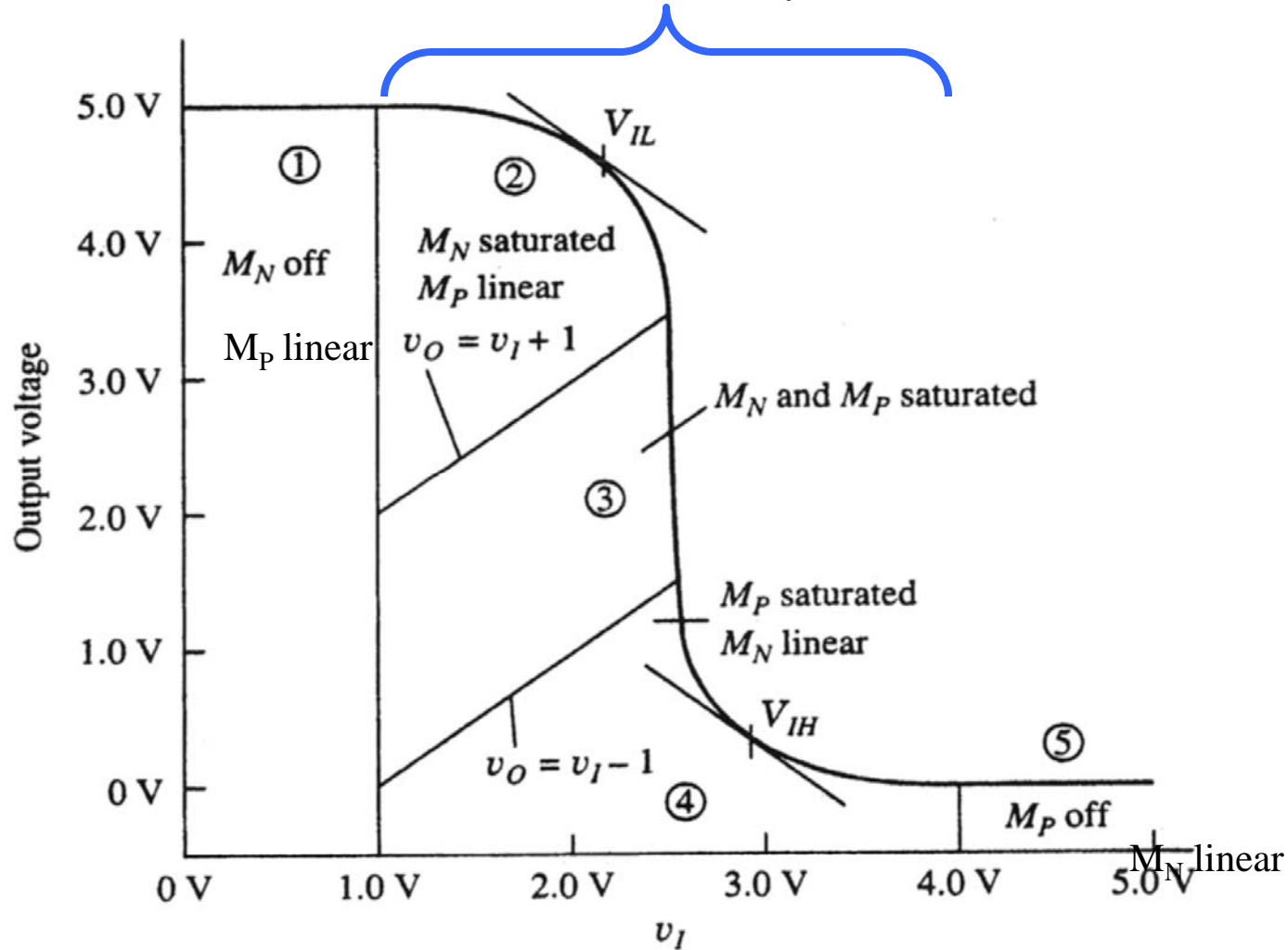
# CMOS Logic Gates

Only during switching are both transistors turned on simultaneously



# CMOS Logic Gates

$V_{IH}$ :

For  $v_i \sim V_{IH}$ ,  $v_{DS-P}$  is large and  $v_{DS-N}$  is small implying  $M_P$  is saturated and  $M_N$  is linear

Inverter Transitional State:  
Input is High  
Output is Low

$$i_{DS-N} = i_{DS-P}$$

$$K_n (v_{GS-N} - V_{TN} - 0.5v_{DS-N})v_{DS-N} = \frac{K_p}{2} (v_{SG-P} + V_{TP})^2$$

$$K_n (v_i - V_{TN} - 0.5v_o)v_o = \frac{K_p}{2} ((V_{DD} - v_i) + V_{TP})^2$$

Solving for  $v_o$ ,

$$v_o = v_i - V_{TN} \pm \sqrt{(v_i - V_{TN})^2 - \frac{(V_{DD} - v_i + V_{TP})^2}{K_R}} \quad \text{where } K_R = \frac{K_n}{K_p}$$

As before, taking the derivative,  $\frac{dv_o}{dv_i}$  and setting this equal to -1 and solving for  $v_i$ ,

$$V_{IH} = v_i \left| \frac{dv_o}{dv_i} = -1 \right. = \frac{2K_R (V_{DD} - V_{TN} + V_{TP})}{(K_R - 1)\sqrt{1 + 3K_R}} - \frac{(V_{DD} - K_R V_{TN} + V_{TP})}{(K_R - 1)}$$



# CMOS Logic Gates

$V_{IH}$  (cont'd):

For a very useful case where  $K_n=K_p$  ( $K_R=1$ )

Do not use this equation without mathematical manipulation to eliminate  $(K_R - 1)$  terms in denominator

$$V_{IH} = v_i \left| \frac{dv_o}{dv_i} = -1 \right. = \frac{2K_R (V_{DD} - V_{TN} + V_{TP})}{(K_R - 1)\sqrt{1 + 3K_R}} - \frac{(V_{DD} - K_R V_{TN} + V_{TP})}{(K_R - 1)}$$

Instead, go back to,

$$v_o = v_i - V_{TN} \pm \sqrt{(v_i - V_{TN})^2 - \frac{(V_{DD} - v_i + V_{TP})^2}{K_R}} \quad \text{where } K_R = \frac{K_n}{K_p} = 1$$

As before, taking the derivative,  $\frac{dv_o}{dv_i}$  and setting this equal to -1 and solving for  $v_i$ ,

$$V_{IH} = v_i \left| \frac{dv_o}{dv_i} = -1 \right. = \frac{(5V_{DD} + 3V_{TN} + 5V_{TP})}{8} \quad \text{For } K_R = \frac{K_n}{K_p} = 1$$

# CMOS Logic Gates

$V_{IL}$ :

For  $v_i \sim V_{IL}$ ,  $v_o$  is large. Thus,  $v_{DS-P}$  is small and  $v_{DS-N}$  is large implying  $M_P$  is linear and  $M_N$  is saturated

Inverter Transitional State:

Input is Low

Output is High

$$i_{DS-P} = i_{DS-N}$$

$$K_p (v_{SG-P} + V_{TP} - 0.5V_{SD-P})V_{SD-P} = \frac{K_n}{2} (v_{GS-N} - V_{TN})^2$$

$$K_p ((V_{DD} - v_i) + V_{TP} - 0.5(V_{DD} - v_o))(V_{DD} - v_o) = \frac{K_n}{2} (v_i - V_{TN})^2$$

Again, solving for  $v_o$ , taking the derivative,  $\frac{dv_o}{dv_i}$  and setting this equal

to -1 and solving for  $v_i$ ,


$$V_{IL} = v_i \left|_{\frac{dv_o}{dv_i} = -1} = \frac{2\sqrt{K_R} (V_{DD} - V_{TN} + V_{TP})}{(K_R - 1)\sqrt{K_R + 3}} - \frac{(V_{DD} - K_R V_{TN} + V_{TP})}{(K_R - 1)}$$

# CMOS Logic Gates

$V_{IL}$  (cont'd):

For a very useful case where  $K_n=K_p$  ( $K_R=1$ )

$$V_{IL} = v_i \left| \frac{dv_o}{dv_i} = -1 \right. = \frac{2\sqrt{K_R} (V_{DD} - V_{TN} + V_{TP})}{(K_R - 1)\sqrt{K_R + 3}} - \frac{(V_{DD} - K_R V_{TN} + V_{TP})}{(K_R - 1)}$$

 

$$V_{IL} = v_i \left| \frac{dv_o}{dv_i} = -1 \right. = \frac{(3V_{DD} + 5V_{TN} + 3V_{TP})}{8} \quad \text{for } K_R = \frac{K_n}{K_p} = 1$$

As always, we can calculate the appropriate noise margins.

# CMOS Logic Gates

Example: Calculate the noise margins for a logic family with  $V_{DD}=3.3V$ ,  $V_{TN}=1V$ ,  $V_{TP}= -0.75V$  and  $K_R=1$ :

$$V_{OH} = 3.3V$$

$$V_{OL} = 0V$$

$$V_{IH} = \frac{(5V_{DD} + 3V_{TN} + 5V_{TP})}{8} = \frac{(5(3.3) + 3(0.75) + 5(-0.75))}{8} = 1.86V$$

$$V_{IL} = \frac{(3V_{DD} + 5V_{TN} + 3V_{TP})}{8} = \frac{(3(3.3) + 5(0.75) + 3(-0.75))}{8} = 1.43V$$

$$NM_H = V_{OH} - V_{IH} = V_{DD} - V_{IH} = 1.43V$$

$$NM_L = V_{IL} - V_{OL} = V_{IL} = 1.43V$$

# CMOS Logic Gates

Dynamic Response of a CMOS Inverter:

For the case when  $V_{TN} = -V_{TP}$  and  $K_R = 1$ , the transistors are said to be “electrically equivalent” meaning they have identically “opposite” current-voltage characteristics (“on resistance” in the linear state is the same, the voltage turn on points are symmetric etc...).

In this case, the turn on transient and the turn off transient are identical (charging of  $C_L$  is through a resistor,  $R_{on-PMOS}$  and discharging of  $C_L$  is through a resistor,  $R_{on-NMOS}$  where  $R_{on-PMOS} = R_{on-NMOS}$ )

$$R_{on-NMOS} = \frac{1}{K_n (V_{DD} - V_{TN})} \quad \text{and} \quad R_{on-PMOS} = \frac{1}{K_p (V_{DD} + V_{TP})}$$

# CMOS Logic Gates

The charging time is related to the “RC time constant” of this resistance and the load capacitor. Detailed analysis indicates a slight elongation of the time constant (due to the resistance of the channel changing during the switching cycle) leading to,

$$\tau_{\text{PHL}} = 1.29R_{\text{on-NMOS}}C_L \quad \text{and} \quad \tau_{\text{PLH}} = 1.29R_{\text{on-PMOS}}C_L$$

It can also be found that,

$$t_f = 2\tau_{\text{PHL}} \quad \text{and} \quad t_r = 2\tau_{\text{PLH}}$$

For  $K_R=1$ , these are equal greatly simplifying timing designs in complex circuits.

$$\tau_P = \frac{\tau_{\text{PHL}} + \tau_{\text{PLH}}}{2} = \tau_{\text{PLH}} = \tau_{\text{PHL}}$$

# CMOS Logic Gates

## Power Considerations:

Since power is only dissipated during a switching event, it can be shown that for a CMOS inverter the power dissipated is,


$$P_D = C_L V_{DD}^2 f$$

Where  $f$  is the switching frequency (assuming a 50% duty cycle).

Note that for DC,  $f=0$ ,  $P_D=0$  as expected

# CMOS Logic Gates

## CMOS NOR GATE:

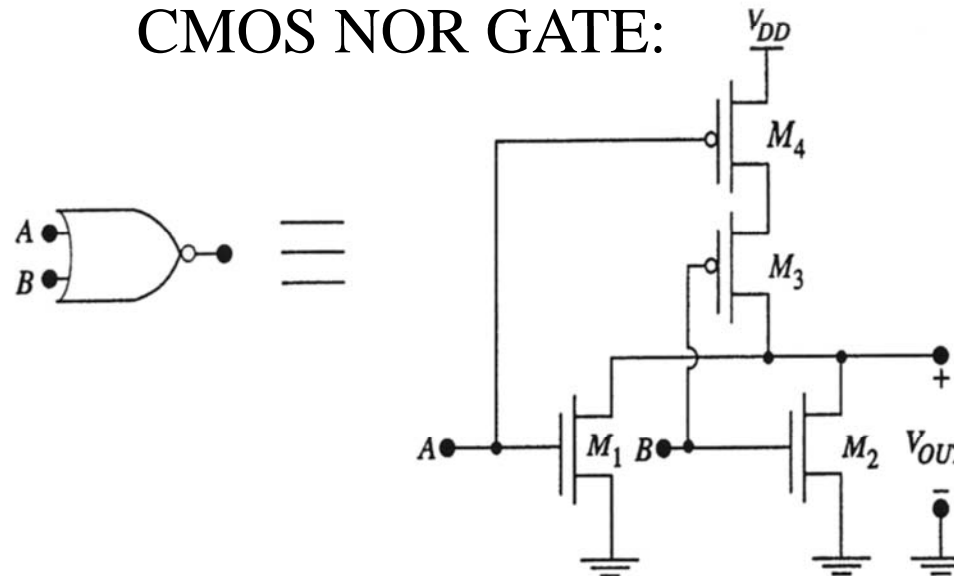


- If both A and B are low,  $M_1$  and  $M_2$  are off, and  $M_3$  and  $M_4$  are on allowing  $V_{out}$  to be pulled high
- If either A, B or both are high,  $M_1$  or  $M_2$  or both are on and  $M_3$ , or  $M_4$  or both are off allowing  $V_{out}$  to be pulled low
- Note that the body effect would modify our design (W/L) of  $M_3$



# CMOS Logic Gates

## CMOS NAND GATE:

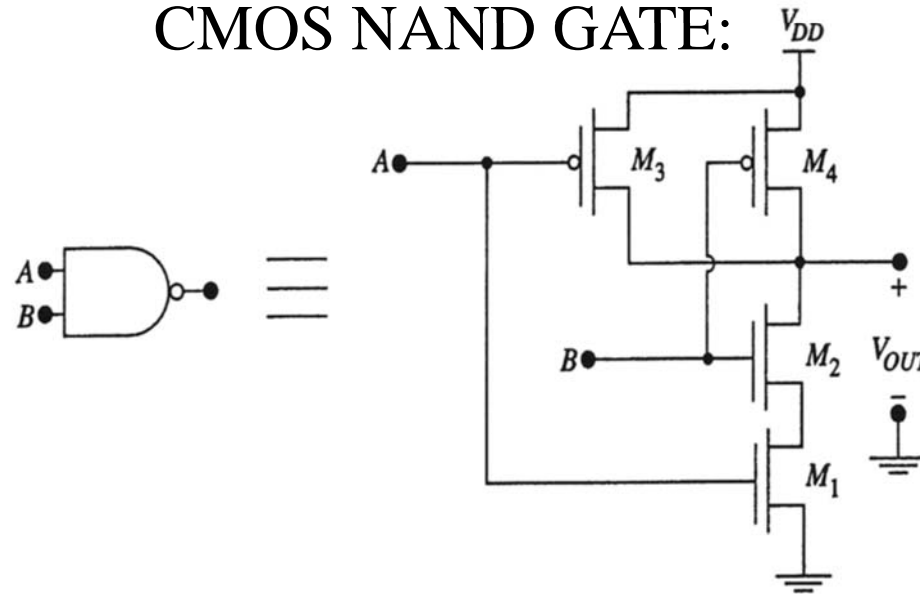

- If both A and B are high,  $M_1$  and  $M_2$  are on, and  $M_3$  and  $M_4$  are off allowing  $V_{out}$  to be pulled low
- If either A, B or both are low,  $M_1$  or  $M_2$  or both are off and  $M_3$ , or  $M_4$  or both are on allowing  $V_{out}$  to be pulled high
- Note that the body effect would modify our design (W/L) of  $M_2$