

RF Energy Harvesting


Presented by: James Ferguson

Overview

- ⦿ Concept
- ⦿ Advantages and Disadvantages
- ⦿ Anatomy
 - Antenna
 - Matching Circuit
 - Rectifier
 - Charging

RF Harvesting Concept

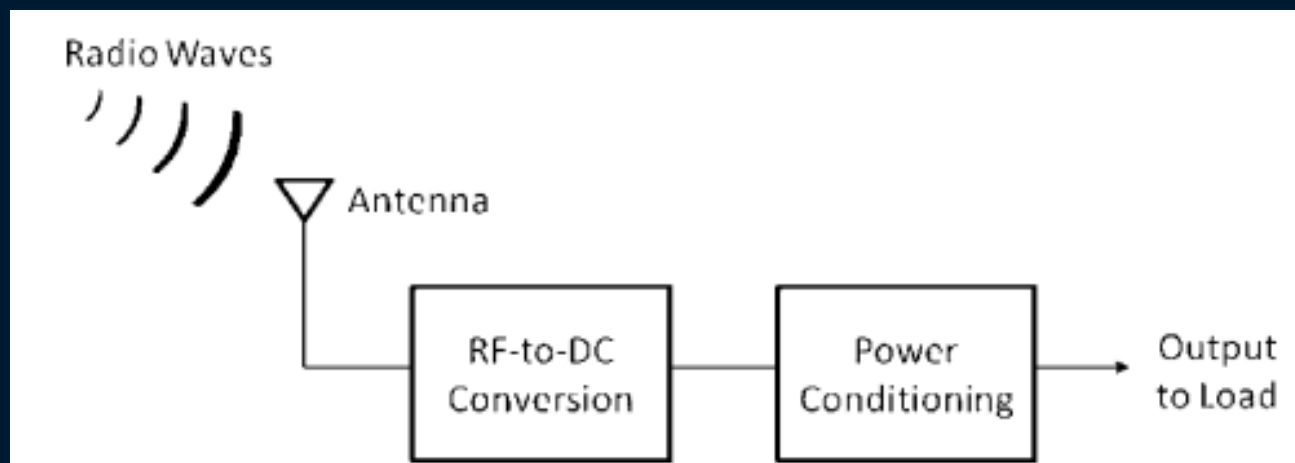- RF waves contain energy
- Convert RF energy into DC power
- Low power applications



Advantages / Disadvantages

ADVANTAGES

- ◉ Abundance
- ◉ Independent of weather
- ◉ Indoors capability
- ◉ Small footprint
- ◉ No blackout period

DISADVANTAGES

- ◉ Low power
- ◉ Frequency dependent
- ◉ Line of Sight

RF Sources

- ⦿ Intentional Sources
- ⦿ Anticipated Ambient Sources
- ⦿ Unknown Ambient Sources

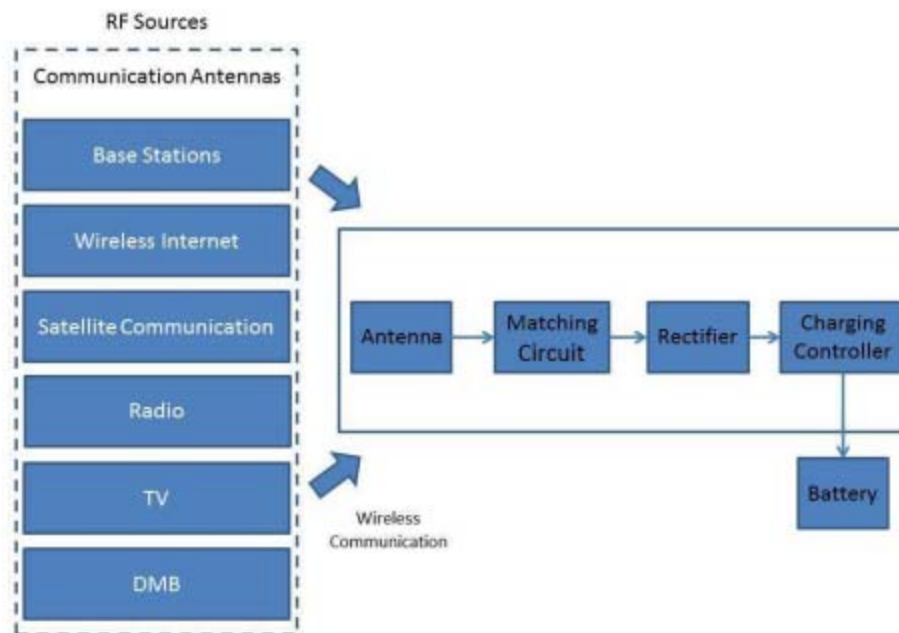


Figure 1.6: RF energy harvesting system architecture

Power and Efficiency

Friss Equation: Free space path loss of TX sig


$$P_R = P_T \frac{G_T G_R \lambda^2}{(4\pi d)^2 L},$$

Efficiency of Harvesting

$$\eta = \frac{P_{dc}}{P_r} * 100$$

Antenna

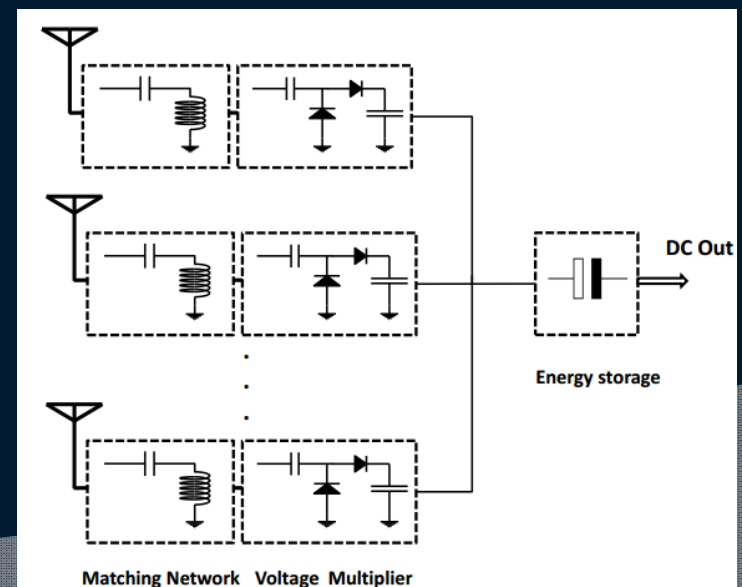- Capturing RF signals
- Miniaturized size and high antenna gain
- Sensitivity
- Multiple Antennas



Matching Circuit

- Reduce the transmission loss from an antenna to a rectifier circuit
- Increase the input voltage of a rectifier circuit
- Reflection Equation


$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Multiplier/Rectifier

⦿ Dickinson Rectifier Design


⦿ Schottky barrier diodes

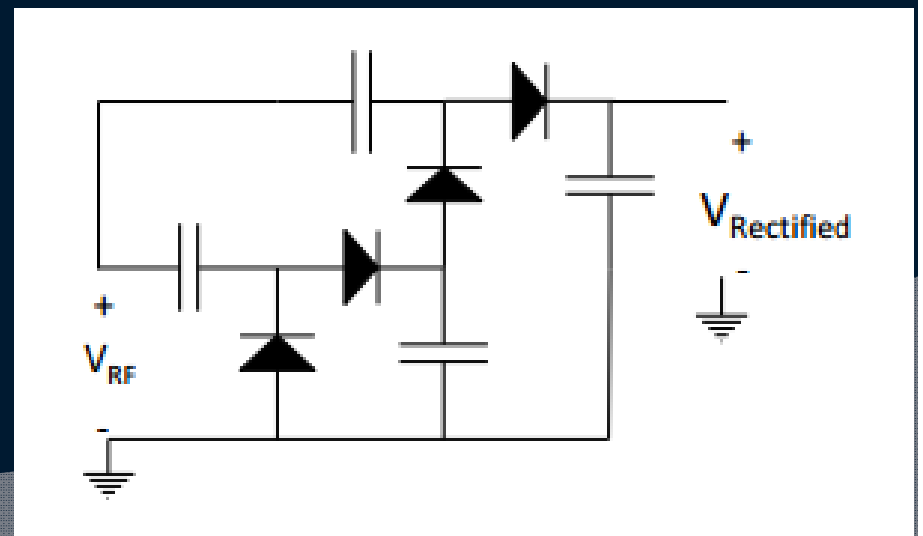- Low built in voltage
- Fast switching time
- High saturation current





Rectifier Stages

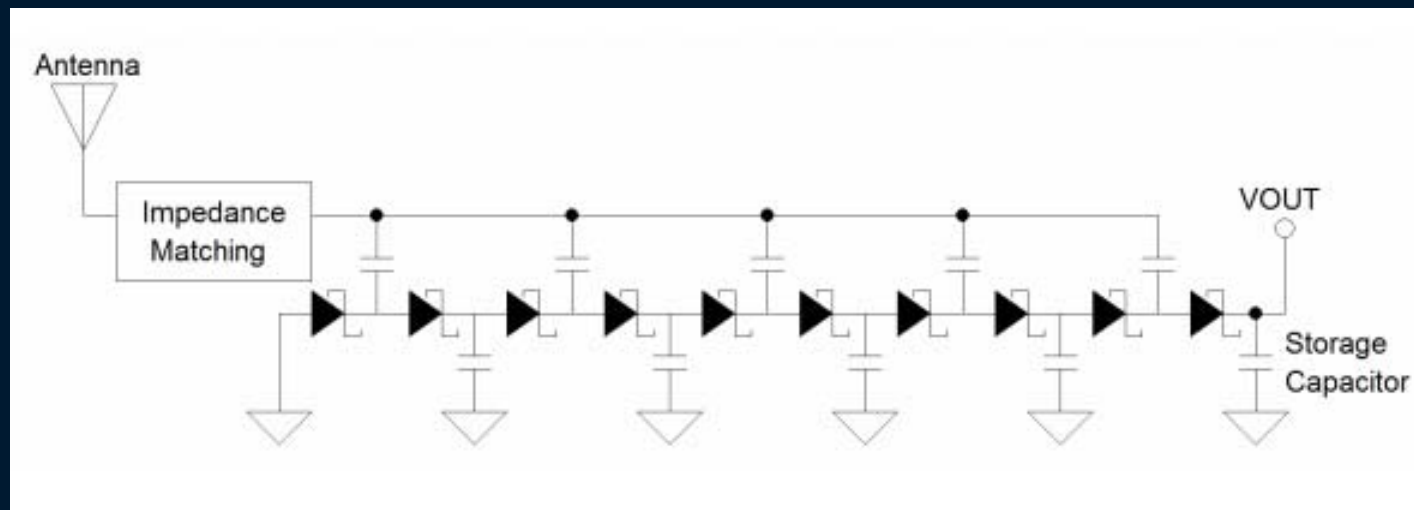
- Proportional to output voltage
- Capacitor parasitic effects



Rectifier Stages
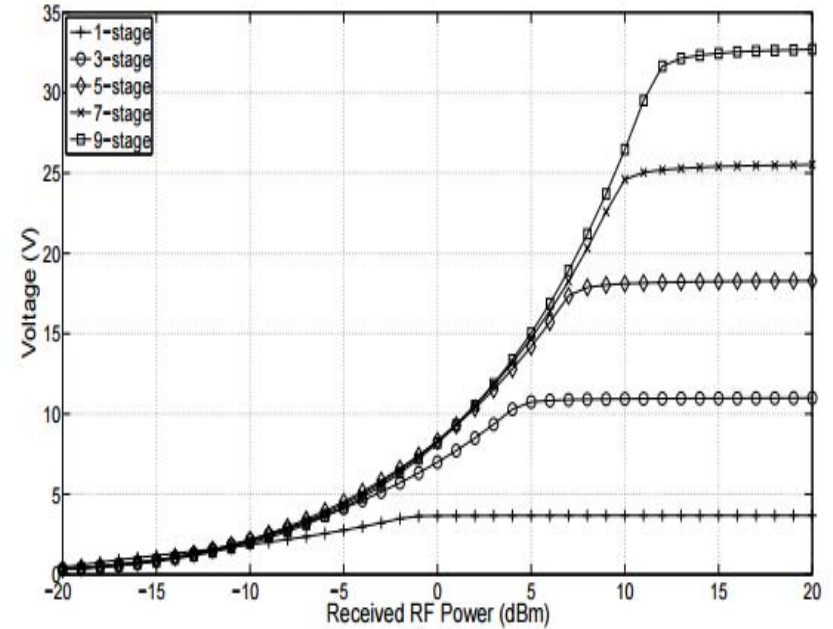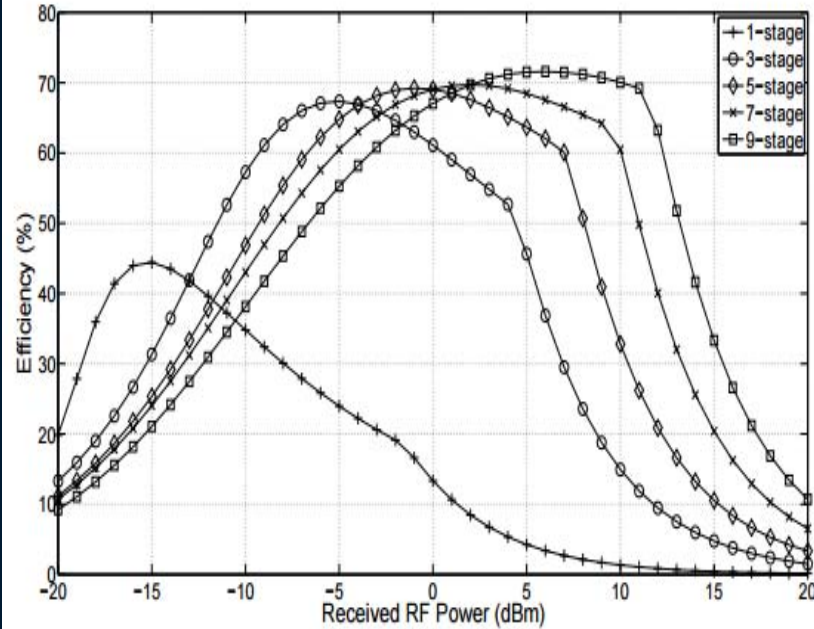
$$V_{out} = \frac{nV_0}{nR_0 + R_L} R_L = V_0 \frac{1}{\frac{R_0}{R_L} + \frac{1}{n}}$$



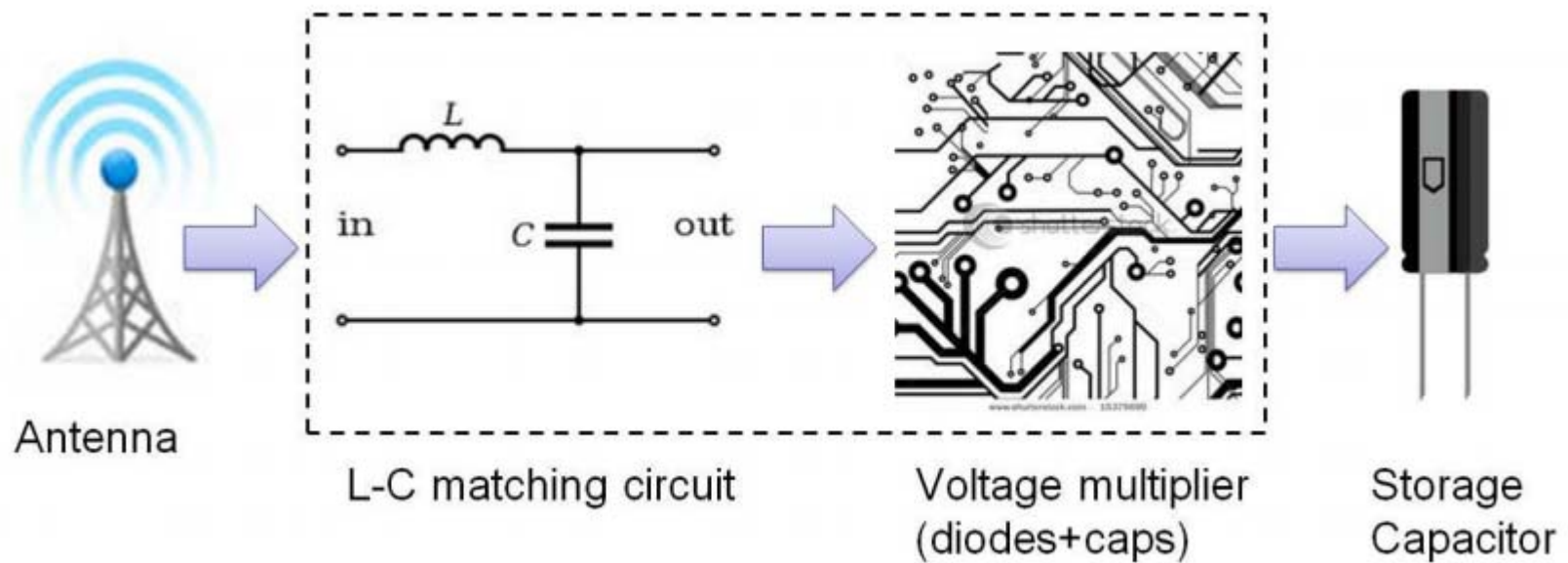

Summary

- ⦿ Concept
- ⦿ Advantages and Disadvantages
- ⦿ Anatomy
 - Antenna
 - Matching Circuit
 - Rectifier
 - Charging

Questions?